

# Electrical Engineering 1

## 12026105

### Chapter 10

## Sinusoidal Steady-State Analysis

## Learning Objectives

*By using the information and exercises in this chapter you will be able to:*

1. Analyze electrical circuits in the frequency domain using nodal analysis.
2. Analyze electrical circuits in the frequency domain using mesh analysis.
3. Apply the superposition principle to frequency domain electrical circuits.
4. Apply source transformation in frequency domain circuits.
5. Understand how Thevenin and Norton equivalent circuits can be used in the frequency domain.
6. Analyze electrical circuits with op amps.

# Sinusoidal Steady-State Analysis Chapter 10

 Introduction

 Nodal Analysis

 Mesh Analysis

 Superposition Theorem


 Source Transformation

 Thevenin and Norton Equivalent Circuits

# 10.1 Introduction (1)

## Steps to Analyze AC Circuits:

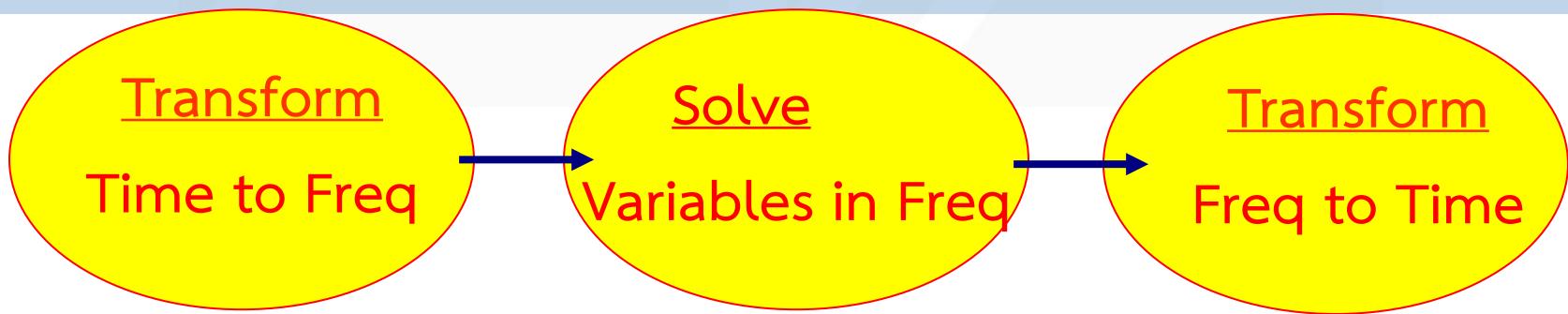1. Transform the circuit to the phasor or frequency domain.
2. Solve the problem using circuit techniques (nodal analysis, mesh analysis, superposition, etc.).
3. Transform the resulting phasor to the time domain.




# 10.1 Introduction (2)

Element	Impedance
$R$	$Z = R$
$L$	$Z = j\omega L$
$C$	$Z = \frac{1}{j\omega C}$
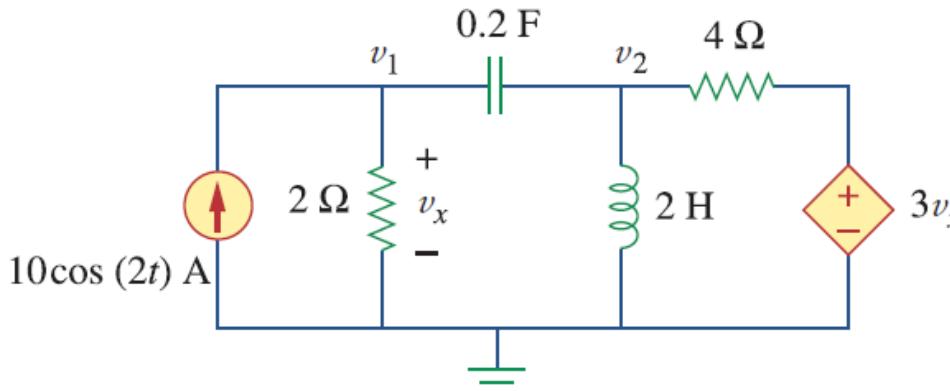
# 10.2 Nodal Analysis (1)

Ex.1 Using nodal analysis, find  $v_1$  and  $v_2$  in the circuit of figure below.




$$\frac{v_1 - v_2}{-j2.5} + \frac{v_1}{2} = 10\angle 0^\circ \Leftrightarrow (-1 + j1.25)v_1 + v_2 = 25\angle 90^\circ$$

$$\frac{v_2 - v_1}{-j2.5} + \frac{v_2}{j4} + \frac{v_2 - 3v_1}{4} = 0 \Leftrightarrow -4(v_2 - v_1) + 2.5v_2 + j2.5v_2 - j7.5v_1 = 0$$

$$(4 - j7.5)v_1 = (1.5 - j2.5)v_2 \Leftrightarrow v_1 = \left( \frac{24.75 + j1.25}{72.25} \right) v_2$$

$$(-1 + j1.25) \left( \frac{24.75 + j1.25}{72.25} \right) v_2 + v_2 = 25\angle 90^\circ \Leftrightarrow (0.636 + j0.411)v_2 = 25\angle 90^\circ$$

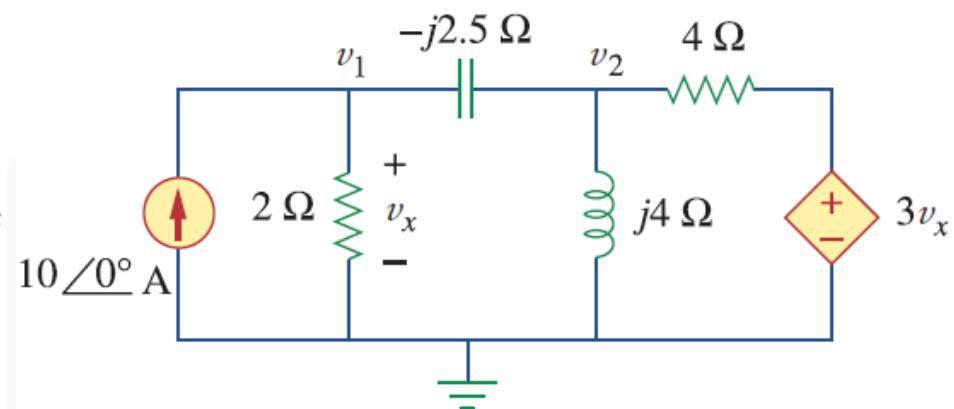Answer:  $v_1(t) = 11.32 \cos(2t + 60.01^\circ) V$      $v_2(t) = 33.02 \cos(2t + 57.12^\circ) V$



$$(0.757\angle 32.8^\circ)v_2 = 25\angle 90^\circ$$

$$v_2 = \frac{25\angle 90^\circ}{0.757\angle 32.8^\circ} = 33.02\angle 57.2^\circ$$


$$v_1 = \left( \frac{24.75 + j1.25}{72.25} \right) 33.02\angle 57.2^\circ$$

$$= (0.343\angle 2.89^\circ)(33.02\angle 57.2^\circ)$$

$$= 11.32\angle 60.09^\circ$$
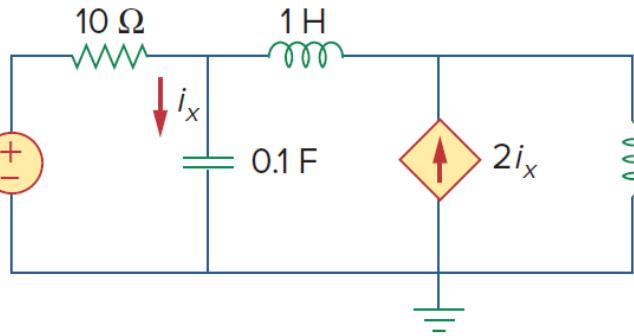
# 10.2 Nodal Analysis (2)

Ex.2 Find  $i_x$  in the circuit of Fig. using nodal analysis.



Applying KCL at node 1,

$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$

or

$$(1 + j1.5)\mathbf{V}_1 + j2.5\mathbf{V}_2 = 20$$

At node 2,


$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$

But  $\mathbf{I}_x = \mathbf{V}_1 / -j2.5$ . Substituting this gives

$$\frac{2\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$

By simplifying, we get

$$11\mathbf{V}_1 + 15\mathbf{V}_2 = 0$$

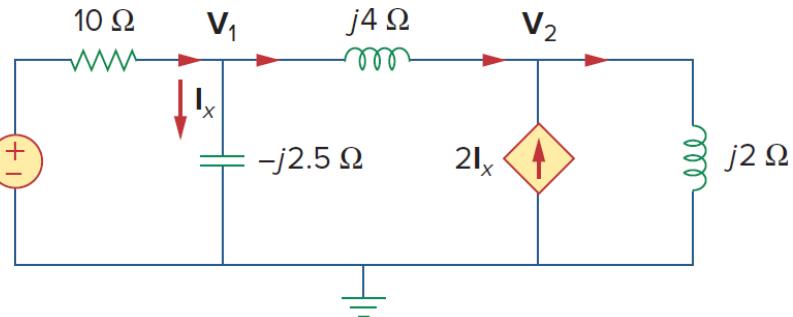

Equations can be put in matrix form as

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

We obtain the determinants as

$$\Delta = \begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix} = 15 - j5$$

$$\Delta_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix} = 300, \quad \Delta_2 = \begin{vmatrix} 1 + j1.5 & 20 \\ 11 & 0 \end{vmatrix} = -220$$

$$\mathbf{V}_1 = \frac{\Delta_1}{\Delta} = \frac{300}{15 - j5} = 18.97 \angle 18.43^\circ \text{ V}$$

$$\mathbf{V}_2 = \frac{\Delta_2}{\Delta} = \frac{-220}{15 - j5} = 13.91 \angle 198.3^\circ \text{ V}$$

The current  $\mathbf{I}_x$  is given by


$$\mathbf{I}_x = \frac{\mathbf{V}_1}{-j2.5} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle -90^\circ} = 7.59 \angle 108.4^\circ \text{ A}$$

Transforming this to the time domain,

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

# 10.3 Mesh Analysis (1)

Ex.3 Find  $V_o$  using node analysis.

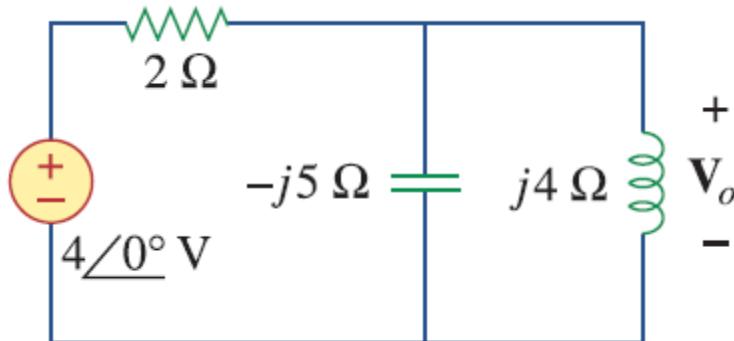

$$\frac{V_0}{j4} + \frac{V_0}{-j5} + \frac{V_0 - 4}{2} = 0$$

$$V_0 \left( \frac{1}{j4} + \frac{1}{-j5} + \frac{1}{2} \right) = 2$$


$$V_0 (-j0.25 + j0.2 + 0.5) = 2$$

$$V_0 = \frac{2}{0.5 - j0.05} = \frac{2}{0.5 - j0.05} \times \frac{0.5 + j0.05}{0.5 + j0.05} = \frac{1 + j0.1}{0.2525} = 3.98\angle 5.71^\circ A$$

Answer:  $V_o = 3.98\angle 5.71^\circ A$

# 10.3 Mesh Analysis (2)

Ex.4 Find  $I_o$  using mesh analysis.

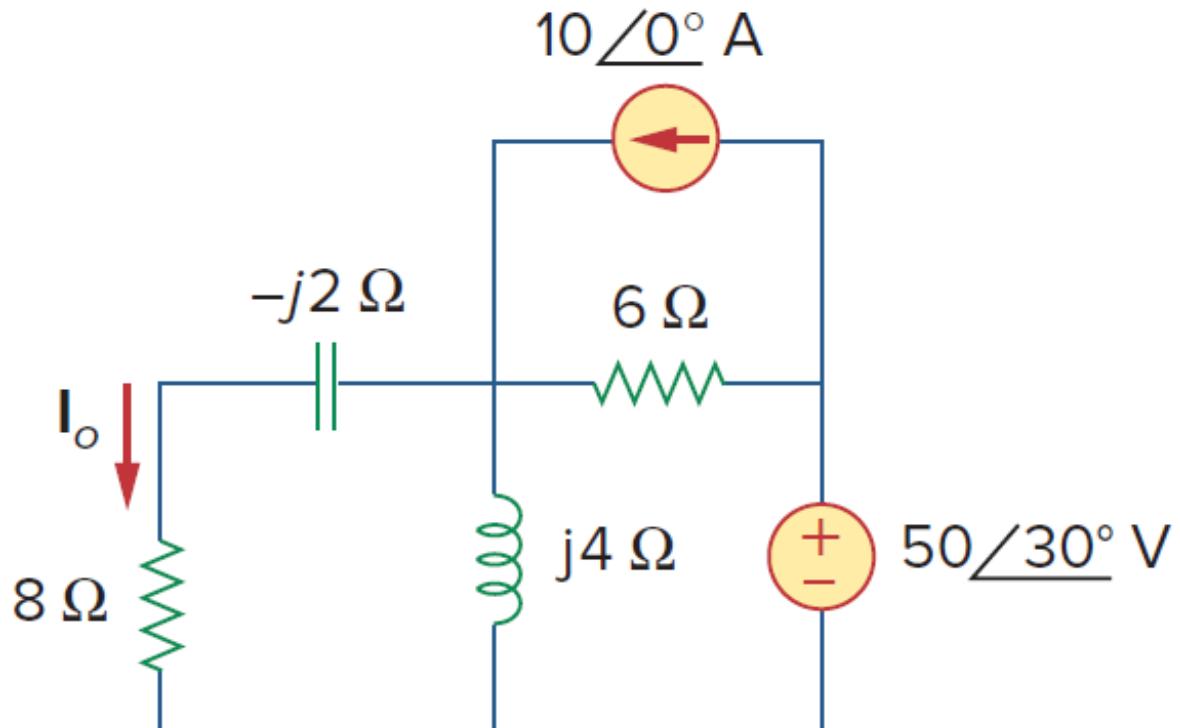

**Answer:**  $5.969\angle65.45^\circ\text{ A}$ .


## 10.4 Superposition Theorem (1)

The theorem becomes important if the circuit has sources operating at different frequencies,

- The separate phasor circuit for each frequency must be solved independently, and
- The total response is the sum of time-domain responses of all the individual phasor circuits.
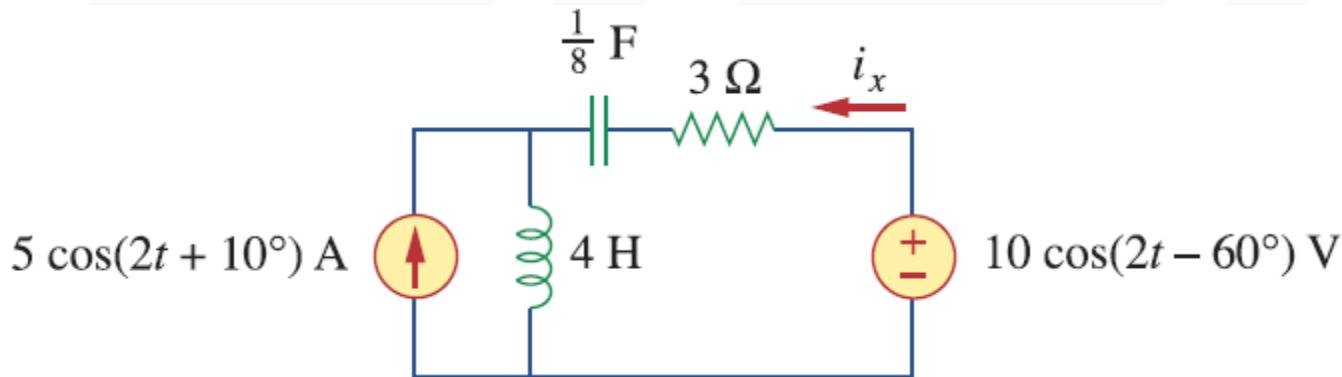
## 10.4 Superposition Theorem (2)

Ex.5 Calculate  $i_x$  in the circuit of figure shown below using the superposition theorem.




$$(i_x)_1 = \frac{10\cos(2t - 60^\circ)}{3 + j8 - j4} = \frac{(10\angle -60^\circ)(5\angle -53.13^\circ)}{25} = 2\angle -113.13^\circ = -0.7856 - j1.839$$

$$(i_x)_2 = -\frac{j8}{3 + j8 - j4} 5\angle 10^\circ = \frac{-32 - j24}{25} 5\angle 10^\circ = 1.6\angle 216.87^\circ \times 5\angle 10^\circ = 8\angle 226.87^\circ = -5.47 - j5.84$$

$$i_x = (i_x)_1 + (i_x)_2 = -6.26 - j7.68 = 9.9\angle -129^\circ$$

Answer :  $i_x = 9.902 \cos(2t - 129.17^\circ) A$


# 10.5 Source Transformation (1)

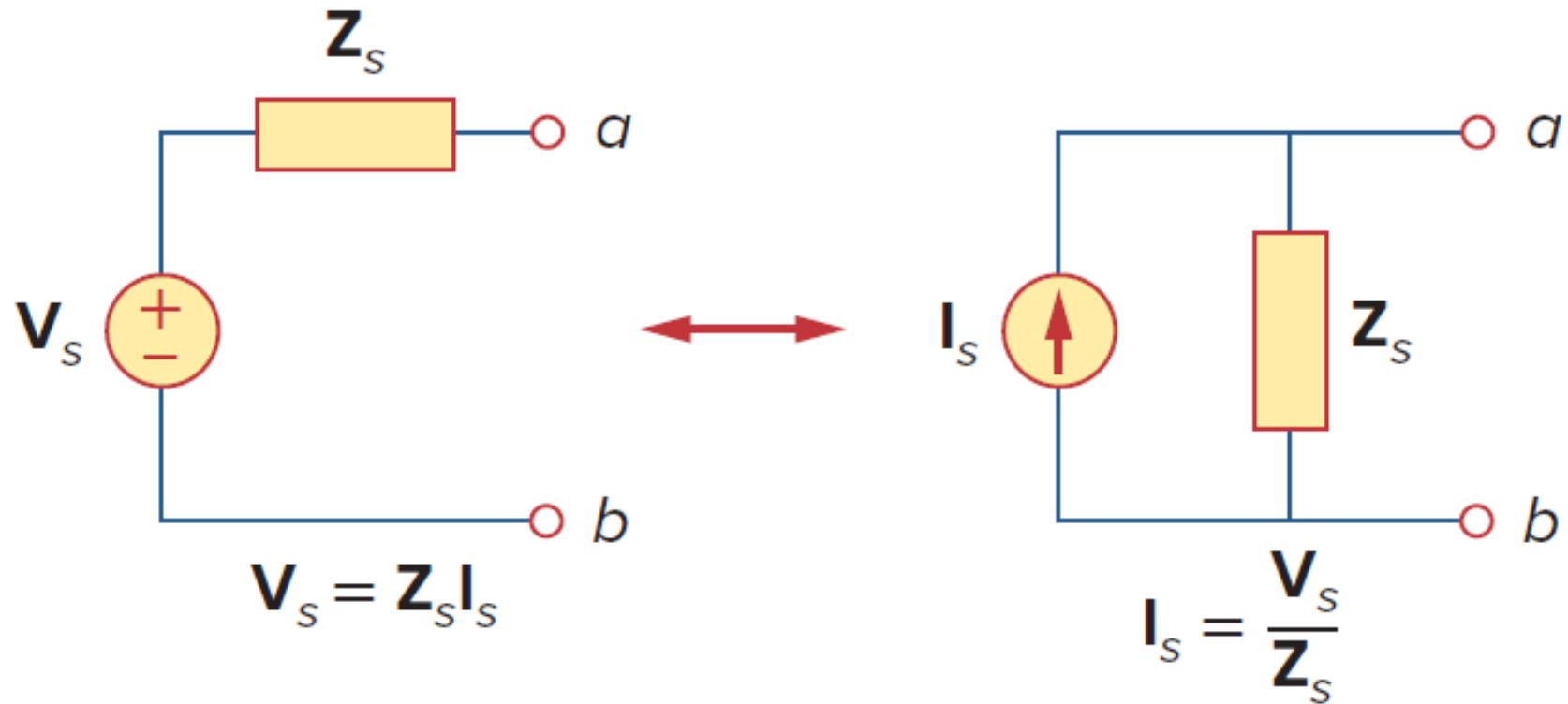

Source transformation.

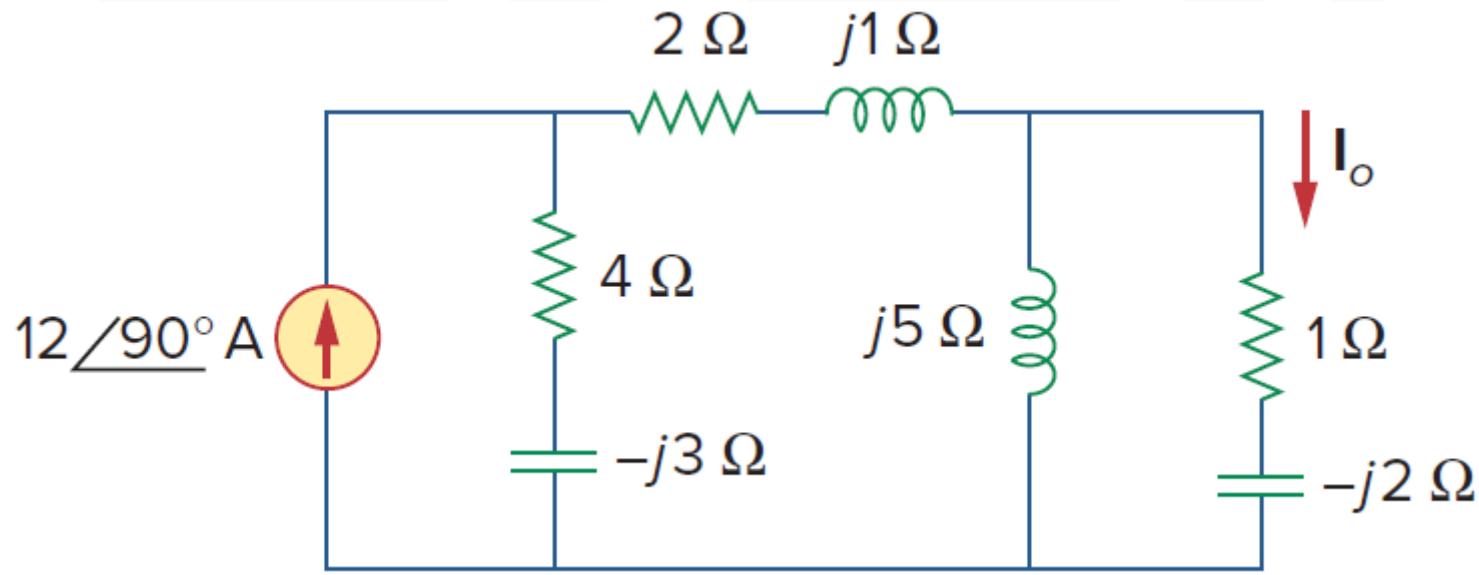
# 10.5 Source Transformation (2)

Ex.6 Find  $I_o$  in the circuit of figure below using the concept of source transformation.




**Answer:**  $9.863\angle 99.46^\circ \text{ A}$ .
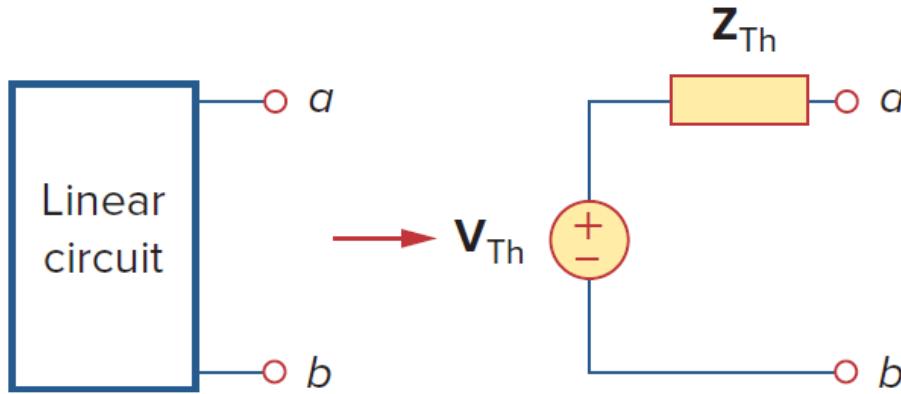
# 10.6 Thevenin and Norton Equivalent Circuits (1)




Thevenin equivalent.

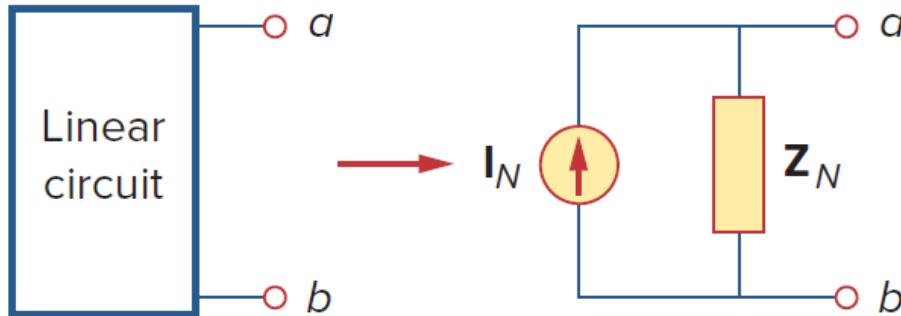

Norton equivalent.
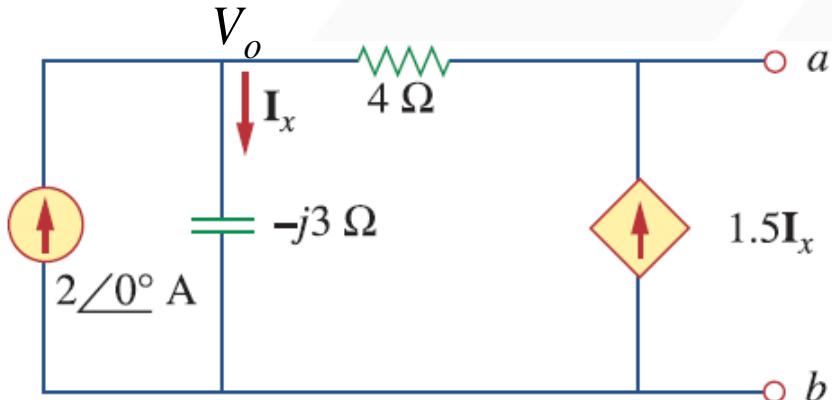
# 10.6 Thevenin and Norton Equivalent Circuits (2)

Ex.7 Find the Thevenin equivalent at terminals a–b of the circuit below.




$$2 + 1.5I_x = I_x \rightarrow I_x = -4$$

$$V_o = I_x(-j3) = j12$$

$$V_{TH} = V_o + 6I_x = -24 + j12$$

$$Z_{TH} = -8 + j6\Omega$$

$$V_{TH} = (-24 + j12)V$$

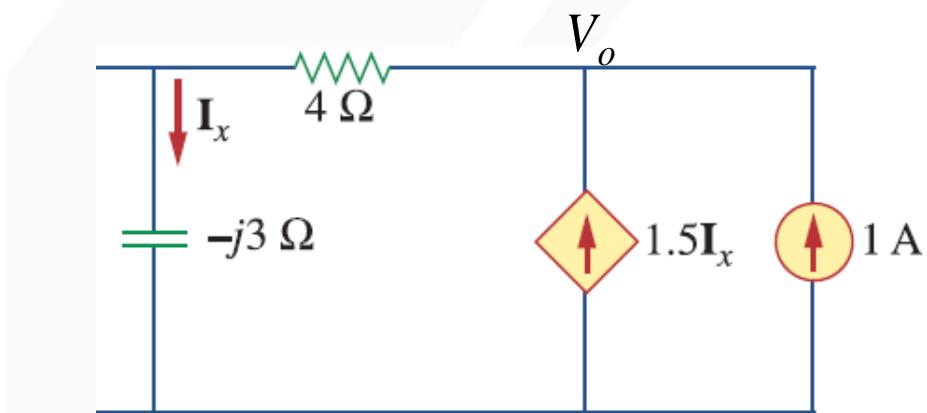

$$1 + 1.5I_x = I_x \rightarrow I_x = -2$$

$$V_o = I_x(4 - j3) = -8 + j6$$

$$Z_{TH} = \frac{V_o}{1} = -8 + j6$$