

# Electrical Engineering 1

## 12026105

### Chapter 12

### Three-Phase Circuit

## Learning Objectives

*By using the information and exercises in this chapter you will be able to:*

1. Understand balanced three-phase voltages.
2. Analyze balanced wye-wye circuits.
3. Understand and analyze balanced wye-delta circuits.
4. Analyze balanced delta-delta circuits.
5. Understand and analyze balanced delta-wye circuits.
6. Explain and analyze power in balanced three-phase circuits.
7. Analyze unbalanced three-phase circuits.

# วัตถุประสงค์การเรียนรู้

โดยใช้ข้อมูลและแบบฝึกหัดในบทนี้ นักเรียนจะสามารถ:

1. เข้าใจสมดุลแรงดันไฟฟ้าสามเฟส
2. วิเคราะห์วงจรสมดุล  $Y - Y$  ได้
3. เข้าใจและวิเคราะห์วงจรสมดุล  $Y - \Delta$  ได้
4. วิเคราะห์วงจรสมดุล  $\Delta - \Delta$  ได้
5. เข้าใจและวิเคราะห์วงจรสมดุล  $\Delta - Y$  ได้
6. อธิบายและวิเคราะห์กำลังในวงจรสมดุลสามเฟสได้
7. วิเคราะห์วงจรสามเฟสที่ไม่สมดุลได้

# Three-Phase Circuits Chapter 12


- What is a Three-Phase Circuit?
- Balance Three-Phase Voltages
- Balance Three-Phase Connection
- Power in a Balanced System
- Unbalanced Three-Phase Systems
- Application – Residential Wiring




Nikola Tesla (1856–1943)
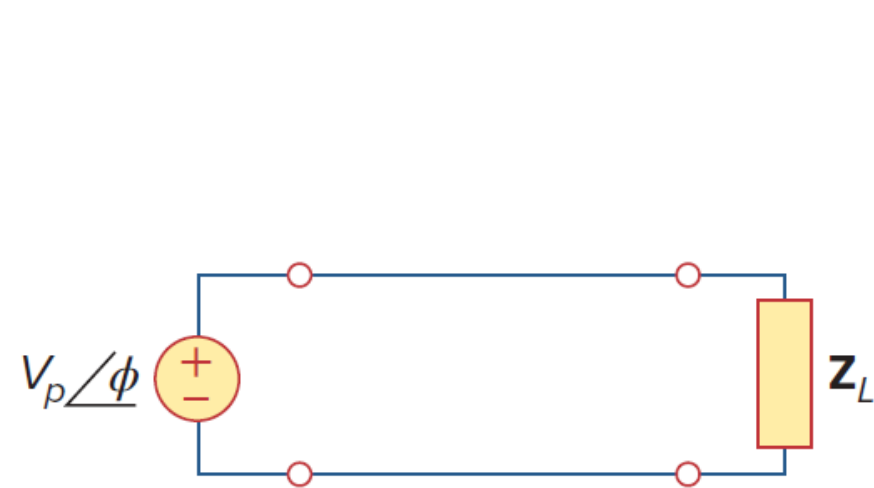
# 12.1 What is a Three-Phase Circuit?

So far, we have dealt with single-phase circuits.



(a)

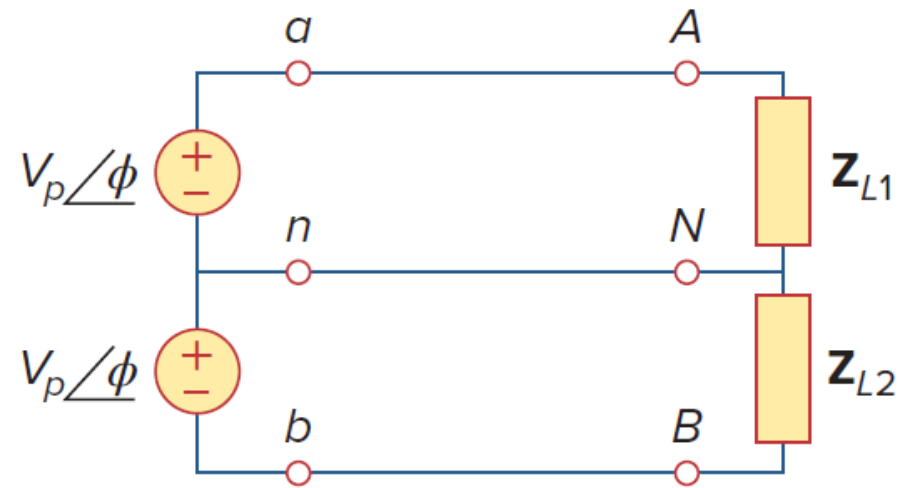


(b)

Single-phase systems: (a) two-wire type, (b) three-wire type.
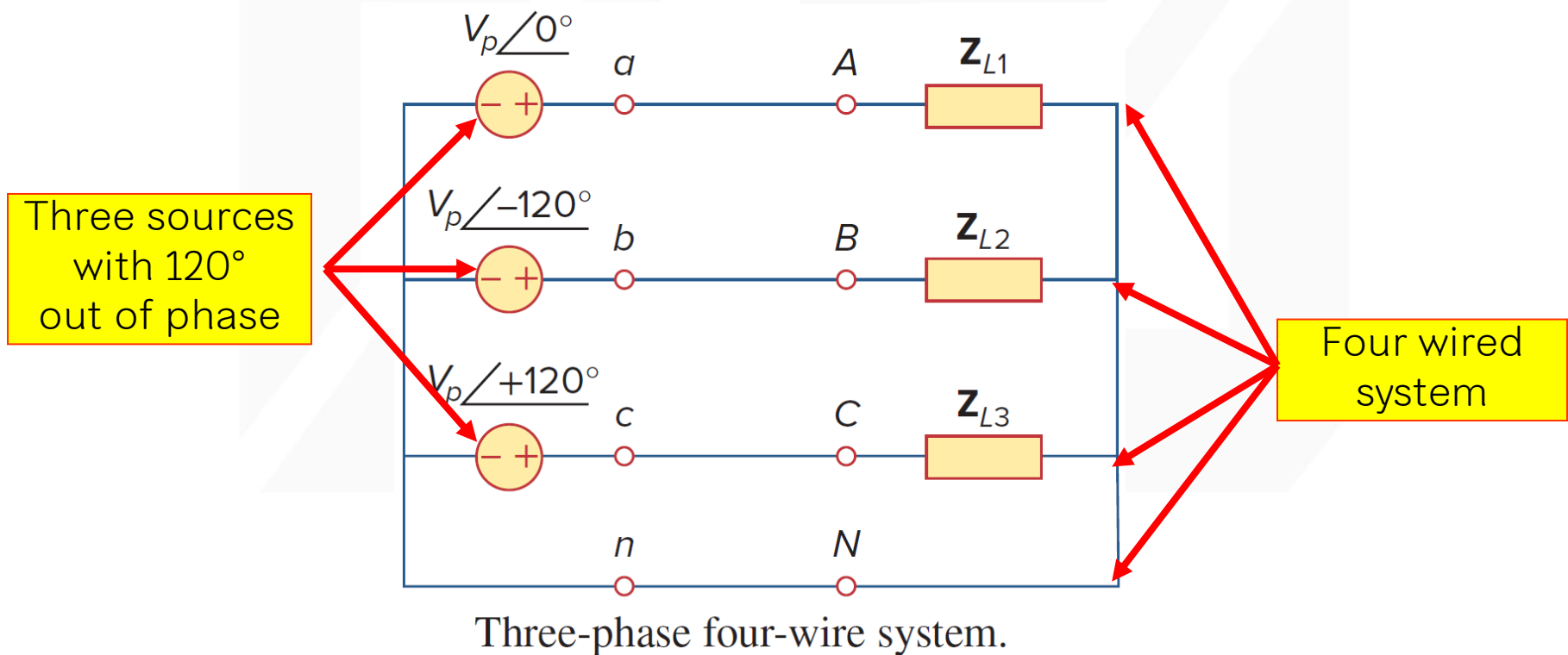
# 12.1 What is a Three-Phase Circuit?

It is a system produced by a generator consisting of three sources having the same amplitude and frequency but out of phase with each other by  $120^\circ$ .




# 12.1 What is a Three-Phase Circuit?

## Advantages:



1. Nearly all electric power is generated and distributed in three-phase, at the operating frequency of 60 Hz (or  $\omega = 377$  rad/s) in the U.S. or 50 Hz (or  $\omega = 314$  rad/s) in some other parts of the world.
2. The instantaneous power in a three-phase system can be constant (not pulsating). This results in uniform power transmission and less vibration of three-phase machines.
3. For the same amount of power, the three-phase system is more economical than the single-phase. In fact, the amount of wire required for a three-phase system is less than that required for an equivalent single-phase system.
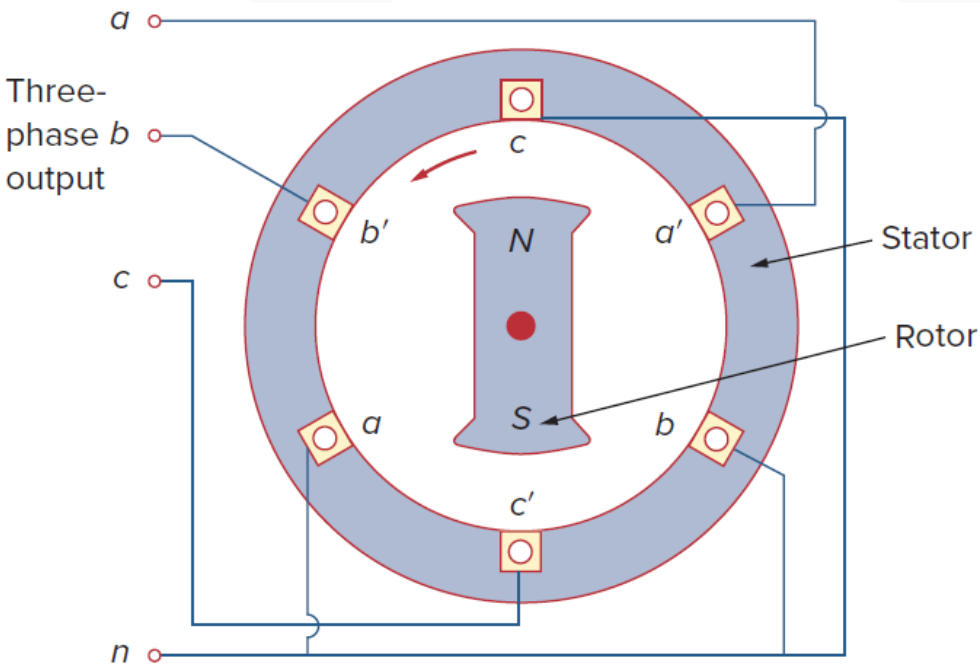
# 12.2 Balance Three-Phase Voltages

A three-phase ac generator (or alternator) consists of a rotating magnet (rotor) surrounded by a stationary winding (stator).



A three-phase generator

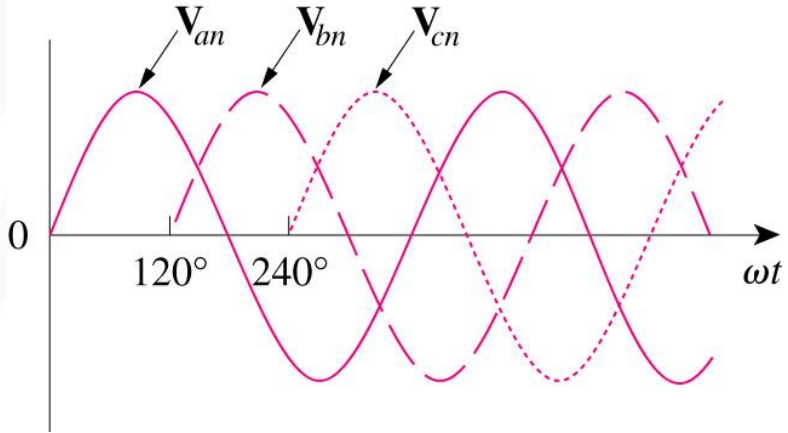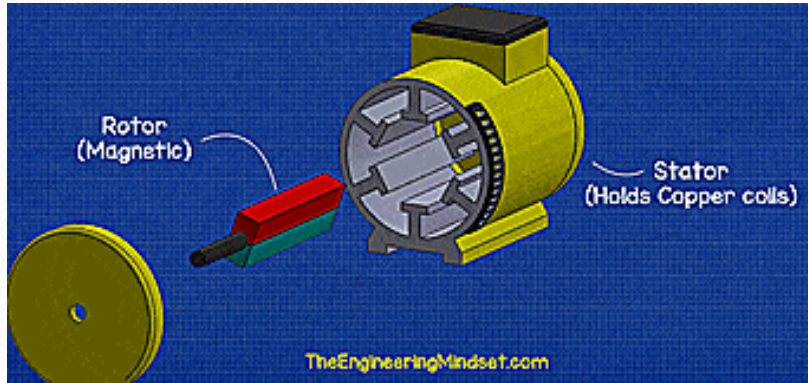


The generated voltages



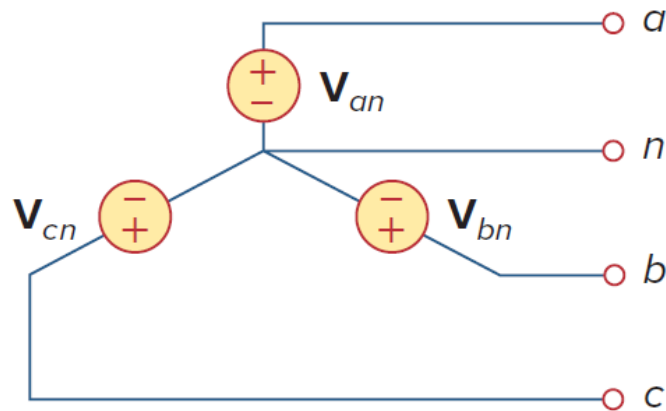
# 12.2 Balance Three-Phase Voltages

- A typical three-phase system consists of three voltage sources connected to loads by three or four wires.
- The voltage sources can be either wye connected as shown in Fig. (a) or delta-connected as in Fig. (b).




(a) Y-connected source

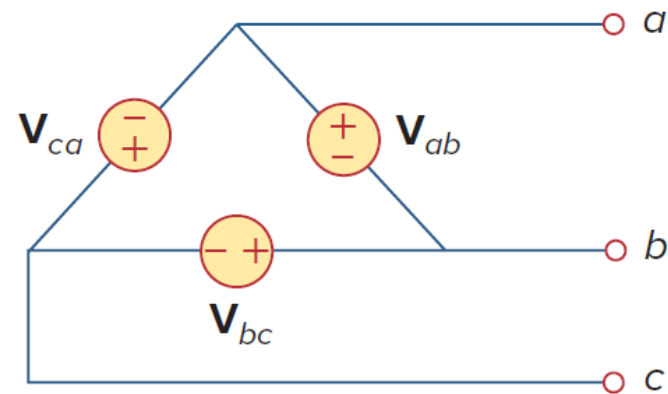

(b)  $\Delta$ -connected source.
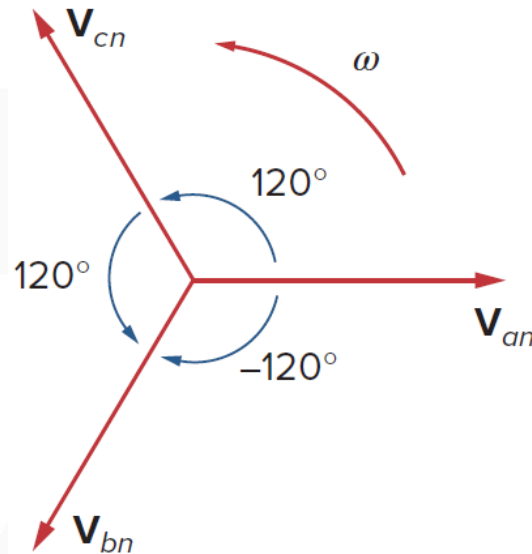
# 12.2 Balance Three-Phase Voltages

Consider the wye-connected voltages. There are two possible combinations.



$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$


$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$

where  $V_p$  is the effective or rms value of the phase voltages.

This is known as the *abc* sequence or positive sequence. In this phase sequence,  $V_{an}$  leads  $V_{bn}$ , which in turn leads  $V_{cn}$ . This sequence is produced when the rotor (Page8) rotates counterclockwise. As the phasors rotate in the counterclockwise direction with frequency  $\omega$ , they pass through the horizontal axis in a sequence *abcabca . . . .* Thus, the sequence is *abc* or *bca* or *cab*.
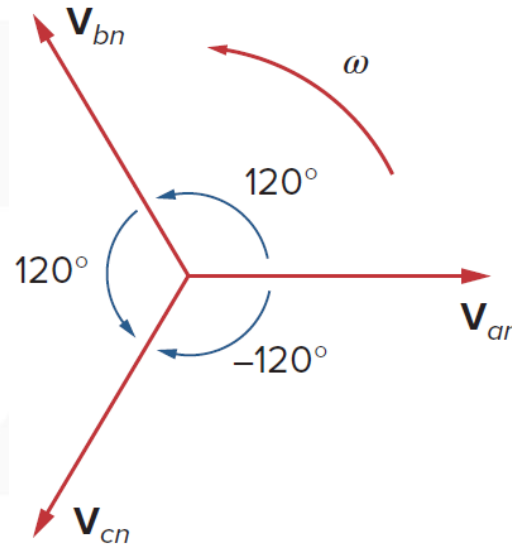
# 12.2 Balance Three-Phase Voltages

Consider the wye-connected voltages. There are two possible combinations.



$$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{cn} &= V_p \angle -120^\circ \\ V_{bn} &= V_p \angle -240^\circ = V_p \angle +120^\circ \end{aligned}$$

This is called the *acb* sequence or negative sequence. In this phase sequence,  $V_{an}$  leads  $V_{cn}$ , which in turn leads  $V_{bn}$ . The *acb* sequence is produced when the rotor (Page8) rotates in the clockwise direction. As the phasors rotate in the counterclockwise direction, they pass the horizontal axis in a sequence *acb* *acba* . . . . This describes the *acb* sequence.

# 12.2 Balance Three-Phase Voltages

- If the voltage sources have the same amplitude and frequency  $\omega$  and are out of phase with each other by  $120^\circ$ , the voltages are said to be balanced. This implies that

$$\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$$



$$|\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}|$$

**Balanced phase voltages** are equal in magnitude and are out of phase with each other by  $120^\circ$ .

$$\begin{aligned} \mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} &= V_p \angle 0^\circ + V_p \angle -120^\circ + V_p \angle +120^\circ \\ &= V_p(1.0 - 0.5 - j0.866 - 0.5 + j0.866) \\ &= 0 \end{aligned}$$
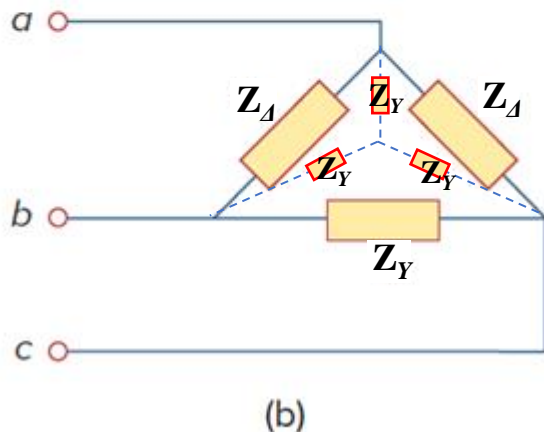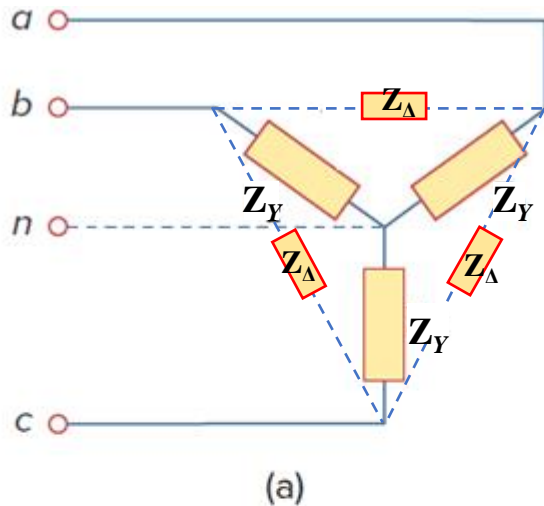
# 12.2 Balance Three-Phase Voltages

- A wye- or delta-connected load is said to be unbalanced if the phase impedances are not equal in magnitude or phase.



For a *balanced* wye-connected load,

$$\mathbf{Z}_1 = \mathbf{Z}_2 = \mathbf{Z}_3 = \mathbf{Z}_Y$$

where  $\mathbf{Z}_Y$  is the load impedance per phase.

For a *balanced* delta-connected load,


$$\mathbf{Z}_a = \mathbf{Z}_b = \mathbf{Z}_c = \mathbf{Z}_\Delta$$

where  $\mathbf{Z}_\Delta$  is the load impedance per phase.

$$\mathbf{Z}_\Delta = 3\mathbf{Z}_Y \quad \text{or} \quad \mathbf{Z}_Y = \frac{1}{3}\mathbf{Z}_\Delta$$

Two possible three-phase load configurations:  
 (a) a Y-connected load, (b) a  $\Delta$ -connected load.
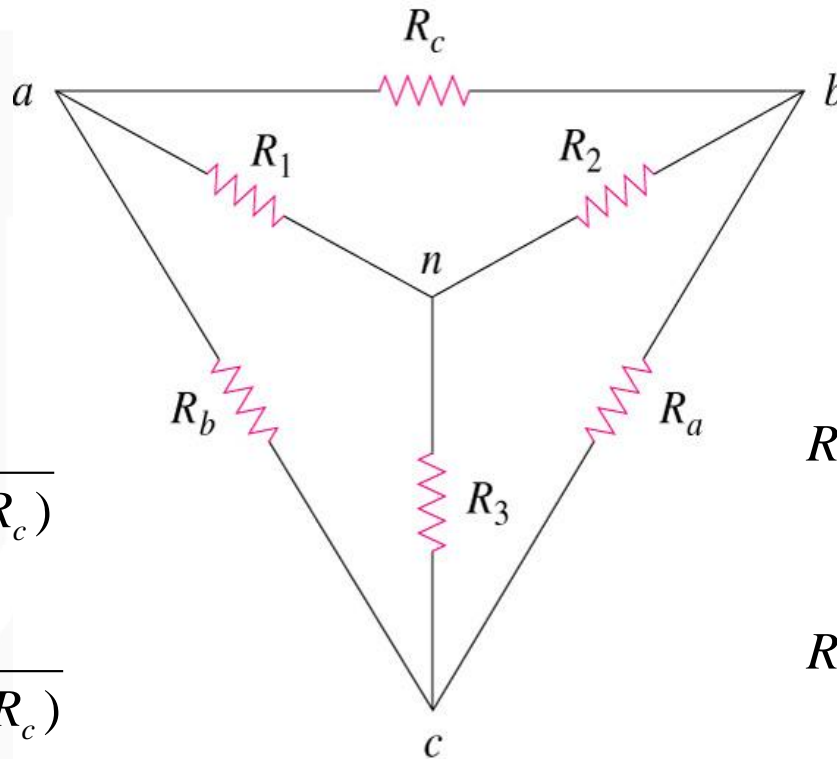
# 12.2 Balance Three-Phase Voltages ( Wye-Delta Transformations)



Delta  $\rightarrow$  Star

$$R_1 = \frac{R_b R_c}{(R_a + R_b + R_c)}$$

$$R_2 = \frac{R_c R_a}{(R_a + R_b + R_c)}$$

$$R_3 = \frac{R_a R_b}{(R_a + R_b + R_c)}$$

Star  $\rightarrow$  Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

## 12.2 Balance Three-Phase Voltages

- **Balanced phase voltages** are equal in magnitude and are out of phase with each other by  $120^\circ$ .
- The **phase sequence** is the time order in which the voltages pass through their respective maximum values.
- A **balanced load** is one in which the phase impedances are equal in magnitude and in phase

# 12.2 Balance Three-Phase Voltages

Ex.1 Determine the phase sequence of the set of voltages.

$$v_{an} = 200 \cos(\omega t + 10^\circ)$$

$$v_{bn} = 200 \cos(\omega t - 230^\circ)$$

$$v_{cn} = 200 \cos(\omega t - 110^\circ)$$

Solution:

The voltages can be expressed in phasor form as

$$V_{an} = 200 \angle 10^\circ \text{ V}$$

$$V_{bn} = 200 \angle -230^\circ \text{ V}$$

$$V_{cn} = 200 \angle -110^\circ \text{ V}$$

We notice that  $V_{an}$  leads  $V_{cn}$  by  $120^\circ$  and  $V_{cn}$  in turn leads  $V_{bn}$  by  $120^\circ$ . Hence, we have an *acb* sequence.



# 12.2 Balance Three-Phase Voltages

Ex.1.2 Given that  $V_{bn} = 110 \angle 30^\circ \text{ V}$ , find  $V_{an}$  and  $V_{cn}$ , assuming a positive (*abc*) sequence.



**Answer:**  $110 \angle 150^\circ \text{ V}$ ,  $110 \angle -90^\circ \text{ V}$ .

# 12.3 Balance Three-Phase Connection

Four possible connections

1. **Y-Y** connection (Y-connected source with a Y-connected load)
2. **Y- $\Delta$**  connection (Y-connected source with a  $\Delta$ -connected load)
3.  **$\Delta$ - $\Delta$**  connection
4.  **$\Delta$ -Y** connection

# 12.3 Balance Three-Phase Connection

A **balanced Y-Y** system is a three-phase system with a balanced y-connected source and a balanced y-connected load.

$V_L = \text{line-to-line voltages } (V_{ab}, V_{bc}, V_{ca})$

$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} = V_{an} - V_{bn} \\ &= V_p \angle 0^\circ - V_p \angle -120^\circ \\ &= V_p \left( 1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \angle 30^\circ \end{aligned}$$


Similarly, we can obtain

$$\begin{aligned} V_{bc} &= V_{bn} - V_{cn} = \sqrt{3} V_p \angle -90^\circ \\ V_{ca} &= V_{cn} - V_{an} = \sqrt{3} V_p \angle -210^\circ \end{aligned}$$


$V_L = \sqrt{3} V_p$ , where

$$V_p = |V_{an}| = |V_{bn}| = |V_{cn}|$$

$$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}|$$

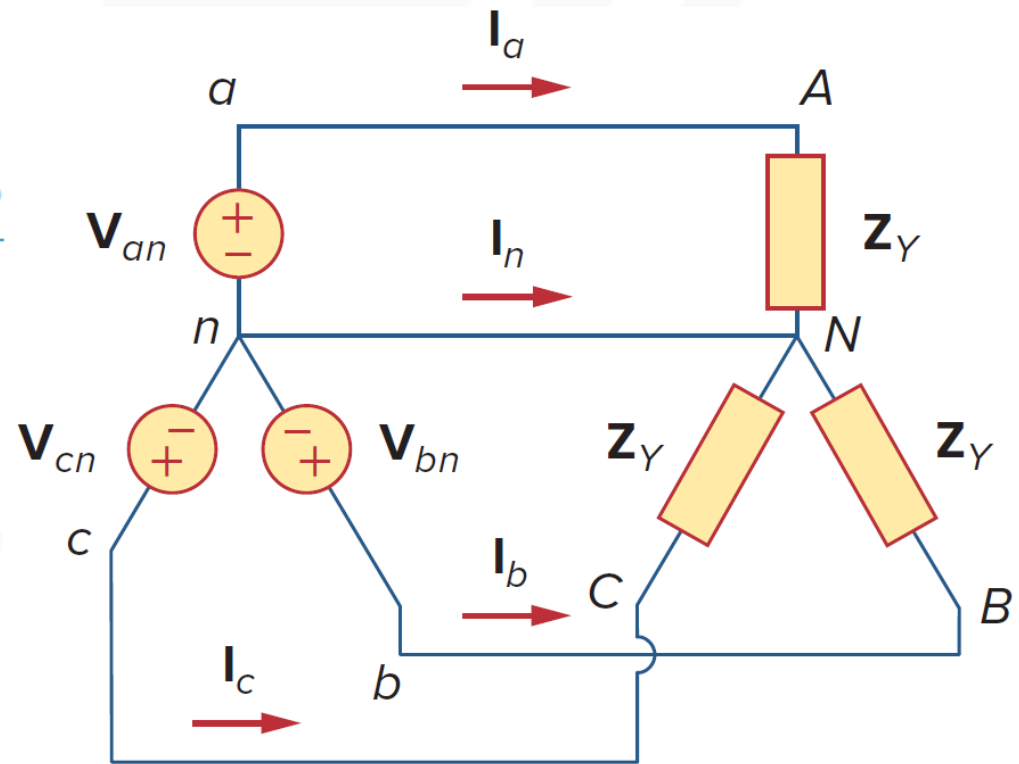

# 12.3 Balance Three-Phase Connection

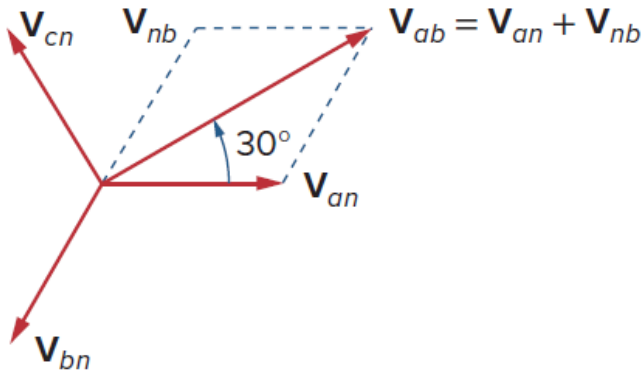

(a)

Applying KVL to each phase in Fig. 12.10, we obtain the line currents as

$$I_a = \frac{V_{an}}{Z_Y}, \quad I_b = \frac{V_{bn}}{Z_Y} = \frac{V_{an} \angle -120^\circ}{Z_Y} = I_a \angle -120^\circ$$

$$I_c = \frac{V_{cn}}{Z_Y} = \frac{V_{an} \angle -240^\circ}{Z_Y} = I_a \angle -240^\circ$$

We can readily infer that the line currents add up to zero,


$$I_a + I_b + I_c = 0$$

so that

$$I_n = -(I_a + I_b + I_c) = 0$$


or

$$V_{nN} = Z_n I_n = 0$$

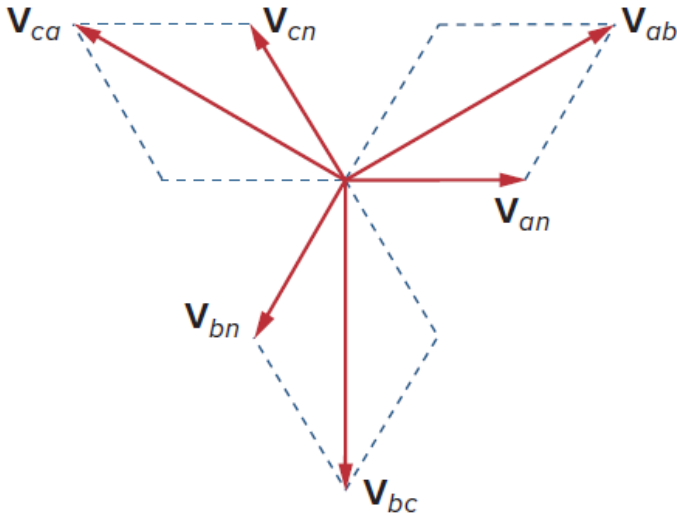


(b)

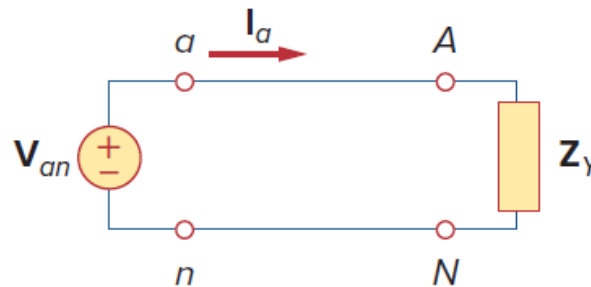Phasor diagrams illustrating the relationship between line voltages & phase voltages.




A single-phase equivalent circuit.

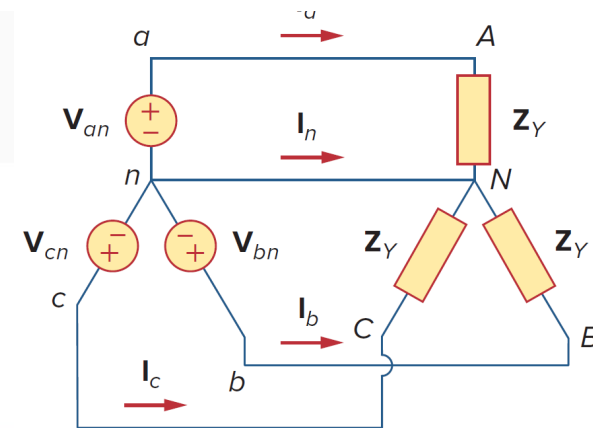

# 12.3 Balance Three-Phase Connection
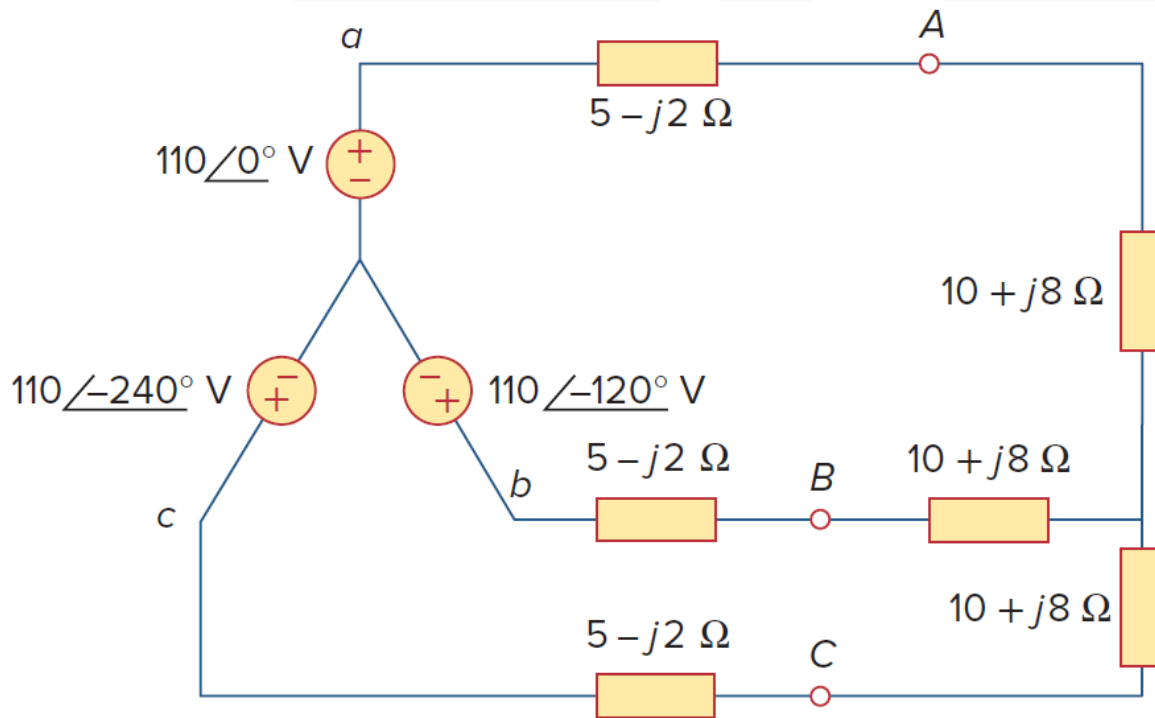
## Ex.2

Calculate the line currents in the three-wire Y-Y system shown below:



Ans

$$I_a = 6.81\angle -21.8^\circ \text{ A}$$

$$I_b = 6.81\angle -141.8^\circ \text{ A}$$

$$I_c = 6.81\angle 98.2^\circ \text{ A}$$

\*Refer to in-class illustration, textbook

# 12.3 Balance Three-Phase Connection

## Solution

We obtain  $\mathbf{I}_a$  from the single-phase analysis as

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y}$$

where  $\mathbf{Z}_Y = (5 - j2) + (10 + j8) = 15 + j6 = 16.155 \angle 21.8^\circ$ . Hence,

$$\mathbf{I}_a = \frac{110 \angle 0^\circ}{16.155 \angle 21.8^\circ} = 6.81 \angle -21.8^\circ \text{ A}$$

In as much as the source voltages in Fig. 12.13 are in positive sequence, the line currents are also in positive sequence:

$$\begin{aligned} \mathbf{I}_b &= \mathbf{I}_a \angle -120^\circ = 6.81 \angle -141.8^\circ \text{ A} \\ \mathbf{I}_c &= \mathbf{I}_a \angle -240^\circ = 6.81 \angle -261.8^\circ \text{ A} = 6.81 \angle 98.2^\circ \text{ A} \end{aligned}$$

\*Refer to in-class illustration, textbook

# 12.3 Balance Three-Phase Connection

A **balanced Y- $\Delta$**  system is a three-phase system with a balanced y-connected source and a balanced  $\Delta$ -connected load.

Assuming the positive sequence, the phase voltages are

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle +120^\circ$$

The line voltages are

$$V_{ab} = \sqrt{3} V_p \angle 30^\circ = V_{AB}$$


$$V_{bc} = \sqrt{3} V_p \angle -90^\circ = V_{BC}$$

$$V_{ca} = \sqrt{3} V_p \angle 150^\circ = V_{CA}$$

$I_L = \sqrt{3} I_p$ , where

$$I_L = |I_a| = |I_b| = |I_c|$$

$$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

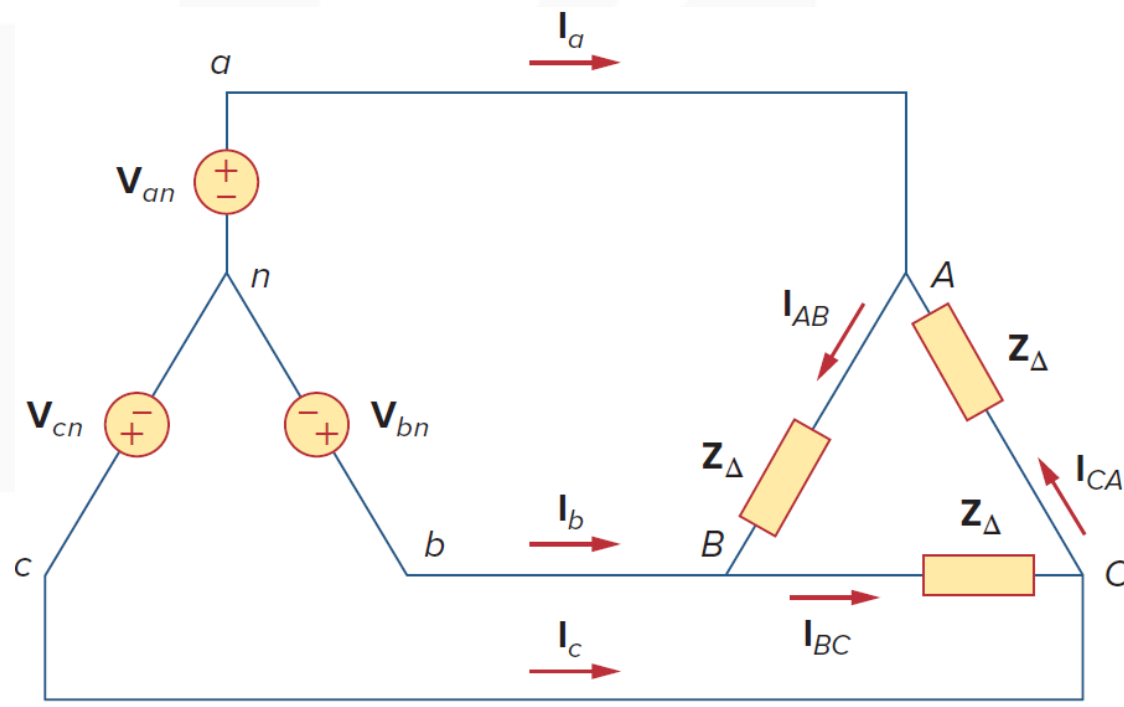


# 12.3 Balance Three-Phase Connection

From these voltages, we can obtain the phase currents as

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{\Delta}}, \quad \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_{\Delta}}, \quad \mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_{\Delta}}$$

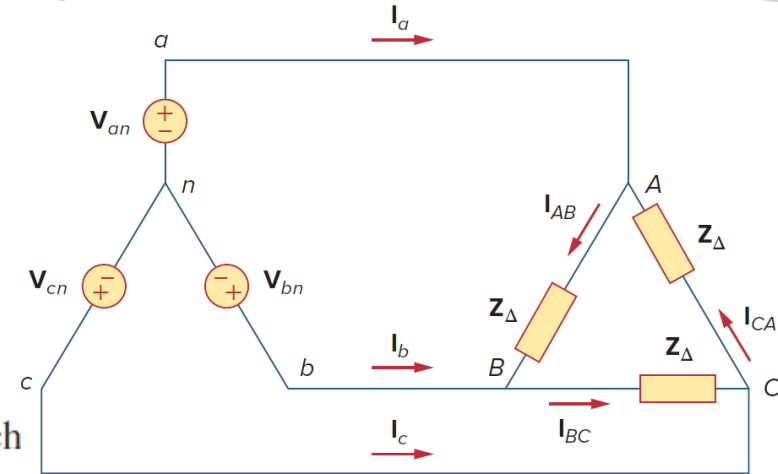These currents have the same magnitude but are out of phase with each other by  $120^\circ$  by applying KVL around loop  $aABbna$  gives



$$-\mathbf{V}_{an} + \mathbf{Z}_{\Delta}\mathbf{I}_{AB} + \mathbf{V}_{bn} = 0 \quad \text{or} \quad \mathbf{I}_{AB} = \frac{\mathbf{V}_{an} - \mathbf{V}_{bn}}{\mathbf{Z}_{\Delta}} = \frac{\mathbf{V}_{ab}}{\mathbf{Z}_{\Delta}} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{\Delta}}$$

The line currents are obtained from the phase currents by applying KCL at nodes  $A$ ,  $B$ , and  $C$ . Thus,

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA}, \quad \mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB}, \quad \mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$

Since  $\mathbf{I}_{CA} = \mathbf{I}_{AB} \angle -240^\circ$ ,


$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA} = \mathbf{I}_{AB}(1 - 1 \angle -240^\circ) = \mathbf{I}_{AB}(1 + 0.5 - j0.866) = \mathbf{I}_{AB}\sqrt{3} \angle -30^\circ$$

showing that the magnitude  $I_L$  of the line current is  $\sqrt{3}$  times the magnitude  $I_p$  of the phase current

$$I_L = \sqrt{3}I_p$$




# 12.3 Balance Three-Phase Connection

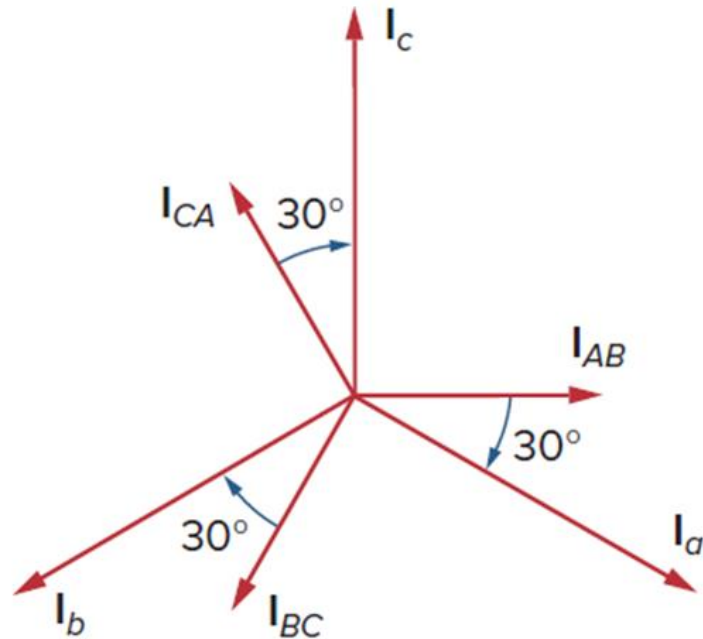

Phasor diagram illustrating the relationship between phase and line currents.

An alternative way of analyzing the Y- $\Delta$  circuit is to transform the  $\Delta$ -connected load to an equivalent Y-connected load. Using the  $\Delta$ -Y transformation formula in Eq. (12.8),

$$Z_Y = \frac{Z_\Delta}{3}$$

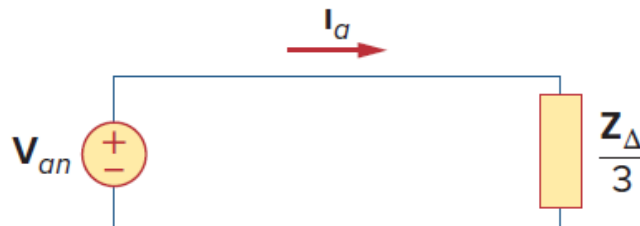

A single-phase equivalent circuit of a balanced Y- $\Delta$  circuit.

# 12.3 Balance Three-Phase Connection

## Example 3

A balanced abc-sequence Y-connected source with ( $V_{an} = 100\angle 10^\circ$ ) is connected to a  $\Delta$ -connected load  $(8+j4) \Omega$  per phase. Calculate the phase and line currents.

## Solution


Using single-phase analysis,

$$I_a = \frac{V_{an}}{Z_{\Delta} / 3} = \frac{100\angle 10^\circ}{2.981\angle 26.57^\circ} = 33.54\angle -16.57^\circ \text{ A}$$

Other line currents are obtained using the abc phase sequence
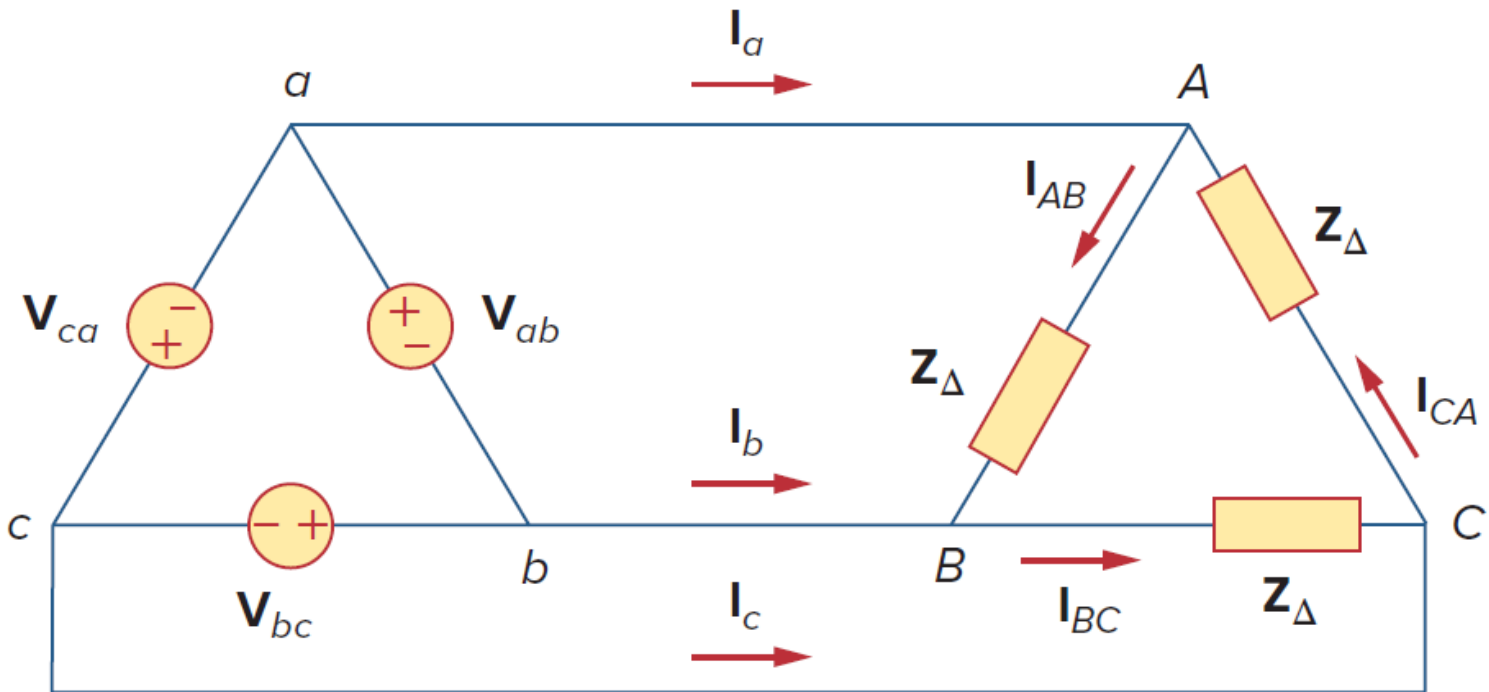
# 12.3 Balance Three-Phase Connection

A **balanced  $\Delta$ - $\Delta$**  system is a three-phase system with a balanced  $\Delta$ -connected source and a balanced  $\Delta$ -connected load.



# 12.3 Balance Three-Phase Connection

Assuming a positive sequence, the phase voltages for a delta-connected source are

$$\mathbf{V}_{ab} = V_p \angle 0^\circ$$

$$\mathbf{V}_{bc} = V_p \angle -120^\circ$$

$$\mathbf{V}_{ca} = V_p \angle +120^\circ$$

The line voltages are the same as the phase voltages. From Fig. 12.17, assuming there is no line impedances, the phase voltages of the delta-connected source are equal to the voltages across the impedances; that is,

$$\mathbf{V}_{ab} = \mathbf{V}_{AB}, \quad \mathbf{V}_{bc} = \mathbf{V}_{BC}, \quad \mathbf{V}_{ca} = \mathbf{V}_{CA}$$

Hence, the phase currents are

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{Z_\Delta} = \frac{\mathbf{V}_{ab}}{Z_\Delta}, \quad \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{Z_\Delta} = \frac{\mathbf{V}_{bc}}{Z_\Delta}$$

$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{Z_\Delta} = \frac{\mathbf{V}_{ca}}{Z_\Delta}$$

# 12.3 Balance Three-Phase Connection

Because the load is delta-connected just as in the previous section, some of the formulas derived there apply here. The line currents are obtained from the phase currents by applying KCL at nodes  $A$ ,  $B$ , and  $C$ , as we did in the previous section:

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA}, \quad \mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB}, \quad \mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$

Also, as shown in the last section, each line current lags the corresponding phase current by  $30^\circ$ ; the magnitude  $I_L$  of the line current is  $\sqrt{3}$  times the magnitude  $I_p$  of the phase current,

$$I_L = \sqrt{3}I_p$$

An alternative way of analyzing the  $\Delta$ - $\Delta$  circuit is to convert both the source and the load to their  $Y$  equivalents. We already know that  $\mathbf{Z}_Y = \mathbf{Z}_\Delta/3$ . To convert a  $\Delta$ -connected source to a  $Y$ -connected source, see the next section.

# 12.3 Balance Three-Phase Connection

## Example 4

A balanced  $\Delta$ -connected load having an impedance  $20-j15 \Omega$  is connected to a  $\Delta$ -connected positive-sequence generator having ( $V_{ab} = 330 \angle 0^\circ \text{ V}$ ). Calculate the phase currents of the load and the line currents.

Ans:

The phase currents


$$I_{AB} = 13.2 \angle 36.87^\circ \text{ A}; I_{BC} = 13.2 \angle -81.13^\circ \text{ A}; I_{CA} = 13.2 \angle 156.87^\circ \text{ A}$$

The line currents

$$I_a = 22.86 \angle 6.87^\circ \text{ A}; I_b = 22.86 \angle -113.13^\circ \text{ A}; I_c = 22.86 \angle 126.87^\circ \text{ A}$$
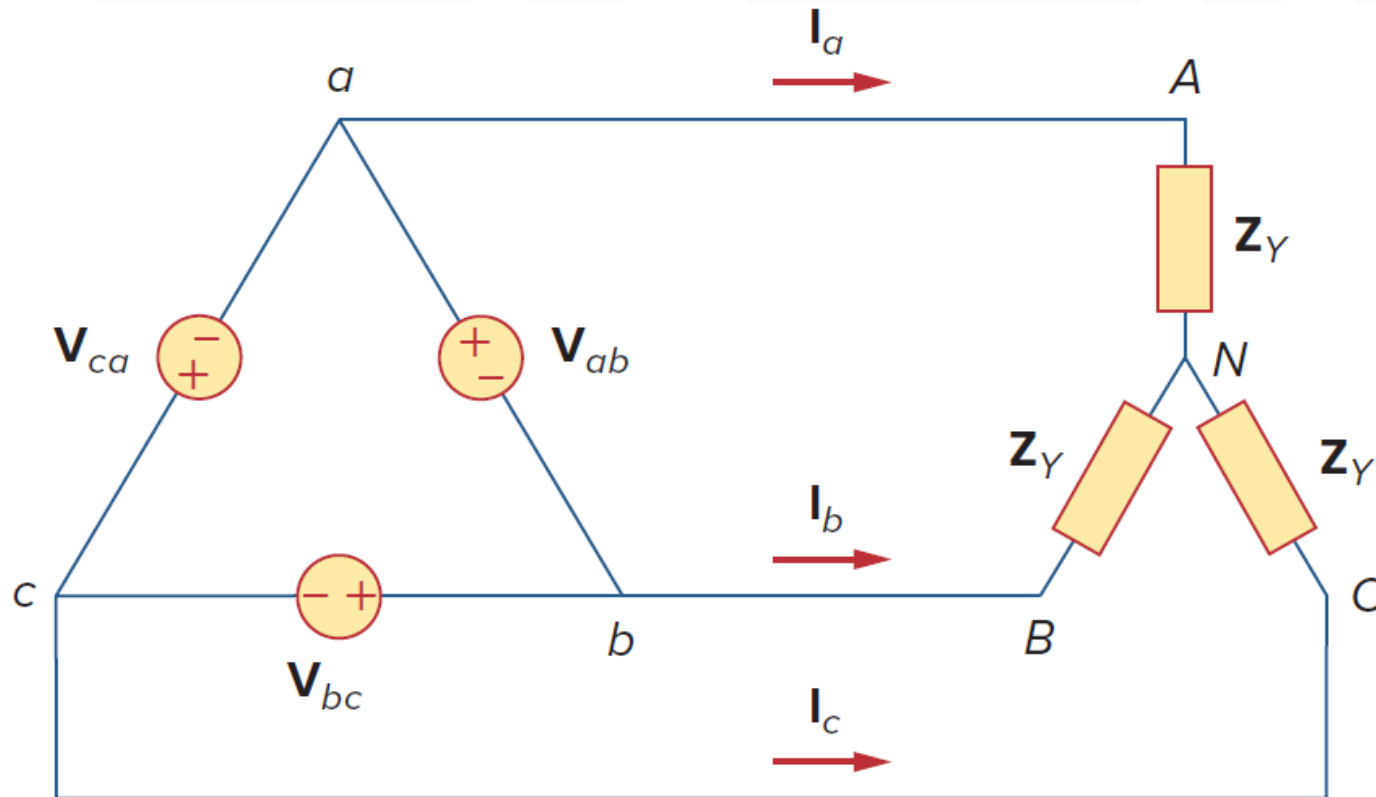
# 12.3 Balance Three-Phase Connection

A **balanced  $\Delta$ -Y** system is a three-phase system with a balanced y-connected source and a balanced y-connected load.



# 12.3 Balance Three-Phase Connection

Consider the  $\Delta$ -Y circuit in Fig. 12.18. Again, assuming the  $abc$  sequence, the phase voltages of a delta-connected source are

$$\begin{aligned} \mathbf{V}_{ab} &= V_p \underline{/0^\circ}, & \mathbf{V}_{bc} &= V_p \underline{/ -120^\circ} \\ \mathbf{V}_{ca} &= V_p \underline{/ +120^\circ} \end{aligned}$$

These are also the line voltages as well as the phase voltages.

We can obtain the line currents in many ways. One way is to apply KVL to loop  $aANBba$  in Fig. 12.18, writing

$$-\mathbf{V}_{ab} + \mathbf{Z}_Y \mathbf{I}_a - \mathbf{Z}_Y \mathbf{I}_b = 0$$

or

$$\mathbf{Z}_Y (\mathbf{I}_a - \mathbf{I}_b) = \mathbf{V}_{ab} = V_p \underline{/0^\circ}$$

Thus,

$$\mathbf{I}_a - \mathbf{I}_b = \frac{V_p \underline{/0^\circ}}{\mathbf{Z}_Y}$$




# 12.3 Balance Three-Phase Connection

But  $I_b$  lags  $I_a$  by  $120^\circ$ , since we assumed the  $abc$  sequence; that is,  
 $I_b = I_a / -120^\circ$ . Hence,


$$\begin{aligned}
 I_a - I_b &= I_a(1 - 1 / -120^\circ) \\
 &= I_a \left( 1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = I_a \sqrt{3} / 30^\circ
 \end{aligned}$$

Substituting Eq. (12.36) into Eq. (12.35) gives
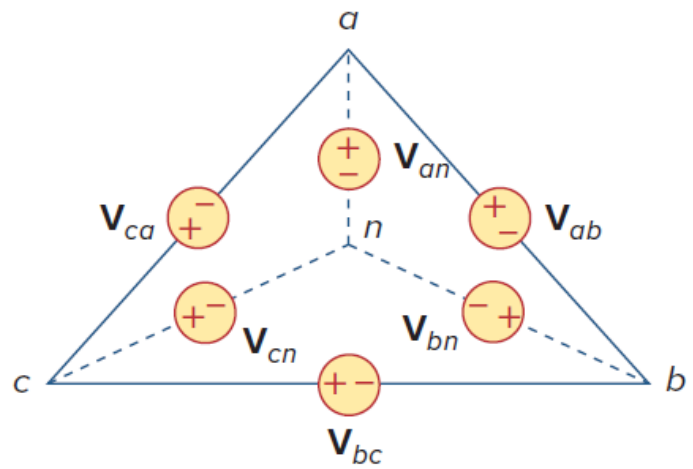
$$I_a = \frac{V_p / \sqrt{3} / -30^\circ}{Z_Y}$$



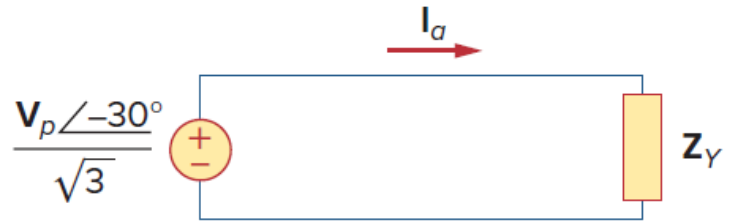Transforming a  $\Delta$ -connected source to an equivalent Y-connected source.



The single-phase equivalent circuit.

# 12.3 Balance Three-Phase Connection

Ex.5 A balanced Y-connected load with a phase impedance  $40+j25 \Omega$  is supplied by a balanced, positive-sequence  $\Delta$ -connected source with a line voltage of 210V. Calculate the phase currents. Use  $V_{ab}$  as reference.

Answer

The phase currents


$$I_{AN} = 2.57 \angle -62^\circ \text{ A};$$

$$I_{BN} = 2.57 \angle -178^\circ \text{ A};$$

$$I_{CN} = 2.57 \angle 58^\circ \text{ A};$$
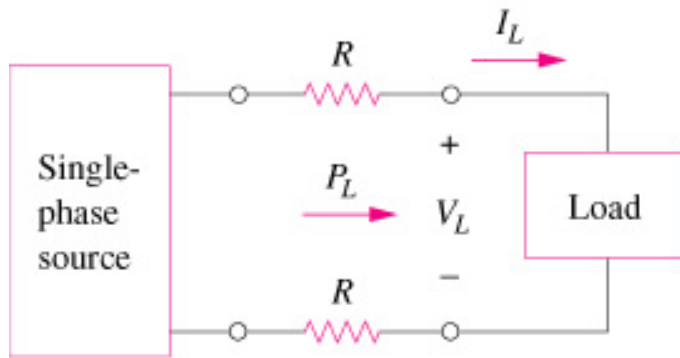
# 12.4 Power in a Balanced System


Comparing the power loss in (a) a single-phase system, and (b) a three-phase system



Transmission lines

(a)
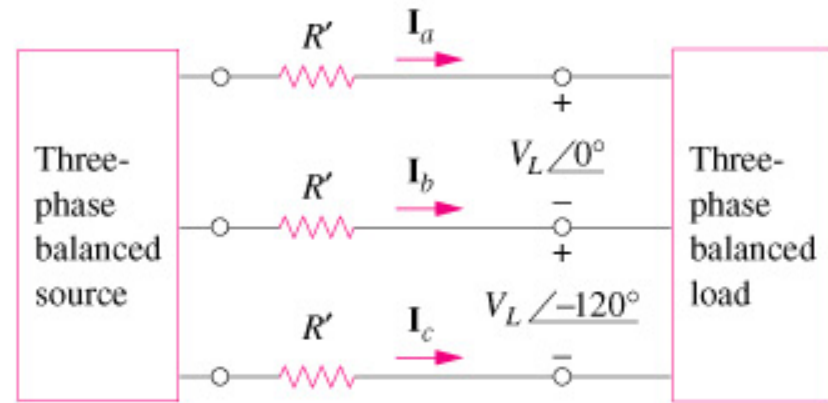
$$P'_{loss} = 2R \frac{P_L^2}{V_L^2}, \text{ single - phase}$$



Transmission lines


(b)

$$P'_{loss} = R' \frac{P_L^2}{V_L^2}, \text{ three - phase}$$

If same power loss is tolerated in both system, three-phase system use only 75% of materials of a single-phase system
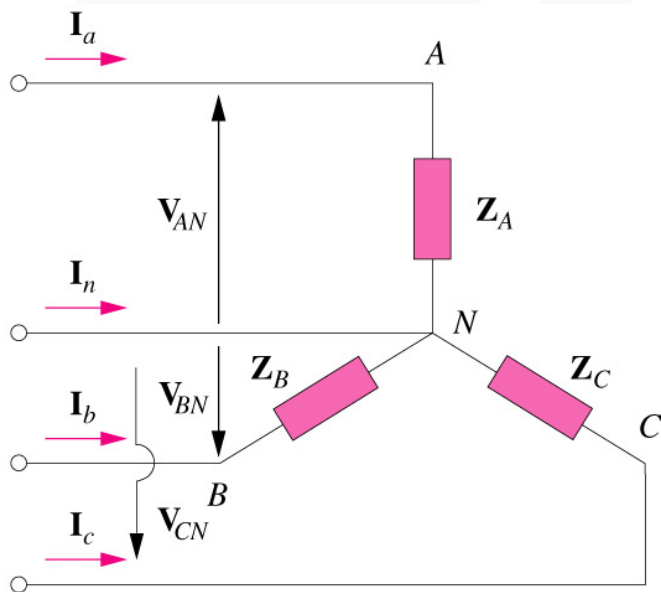
# 12.5 Unbalanced Three-Phase Systems

An unbalanced system is due to unbalanced voltage sources or an unbalanced load.




$$I_a = \frac{V_{AN}}{Z_A}, I_b = \frac{V_{BN}}{Z_B}, I_c = \frac{V_{CN}}{Z_C},$$

$$I_n = -(I_a + I_b + I_c)$$

- To calculate power in an unbalanced three-phase system requires that we find the power in each phase.
- The total power is not simply three times the power in one phase but the sum of the powers in the three phases.
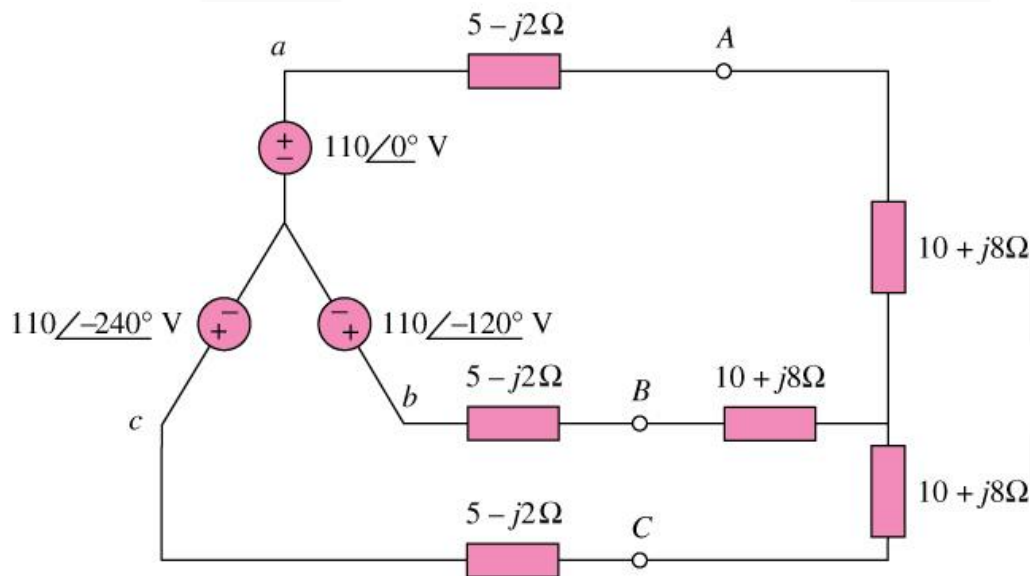
# 12.5 Unbalanced Three-Phase Systems

Ex.6 Determine the total average power, reactive power, and complex power at the source and at the load



Ans

At the source:

$$S_s = -(2087 + j834.6) \text{ VA}$$

$$P_a = -2087 \text{ W}$$

$$P_r = -834.6 \text{ VAR}$$

At the load:


$$S_L = (1392 + j1113) \text{ VA}$$

$$P_a = 1392 \text{ W}$$

$$P_r = 1113 \text{ VAR}$$


\*Refer to in-class illustration, textbook

# 12.6 Application Residential Wiring

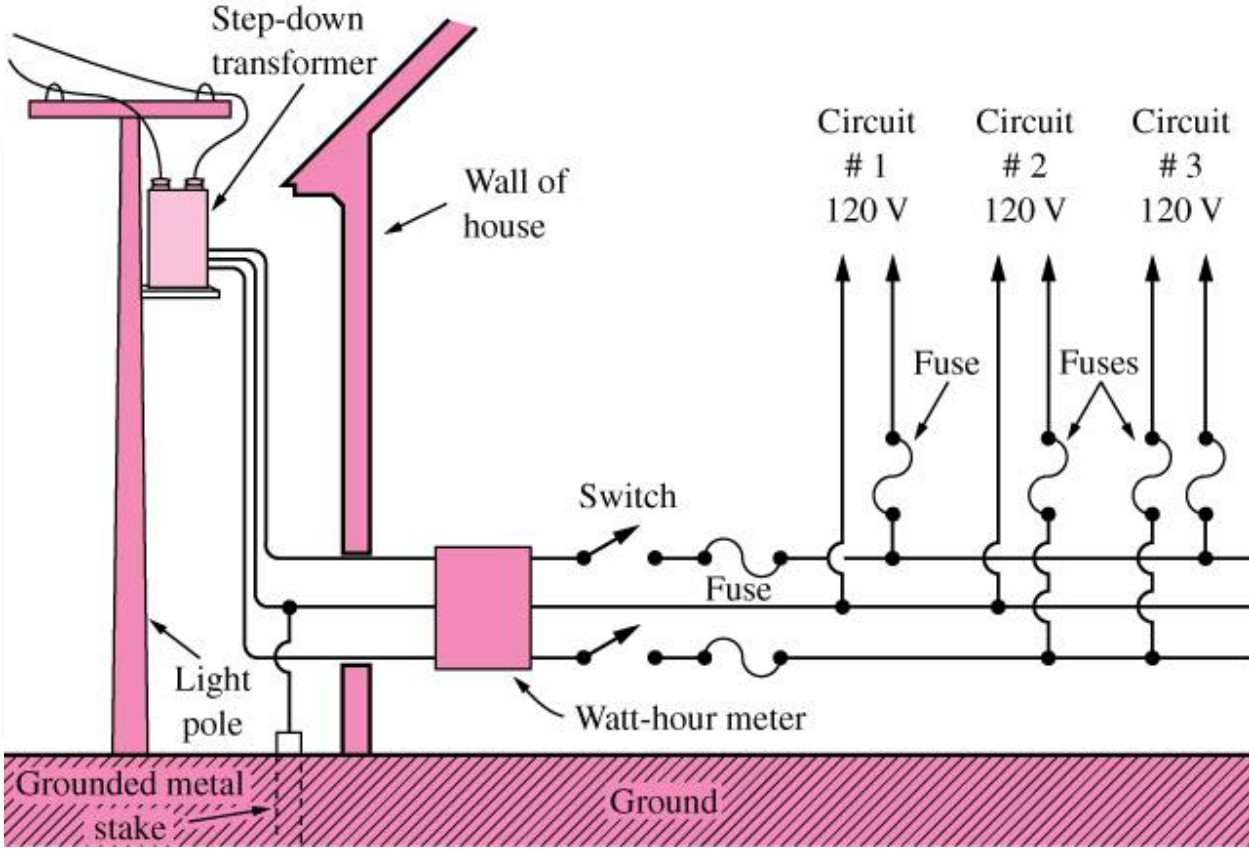


A 120/240 household power system

# 12.6 Application Residential Wiring

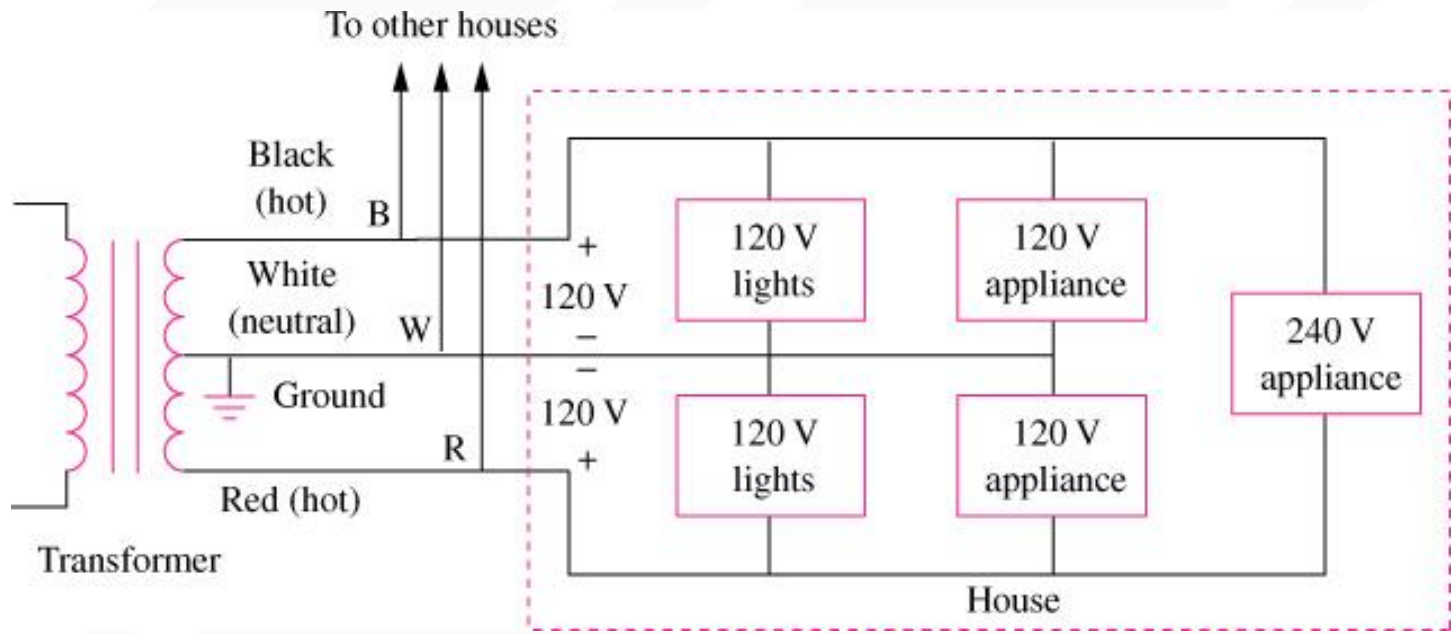

Single-phase three-wire residential wiring

# 12.6 Application Residential Wiring

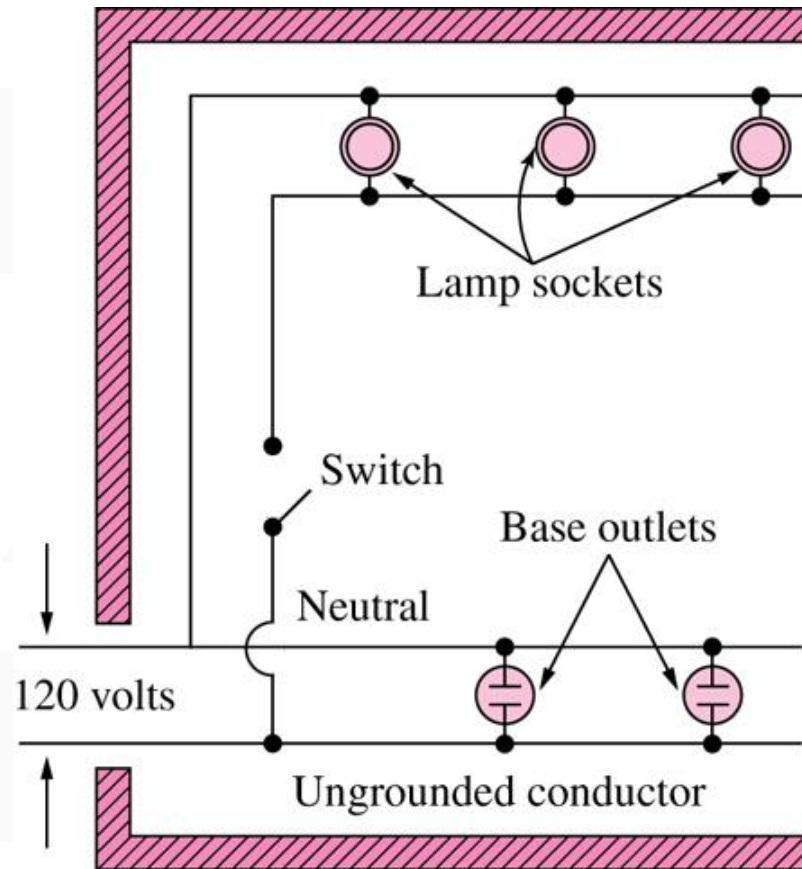

A typical wiring diagram of a room