

#### Learning Objectives

By using the information and exercises in this chapter you will be able to:

- 1. Better understand sinusoids.
- 2. Understand phasors.
- 3. Understand the phasor relationships for circuit elements.
- 4. Know and understand the concepts of impedance and admittance.
- 5. Understand Kirchhoff's laws in the frequency domain.
- 6. Comprehend the concept of phase-shift.
- 7. Understand the concept of AC bridges.

# Sinusoids and Phasor Chapter 9

- 9.1 Motivation
- 9.2 Sinusoids' features
- 9.3 Phasors
- 9.4 Phasor relationships for circuit elements
- 9.5 Impedance and admittance
- 9.6 Kirchhoff's laws in the frequency domain
- 9.7 Impedance combinations

# 9.1 Motivation



How can we apply what we have learned before to determine i(t) and v(t)?

### 9.2 Sinusoids (1)

A sinusoid is a signal that has the form of the sine or cosine function.



## 9.2 Sinusoids (2)

A periodic function is one that satisfies v(t) = v(t + nT), for all t and for all integers n.



Only 2 sinusoidal values with the <u>same freq</u>. can be compared.
 If phase difference is zero, they are in phase; otherwise, they are out of phase.

# 9.2 Sinusoids (3)

Example 1 Given a sinusoid,  $5\sin(4\pi t - 60^\circ)$ , calculate its amplitude  $(V_m)$ , phase  $(\phi)$ , angular frequency  $(\omega)$ , period (T), and frequency (f).



#### 9.2 Sinusoids (4)

Example 2 Find the phase angle between  $i_1 = -4\sin(377t+25^\circ)$ and  $i_2 = 5\cos(377t - 40^\circ)$ , does  $i_1$  lead or lag  $i_2$ ?

Complementary Angle:

- $\sin\theta = \cos(90^\circ \theta)$
- $\cos\theta = \sin(90^\circ \theta)$
- $\tan \theta = \cot(90^\circ \theta)$
- $\cot \theta = \tan(90^\circ \theta)$
- $\sec\theta = \csc(90^\circ \theta)$

• 
$$\csc\theta = \sec(90^\circ - \theta)$$

 $egin{aligned} \sin( heta+\pi) &= -\sin heta\ \cos( heta+\pi) &= -\cos heta\ \sin( heta+rac{\pi}{2}) &= +\cos heta\ \cos( heta+rac{\pi}{2}) &= -\sin heta \end{aligned}$ 

 $i_1 = -4\sin(377t+25^\circ) = 4\cos(377t+25^\circ+90^\circ) = 4\cos(377t+115^\circ)$  $i_2 = 5\cos(377t-40^\circ)$  so that  $i_1$  lead  $i_2$  by 155°



# 9.2 Sinusoids (5)

Reflected in $ heta=0$	Reflected in $ heta=\pi/2$ (co-function identities)	Reflected in $ heta=\pi$
$\sin(- heta) = -\sin heta \ \cos(- heta) = +\cos heta$	$\sin(rac{\pi}{2}- heta)=+\cos heta\ \cos(rac{\pi}{2}- heta)=+\sin heta$	$\sin(\pi- heta)=+\sin heta\ \cos(\pi- heta)=-\cos heta$
Shift by π/2	Shift by π Period for tan and cot	Shift by 2π Period for sin, cos
$\sin( heta+rac{\pi}{2})=+\cos heta\ \cos( heta+rac{\pi}{2})=-\sin heta$	$\sin( heta+\pi)=-\sin heta\ \cos( heta+\pi)=-\cos heta$	$\sin( heta+2\pi)=+\sin heta\ \cos( heta+2\pi)=+\cos heta\ _{90^\circ}$
	$\begin{array}{c} 1\\ 1\\ \theta\\ \end{array} \\ x \end{array} $ 180	$ \begin{array}{c ccccc} 2 \\ SIN \\ 3 \\ 270^{\circ} \end{array} $

> จงหาว่าในแต่ละคู่ของสัญญาณ sinusoids ตัวใดน้ำและน้ำกื่องศา

(a) 
$$v(t) = 10 \cos(4t - 60^\circ)$$
 and  
 $i(t) = 4 \sin(4t + 50^\circ)$   
(b)  $v_1(t) = 4 \cos(377t + 10^\circ)$  and  
 $v_2(t) = -20 \cos 377t$ 

Solution:

- a.  $i(t) = 4\sin(4t 40^\circ + 90^\circ) = 4\cos(4t 40^\circ)$  ดังนั้น i(t) un v(t) อยู่ 20°
- b.  $v_2(t) = 20 \cos(377t + 180^\circ)$  ดังนั้น  $v_2(t)$  นำ  $v_1(t)$  อยู่  $170^\circ$

> จงหาว่าในแต่ละคู่ของสัญญาณ sinusoids ตัวใดน้ำและน้ำกื่องศา

(c)  $x(t) = 13 \cos 2t + 5 \sin 2t$  and  $y(t) = 15 \cos(2t - 11.8^{\circ})$ 

Solution:

 $x(t) = 13 \cos(2t) + 5 \cos(2t - 90^\circ) = 13 \angle 0^\circ + 5 \angle -90^\circ$ =  $13 - 5j = 13.93 \angle -21.04^\circ = 13.93 \cos(2t - 21.04^\circ)$  ดังนั้น y(t)นำ x(t) อยู่ 9.24°

# 9.3 Phasor (1)

A phasor is a complex number that represents the amplitude and phase of a sinusoid.

> It can be represented in one of the following three forms:



# 9.3 Phasor (2)

Example 3 Evaluate the following complex numbers:



Solution:

a. -15.5 + j13.67

b. 8.293 + j2.2

# 9.3 Phasor (3)

Mathematic operation of complex number:

- 1. Addition
- 2. Subtraction
- 3. Multiplication
- 4. Division
- 5. Reciprocal
- 6. Square root
- 7. Complex conjugate
- 8. Euler's identity

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$
$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

$$z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$$

$$\frac{1}{z} = \frac{1}{r} \angle -\phi$$

$$z^* = x - jy = r \angle -\phi = re^{-j\phi}$$

 $e^{\pm j\phi} = \cos\phi \pm j\sin\phi$ 

#### 9.3 Phasor (4)

Transform a sinusoid to and from the time domain to the phasor domain:

$$v(t) = V_m \cos(\omega t + \phi) \longleftrightarrow V = V_m \angle \phi$$
  
(time domain) (phasor domain)

Amplitude and phase difference are two principal concerns in the study of voltage and current sinusoids.
 Phasor will be defined from the cosine function in all our proceeding study.

#### 9.3 Phasor (5)

Example 4 Transform the following sinusoids to phasors:

$$i(t)=5\cos(50t-40^{\circ}) \text{ A}$$
  
 $v(t)=-4\sin(30t+50^{\circ}) \text{ V}$ 

Answer : 
$$I=5 \angle -40^{\circ}$$
 A

เนื่องจาก –sin(θ)=cos(θ+90°) ดังนั้น v(t)=4cos(30t+50° + 90°) ⇒ V = 4∠140° V

### 9.3 Phasor (6)

Example 5 Transform the sinusoids corresponding to phasors:

<sup>a.</sup> 
$$V = -10 \angle 30^{\circ}$$
 V  
b.  $I = j(5 - j12)$  A

#### Solution:

a).  $v(t)=10\cos(\omega t+210^{\circ})$  V

Since 
$$I = 12 + j5 = \sqrt{12^2 + 5^2} \angle \tan^{-1}(\frac{5}{12}) = 13 \angle 22.62^\circ$$
  
b).  $i(t) = 13 \cos(\omega t + 22.62^\circ) A$ 

# 9.3 Phasor (7)

The differences between  $v(t) \, \text{and} \, \mathbf{V}$ 

- $\succ$  v(t) is instantaneous or <u>time-domain</u> representation v is the frequency or <u>phasor-domain</u> representation.
- $\succ$  v(t) is time dependent, V is not.
- v(t) is always real with no complex term, v is generally complex.

<u>Note</u>: Phasor analysis applies only when frequency is constant; when it is applied to <u>two or more</u> sinusoid signals only if they have the <u>same frequency</u>.

# 9.3 Phasor (8)

Relationship between differential, integral operation

in phasor listed as follow:

Time domain

Phasor domain

$$v(t) = V_m \cos(\omega t + \varphi) \longleftrightarrow \mathbf{V} = V_m \angle \varphi$$

$$\frac{v(t)}{dt} \longrightarrow j\omega \mathbf{V}$$

 $\leftarrow$   $\frac{1}{j\omega}$ 

 $v(t) = V_m \cos(\omega t + \varphi) = Re(V_m e^{j\varphi} e^{j\omega t}) = Re(\mathbf{V} e^{j\omega t}) \leftrightarrow \mathbf{V} = V_m \angle \varphi = V_m e^{j\varphi}$ 

v(t)dt

# 9.3 Phasor (9)

Example 6 Use phasor approach, determine the current i(t) in a circuit described by the integrodifferential equation.

$$4i+8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t+75^{\circ})$$
  
$$4I+8 \frac{I}{j\omega} - 3j\omega I = 50 \angle 75^{\circ}$$
  
$$4I - j4I - j6I = 50 \angle 75^{\circ}$$

 $I(4 - 10j) = (10.77 \angle - 68.2^{\circ})I = 50 \angle 75^{\circ}$  $I = 4.642 \angle 143.2^{\circ} \iff i(t) = 4.642 \cos(2t + 143.2^{\circ})$ Answer:  $i(t) = 4.642 \cos(2t + 143.2^{\circ})$  A

# 9.3 Phasor (10)

We can derive the differential equations for the following circuit to solve for  $v_o(t)$  in phasor domain  $V_o$ .



#### 9.3 Phasor (11)

#### The answer is YES!

- Instead of first deriving the differential equation and then transforming it into phasor to solve for V<sub>0</sub>.
  - we can transform all the RLC components into phasor first, then apply the KCL laws and other theorems to set up a phasor equation involving V<sub>o</sub> directly.

#### 9.4 Phasor Relationships for Circuit Elements (



#### 9.4 Phasor Relationships for Circuit Elements (2)

Voltage-Current relationship				
Element	Time domain	Frequency domain		
R	v=iR	V=IR		
L	$v = L \frac{di}{dt}$	V=j@LI		
С	$i = C \frac{dv}{dt}$	I=j@CV		

#### 9.4 Phasor Relationships for Circuit Elements

Example 7 If  $v(t) = 6\cos(100t - 30^\circ)$  is applied to a 50  $\mu$ F capacitor, calculate the current, i(t), through the capacitor.

 $I = j\omega CV$ 

 $I = j \times 100 \times 50 \times 10^{-6} \times 6 \angle -30^{\circ} = 0.03 \angle 90^{\circ} \times \angle -30^{\circ} = 0.03 \angle 60^{\circ}$ 

 $i(t)=0.03\cos(100t+60^\circ)$  A

<u>Answer</u>:  $i(t) = 30\cos(100t + 60^{\circ}) \text{ mA}$ 

• The impedance Z of a circuit is the ratio of the phasor voltage V to the phasor current I, measured in  $\Omega$ .

$$Z = \frac{V}{I} = R + jX$$

where R = Re(Z) is the resistance and X = Im(Z) is the reactance. Positive X is for L and negative X is for C.

• The admittance Y is the reciprocal of impedance (Z),

measured in siemens (S).  $Y = \frac{1}{7}$ 

Impedances of elements			
Element	Impedance	Admittance	
R	Z=R	$Y=\frac{1}{R}$	
L	Z=j@L	$Y = \frac{1}{j \omega L}$	
С	$Z = \frac{1}{j\omega C}$	Y=j@C	



After we know how to convert RLC components from time to phasor domain, we can <u>transform</u> a time domain circuit into a phasor/frequency domain circuit.

Hence, we can apply the <u>KCL laws and other theorems</u> to directly set up phasor equations involving our target variable(s) for solving.

<u>Example 8</u> Refer to Figure below, determine i(t) and v(t).



 $v_s = 20\sin(10t+30^\circ) = 20\cos(10t+30^\circ-90^\circ) \implies V_s = 20\angle -60^\circ$ 

 $I = \frac{V_{\rm s}}{Z} = \frac{20\angle -60^{\circ}}{4+j2} \times \frac{4-j2}{4-j2} = -2\sqrt{5}\angle -86.57^{\circ} \Rightarrow i = 4.472\cos(10t-86.57^{\circ}) = 4.472\sin(10t+3.43^{\circ})$ 

 $V = IZ_L = -2\sqrt{5} \angle -86.57^\circ \times j2 = -4\sqrt{5} \angle 3.43^\circ \Rightarrow v = 8.944\cos(10t + 3.43^\circ) = 8.944\sin(10t + 93.43^\circ)$ 

30

<u>Answers</u>:  $i(t)=4.472\sin(10t+3.43^\circ)$  A,  $v(t)=8.944\sin(10t+93.43^\circ)$  V

<u>Example 9</u> Find  $i_o$  in the circuit using superposition.



 $i_0 = i_{01} + i_{02} = 10 + 1.98\cos(4t-71.6^\circ)$  A

9.6 Kirchhoff's Laws in the Frequency Domain (1)

- Both <u>KVL and KCL</u> are hold in the phasor(frequency) domain.
- Moreover, the variables to be handled are <u>phasors</u>, which are <u>complex numbers</u>.

# 9.7 Impedance Combinations (1

• The following principles used for DC circuit analysis all apply to AC circuit.

- For example:
  - a. voltage division
  - b. current division
  - c. circuit reduction
  - d. impedance equivalence
  - e. Y- $\Delta$  transformation



A delta or wye circuit is said to be balanced if it has equal impedances in all three branches.

# 9.7 Impedance Combinations (3

Example 9 Determine the input impedance of the circuit in figure below at  $\omega = 10$  rad/s.



$$((50+20j)||-25j)+20-50j=32.38-j73.76$$

<u>Answer</u>:  $Z_{in} = (32.38 - j73.76) \Omega$ 

# 9.7 Impedance Combinations (4

Example 10 Determine the input impedance of the circuit in figure below at  $\omega = 10$  rad/s.



<u>Answer</u>:  $Z_{in} = (149.52 - j195) \Omega$