

$$F = G \frac{m_1 m_2}{d^2}$$

Electrical Engineering 1

12026105

Chapter 2

Basic Laws

$$\frac{df}{dt} = \lim_{h \rightarrow 0} \frac{f(t+h) - f(t)}{h}$$

Learning Objectives

By using the information and exercises in this chapter you will be able to:

1. Know and understand the voltage current relationship of resistors (Ohm's law).
2. Understand the basic structure of electrical circuits, essentially nodes, loops, and branches.
3. Understand Kirchhoff's voltage and current laws and their importance in analyzing electrical circuits.
4. Understand series resistances and voltage division, and parallel resistances and current division.
5. Know how to convert delta-connected circuits to wye-connected circuits and how to convert wye-connected circuits to delta-connected circuits.

วัตถุประสงค์ การเรียนรู้

โดยใช้ข้อมูลและแบบฝึกหัดในบทนี้ นักเรียนจะสามารถ:

1. รู้และเข้าใจความสัมพันธ์ระหว่างแรงดันไฟฟ้าและกระแสไฟฟ้าของตัวต้านทาน (กฎของโอห์ม)
2. เข้าใจโครงสร้างพื้นฐานของวงจรไฟฟ้าว่าประกอบด้วยโหนด ลูป และแขนง (nodes, loops, branches)
3. เข้าใจกฎแรงดันไฟฟ้าและกระแสไฟฟ้าของ Kirchhoff และความสำคัญในการวิเคราะห์วงจรไฟฟ้า
4. เข้าใจการต่ออนุกรมความต้านทานและการแบ่งแรงดัน และการต่อขนานความต้านทานและการแบ่งกระแส
5. รู้วิธีแปลงวงจรที่เชื่อมต่อเดลต้าเป็นไวย์ ($\nabla \rightarrow Y$) และวิธีการแปลงวงจรที่เชื่อมต่อไวย์เป็นเดลต้า ($Y \rightarrow \nabla$)

Basic Laws - Chapter 2



Ohm's Law.



Nodes, Branches, and Loops.



Kirchhoff's Laws.




Series Resistors and Voltage Division.





Parallel Resistors and Current Division.



Wye-Delta Transformations.

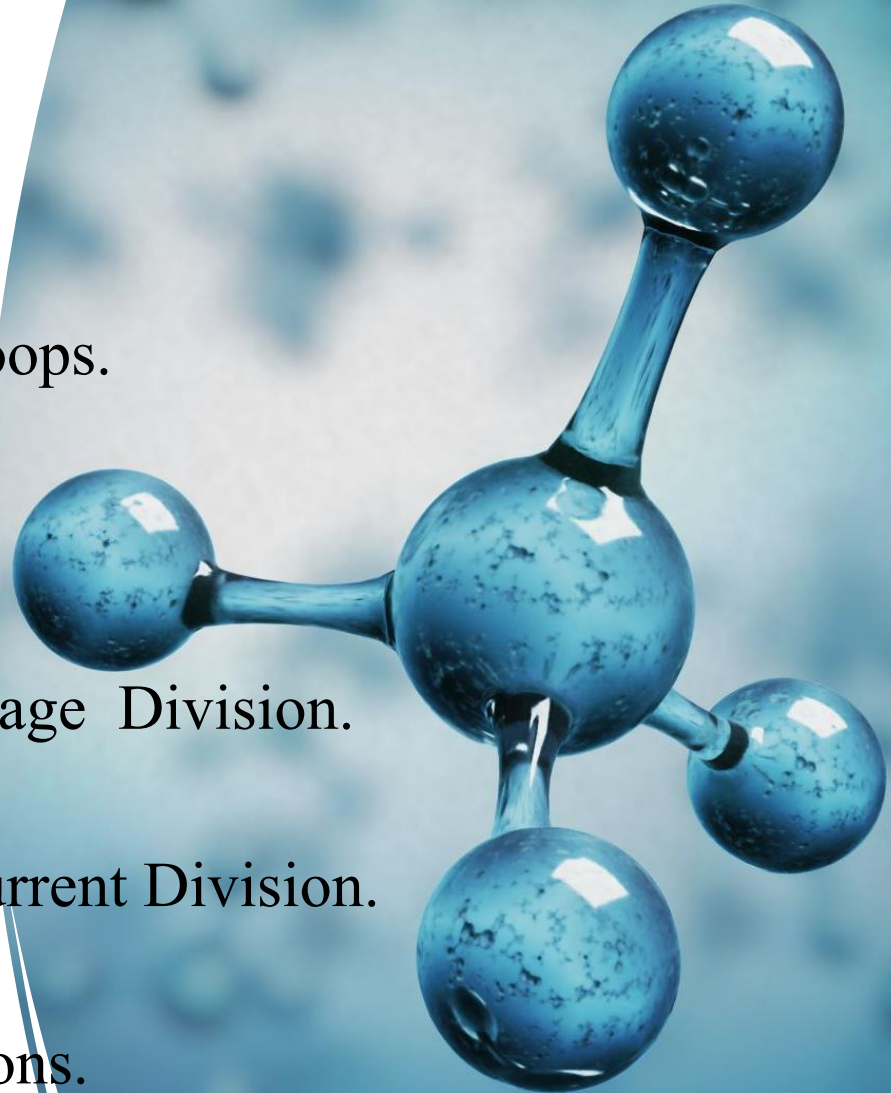

2.1 Ohms Law (1)

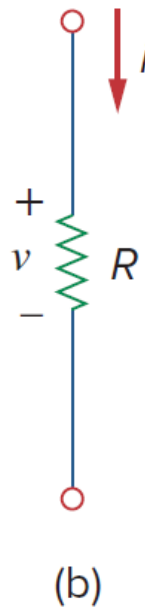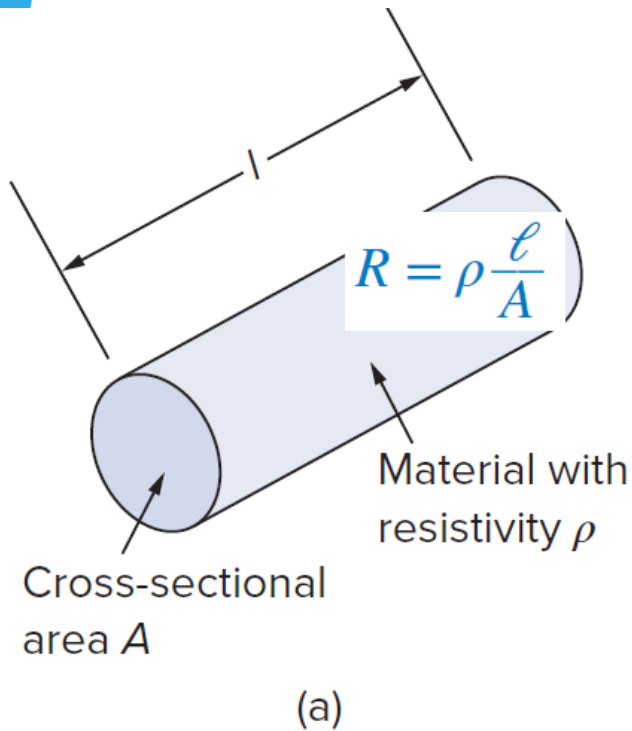


- The resistance R of any material with a uniform cross-sectional area A depends on A and its length l .
- ρ is known as the resistivity of the material in ohm-meters.

(a) Resistor, (b) Circuit symbol for resistance.

2.1 Ohms Law (2)


- Ohm's law states that "the voltage v across a resistor is directly proportional to the current i flowing through the resistor R ". ($v \propto i$)
- Mathematical expression for Ohm's Law is as follows:

$$v = i \times R$$

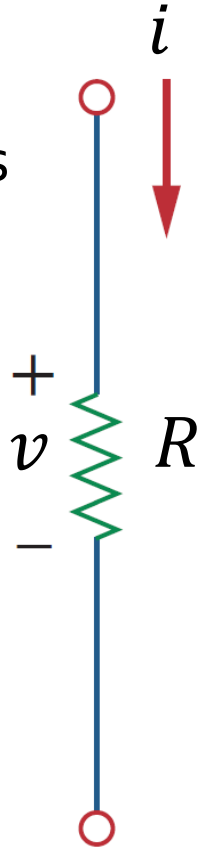


2.1 Ohms Law (3)

- Two extreme possible values of R

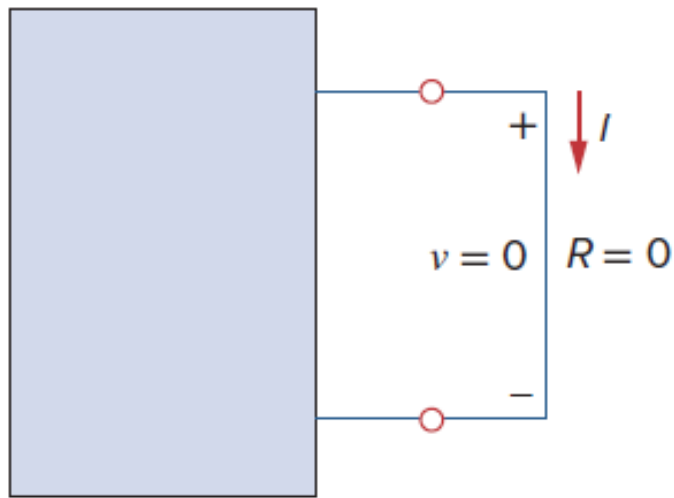

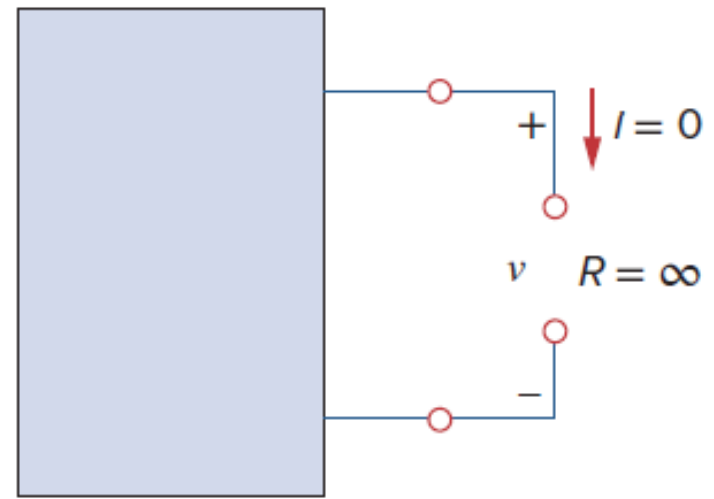(a) Short circuit ($R = 0$)


A *short circuit (SC)* is a circuit element with R approaching zero ($R = 0$)





(b) Open circuit ($R = \infty$).

An *open circuit (OC)* is a circuit element with R approaching infinity ($R = \infty$)

2.1 Ohms Law (4)

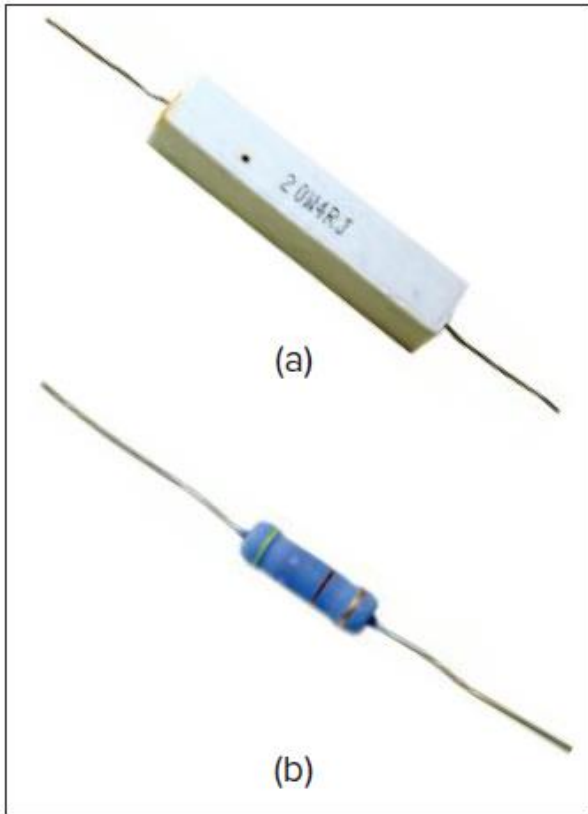

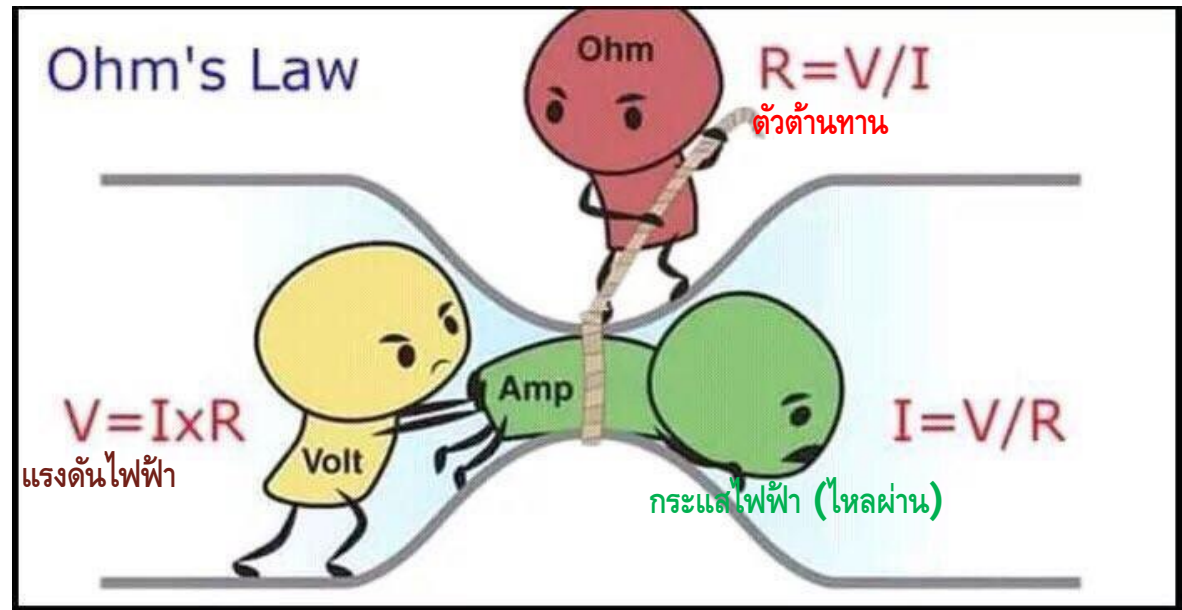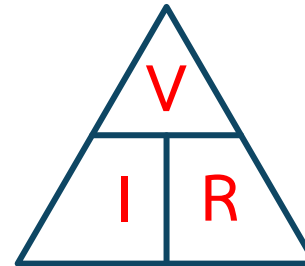Fixed resistors: (a) wirewound type,
(b) carbon film type.
Mark Dierker/McGraw-Hill Education



Ability to resist current (I) is known as resistance (R) measured in ohms (Ω)

2.1 Ohms Law (5)

Conductance is the ability of an element to conduct electric current; it is measured in mho (ohm spelled backward) (\mathcal{U}) or siemens.


$$G = \frac{1}{R} = \frac{i}{v}$$

The power dissipated by a resistor: (*always positive*)

$$p = vi = i^2R = \frac{v^2}{R}$$

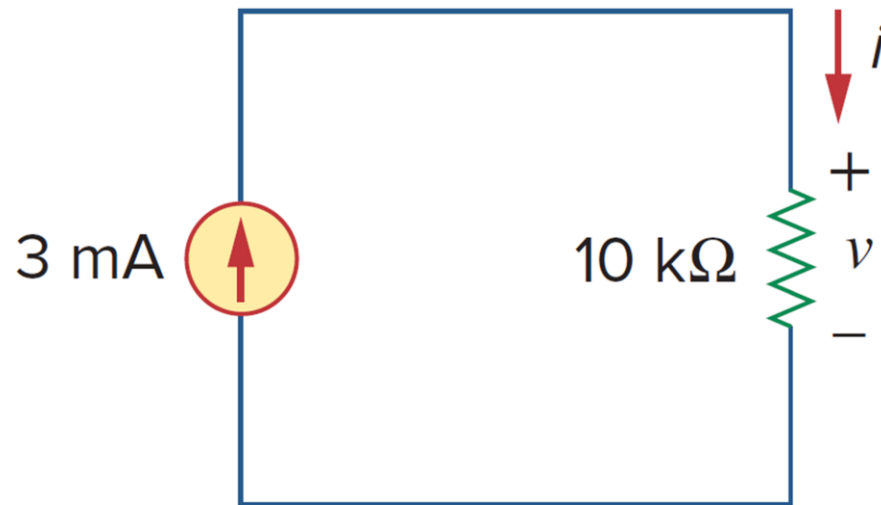2.1 Ohms Law (6)


Ex.1 Calculate the voltage v , the conductance G , and the power p .



30 V, 100 μmho , 90 mW.

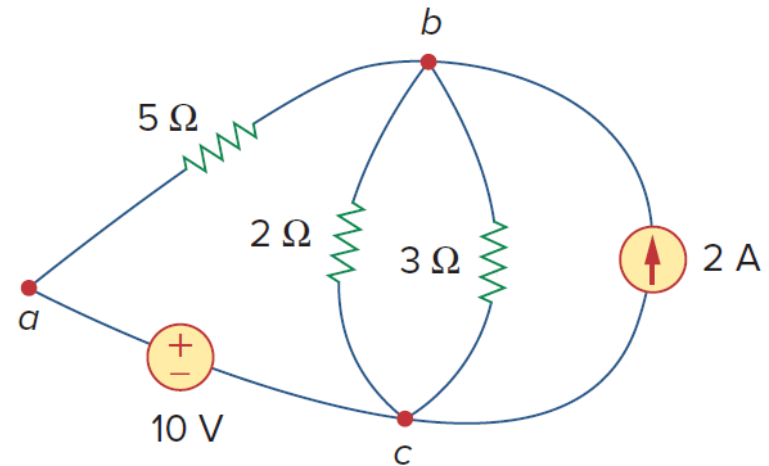
2.2 Nodes, Branches and Loops (1)

- A branch (b) is a single element such as a voltage source, a current source, or a resistor.
- A node (n) is the point of connection between two or more branches.
- A loop (l) is any closed path in a circuit.
- A network with b branches, n nodes, and l independent loops will satisfy the fundamental theorem of network topology: $b = l + n - 1$



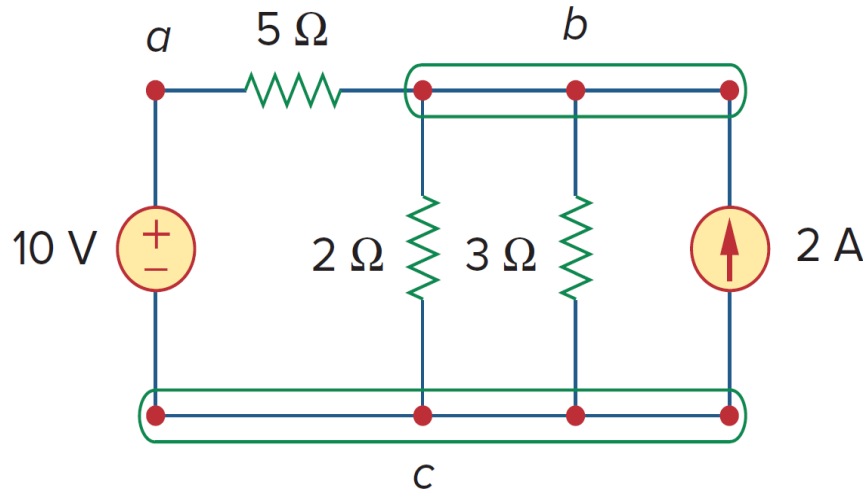
2.2 Nodes, Branches and Loops (2)

Ex.2 How many branches, nodes and loops are there?



Original circuit

$$b = l + n - 1$$
$$5 = 3 + 3 - 1$$

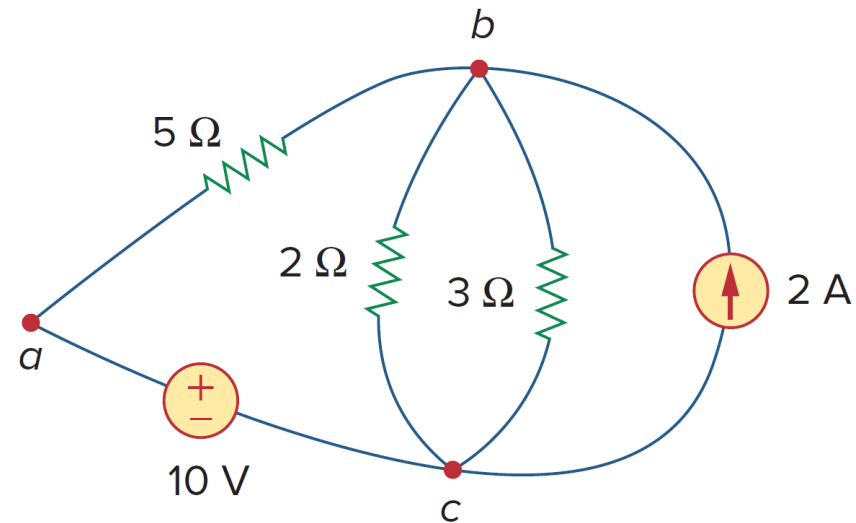


Equivalent circuit 12

2.2 Nodes, Branches and Loops (3)

Ex.3 How many branches, nodes and loops are there?

We must consider it as 2 branches.

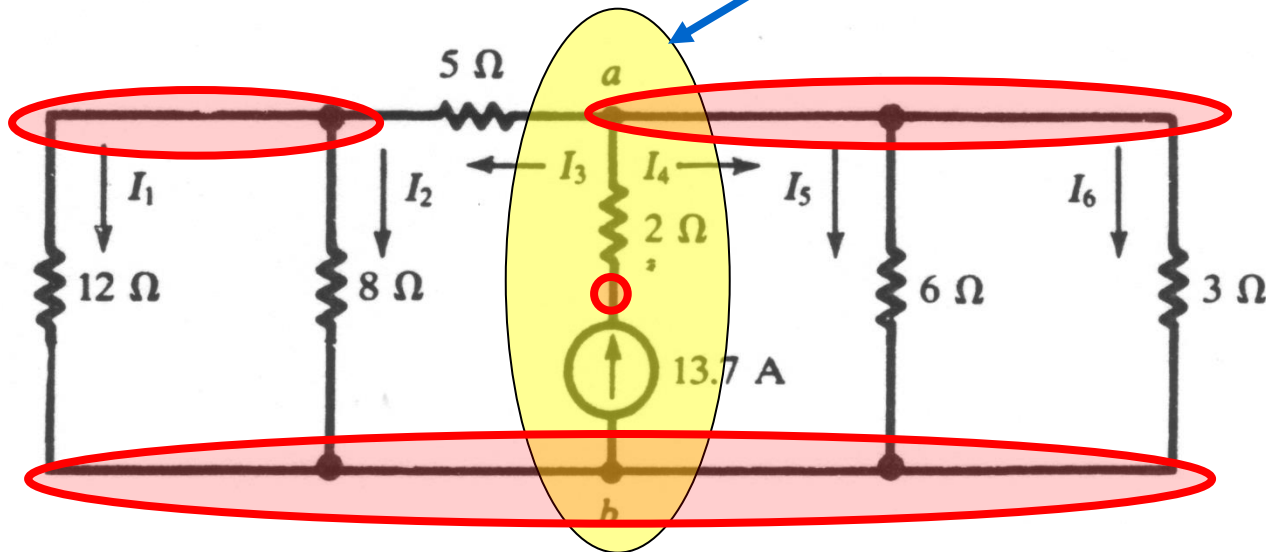


$$b = l + n - 1$$

$$7 = 4 + 4 - 1$$

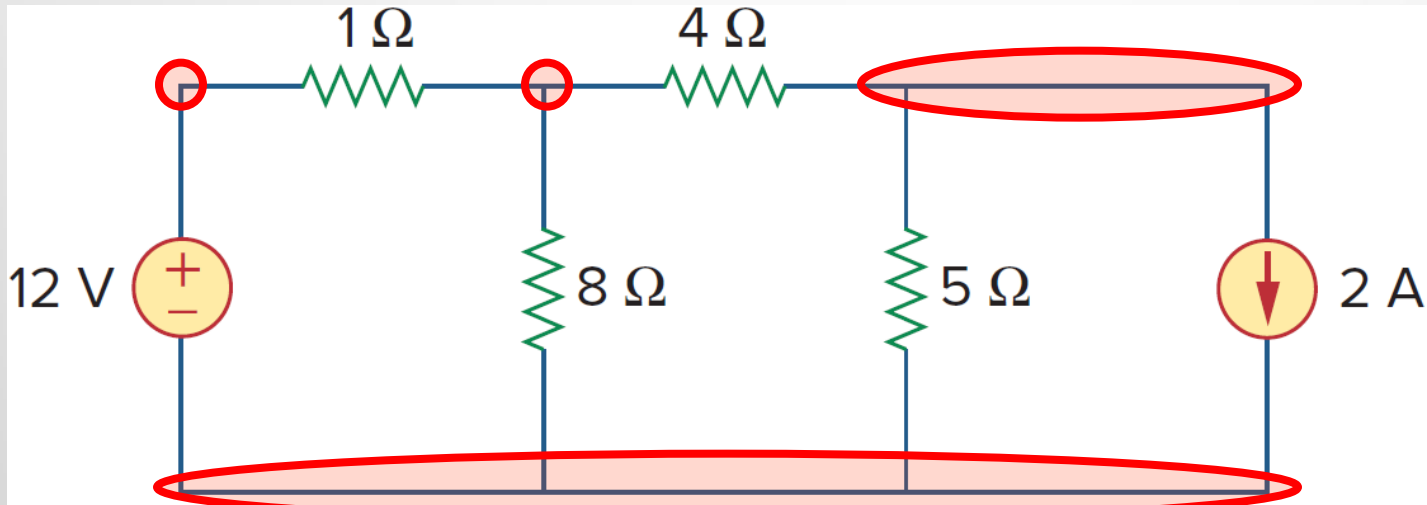2.2 Nodes, Branches and Loops (4)


Ex.4 How many branches, nodes and loops are there?



$$b = l + n - 1$$


$$6 = 3 + 4 - 1$$

2.3 Kirchhoff's Laws (KCL)

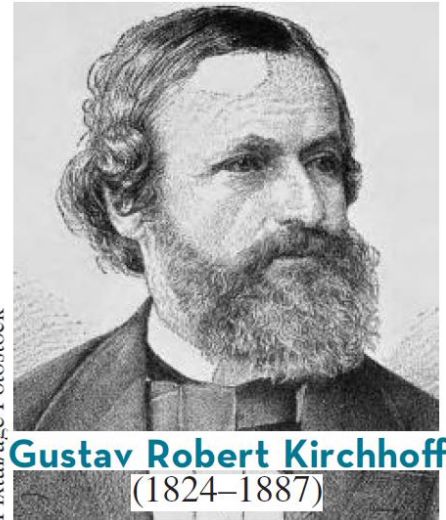


Pixtal/age Fotostock

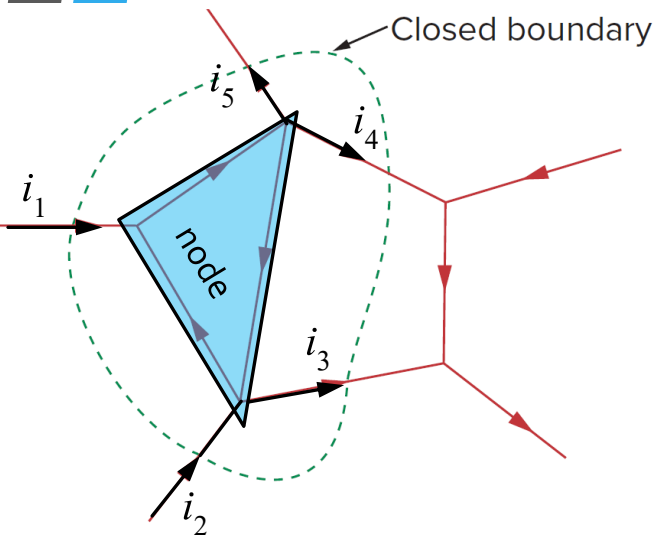- Kirchhoff's current law (KCL) : algebraic sum of currents entering a node (or a closed boundary) is **ZERO**. (ผลรวมของกระแสที่ไหลเข้าโหนดเท่ากับศูนย์ หรือ กระแสไหลเข้าโหนดเท่ากับกระแสไหลออกจากโหนด)



Applying KCL to a closed boundary.

$$i_1 + i_2 - i_3 - i_4 - i_5 = 0$$

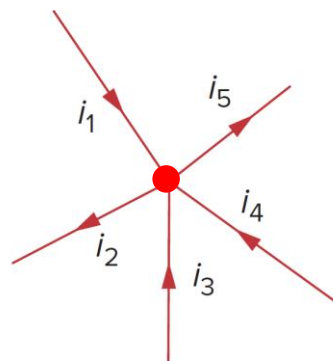

Currents at a node illustrating KCL


$$i_1 - i_2 + i_3 + i_4 - i_5 = 0$$

$$i_1 + i_3 + i_4 = i_2 + i_5$$

$$\sum_{n=1}^N i_n = 0$$


2.3 Kirchhoff's Laws (KCL)

$$I_1 = I_2 + I_3$$

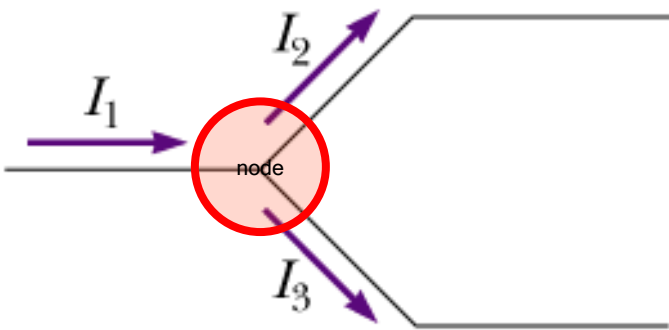

(a)


กระแสไฟฟ้า

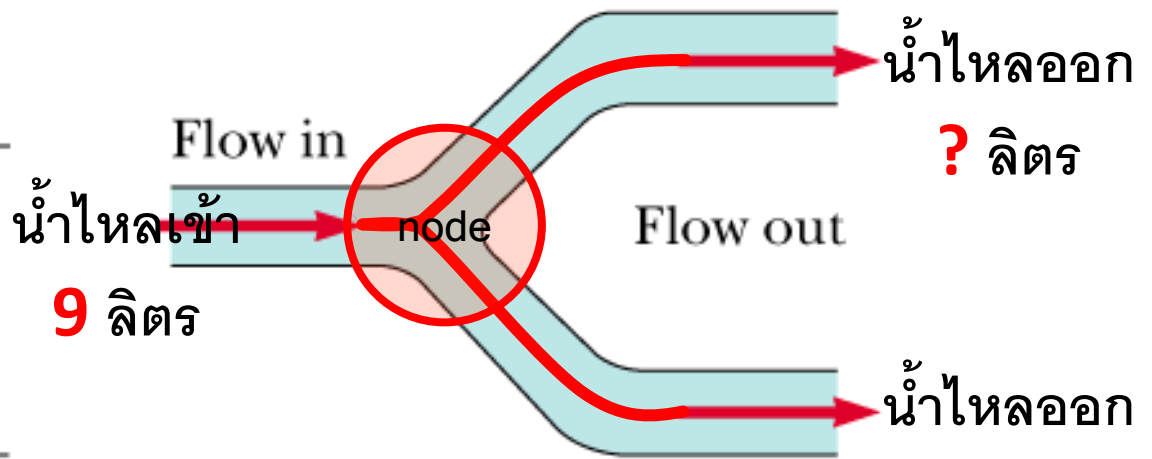

(b)

กระแสน้ำ

2.3 Kirchhoff's Laws (KVL)

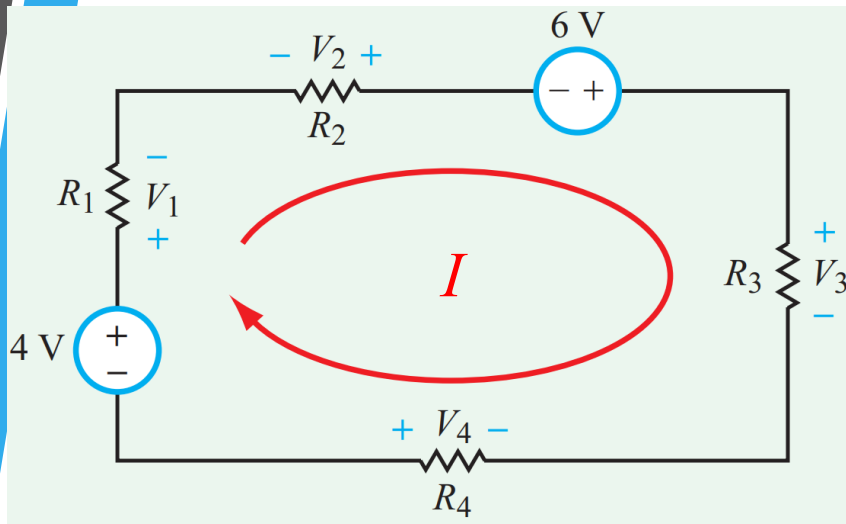

$$V_1 - V_2 - 6 + V_3 - V_4 - 4 = 0$$

$$V_1 = IR_1$$

$$V_2 = -IR_2$$

$$V_3 = IR_3$$


$$V_4 = -IR_4$$

- Kirchhoff's voltage law (KVL): algebraic sum of all voltages around a closed path (or loop) is **ZERO**. (ผลรวมของแรงดันไฟฟ้ารอบลูปใด ๆ มีค่าเท่ากับศูนย์)

$$\sum_{n=1}^N V_n = 0$$

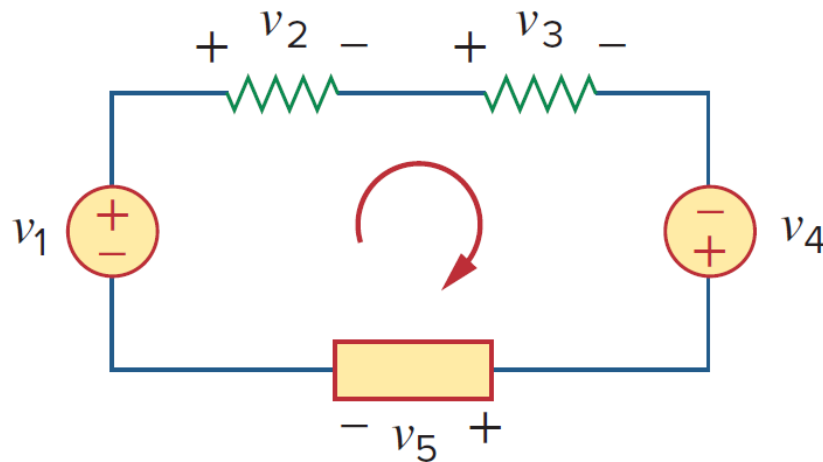2.3 Kirchhoff's Laws (KVL)

Ex.5 Applying the KVL equation for the circuit of the figure below.




$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

$$v_1 + v_4 = v_2 + v_3 + v_5$$

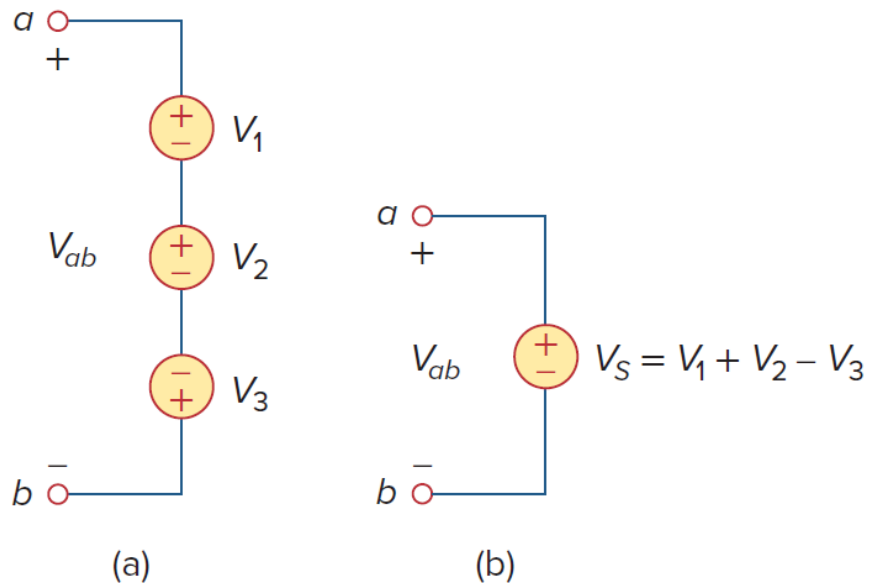2.3 Kirchhoff's Laws (KVL)

Ex.6 Applying the KVL equation for the circuit of the figure below.



$$V_a - V_b = V_{ab} = V_1 + V_2 - V_3$$


2.3 Kirchhoff's Laws (KVL)

Ex.7 Find v_1 and v_2 in the circuit

$$v_1 - 8 - v_2 - 34 = 0$$

$$v_1 - v_2 = 42$$

$$v_1 = 4i, \quad v_2 = -2i$$

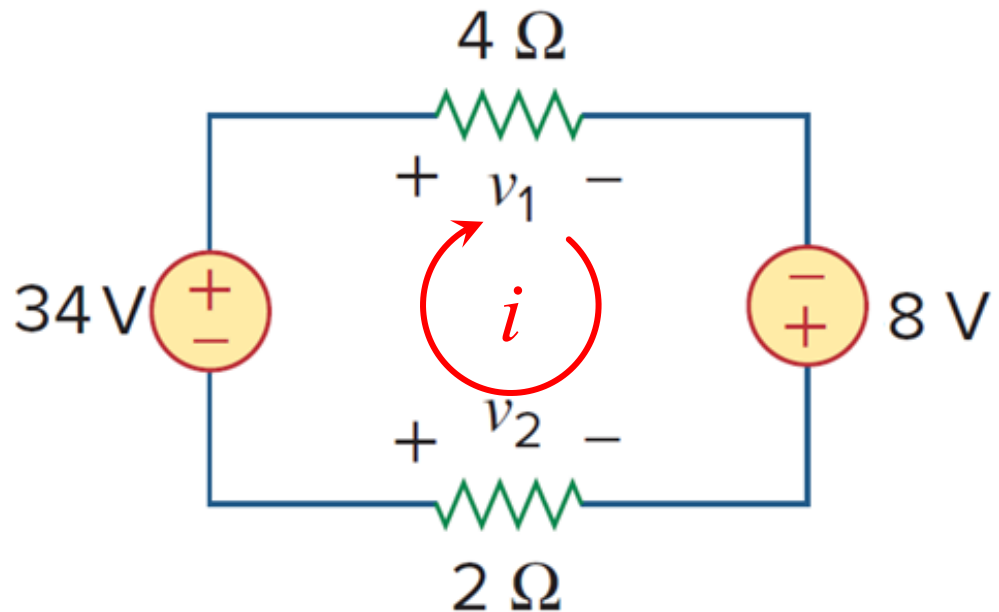

20

$$i = 7\text{A}, \quad v_1 = 28\text{V}, \quad v_2 = -14\text{V}$$


Realistic Resistors

Resistor color code


Band color	Value
Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Grey	8
White	9
Gold	0.1
Silver	0.01

Tolerance color code


Band color	$\pm\%$
Brown	1
Red	2
Gold	5
Silver	10
None	20

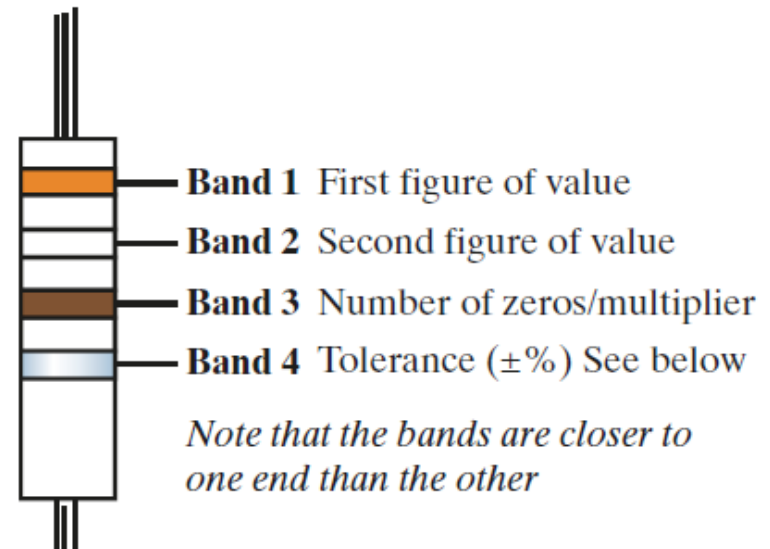


Resistor Values

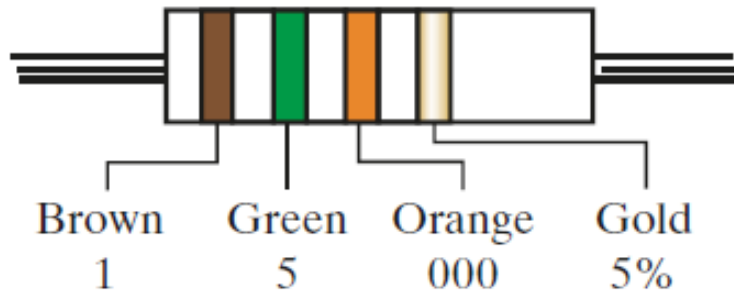

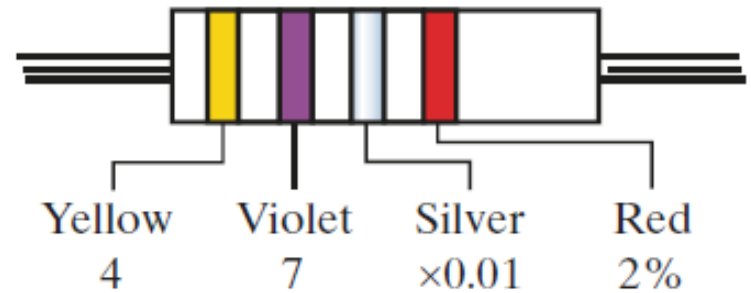
Resistor is 15000Ω or $15 \text{ k}\Omega \pm 5\%$



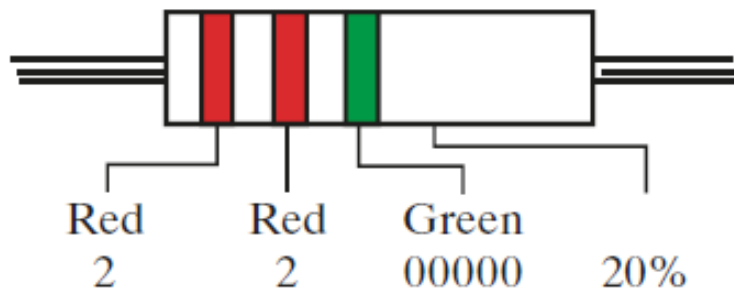Resistor is $47 \times 0.01 \Omega$ or $0.47 \Omega \pm 2\%$



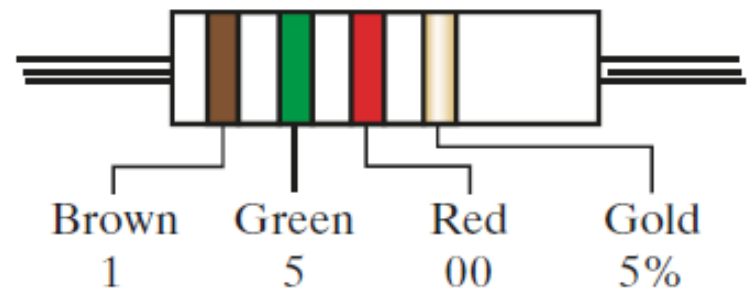Resistor is 2200000Ω or $2.2 \text{ M}\Omega \pm 20\%$




Resistor is 1500Ω or $1.5 \text{ k}\Omega \pm 5\%$

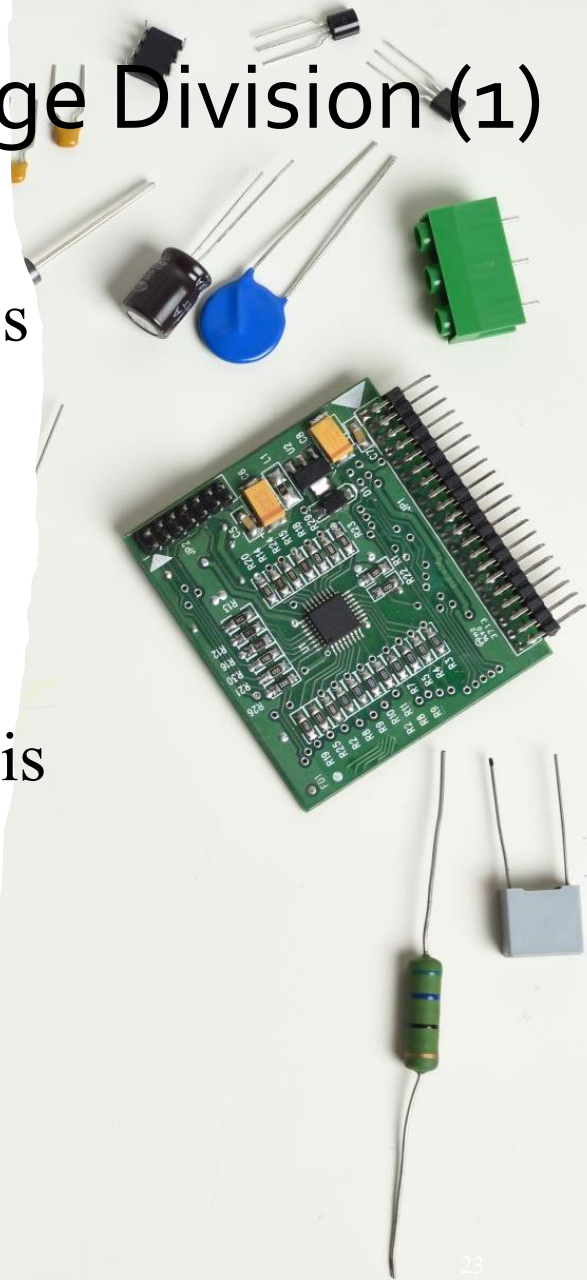2.4 Series Resistors and Voltage Division (1)


- Series: Two or more elements are in series if they are connected sequentially and consequently carry the *same current*.
- The equivalent resistance (R_{eq}) of any number of resistors connected in a series is the sum of the individual resistances.
- The *voltage divider* can be expressed as

$$v_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} v$$




2.4 Series Resistors and Voltage Division (2)

Ex.8

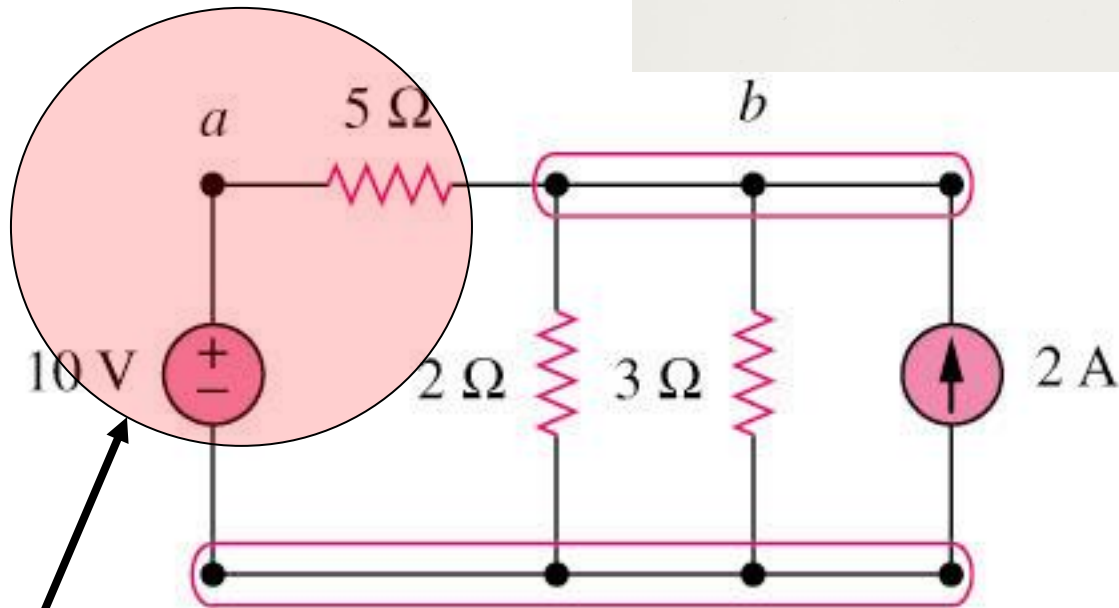

10V and 5Ω are in series

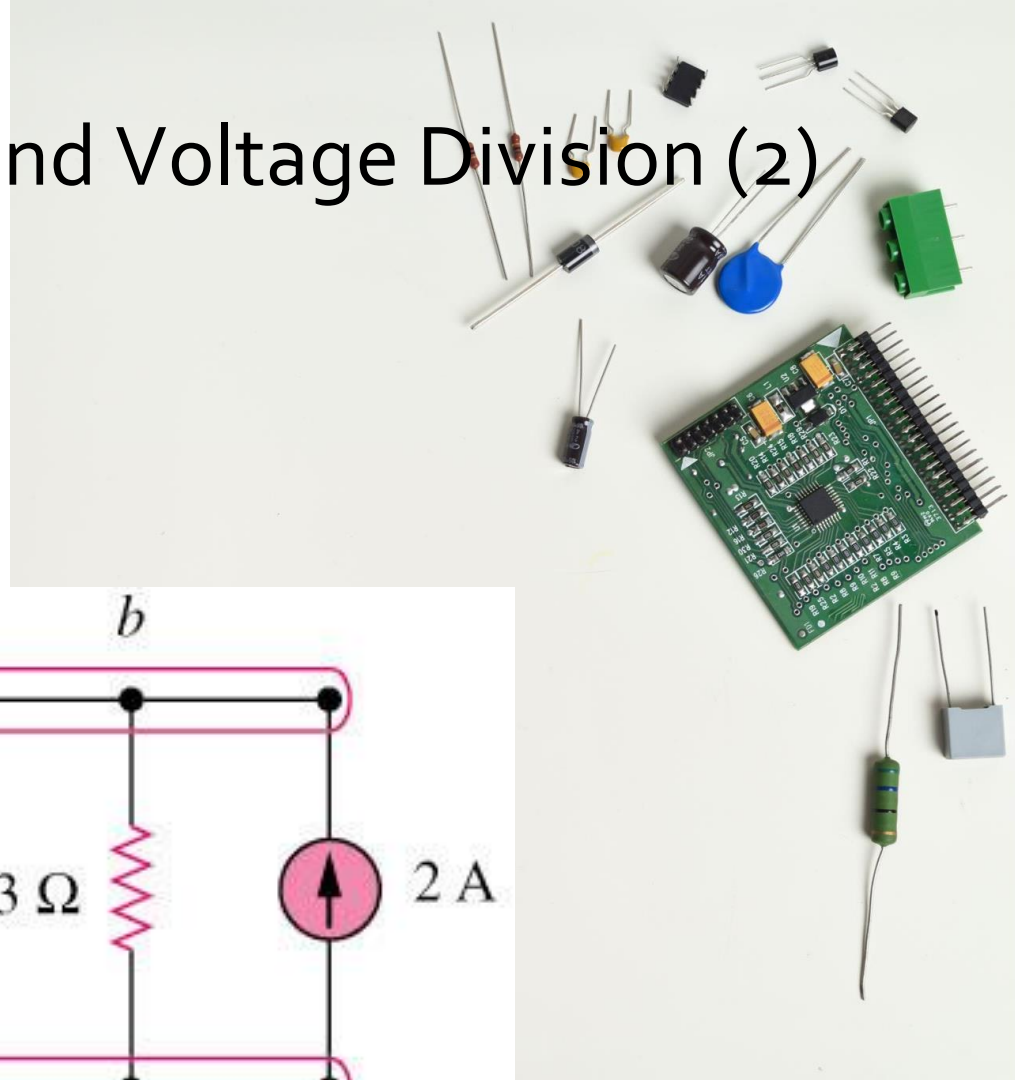

2.5 Parallel Resistors and Current Division (1)

- Parallel: Two or more elements are in parallel if they are connected to the same two nodes and consequently have the *same voltage* across them.
- The equivalent resistance of a circuit with N resistors in parallel is :

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

- The total current *i* is shared by the resistors in inverse proportion to their resistances. The *current divider* can be expressed as

$$i_n = \frac{v}{R_n} = \frac{i R_{eq}}{R_n}$$

2.5 Parallel Resistors and Current Division (2)

- $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

- $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$


$$\Rightarrow R_{eq} = \frac{R_1 R_2 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2}$$

- $\frac{1}{R_{eq}} = \underbrace{\frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R}}_N \Rightarrow R_{eq} = \frac{R}{N}$

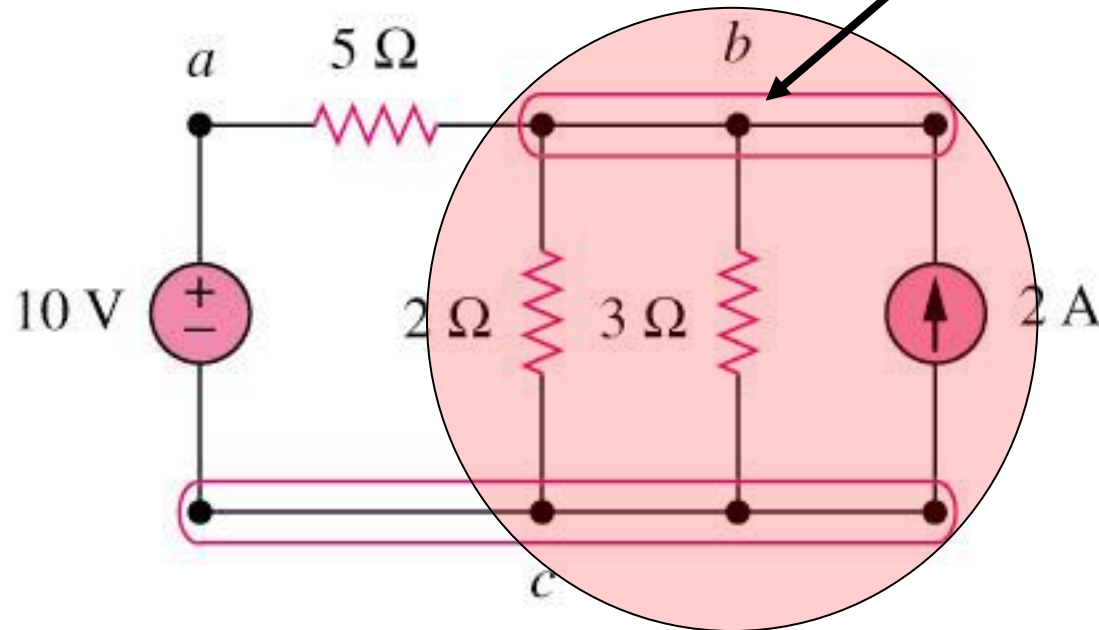2.5 Parallel Resistors and Current Division (3)


Ex.9

$2\ \Omega$, $3\ \Omega$ and 2A
are in parallel






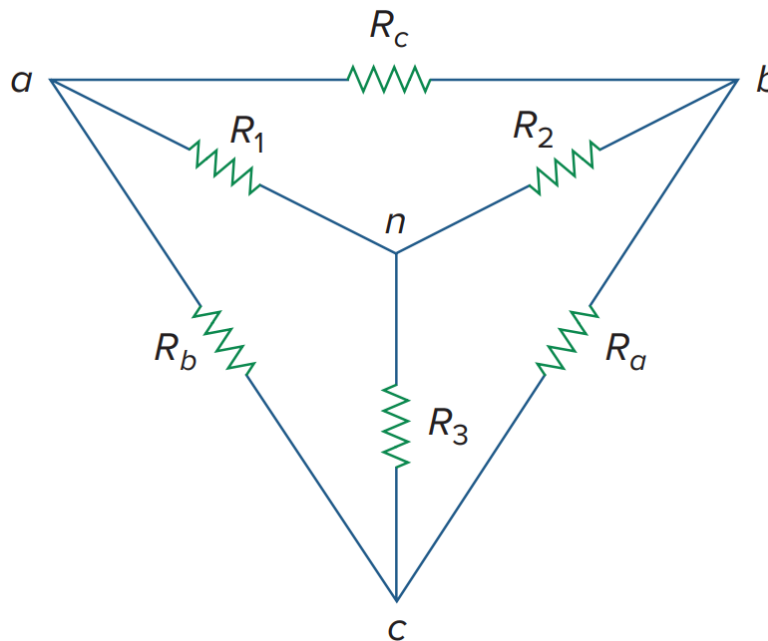2.6 Wye-Delta Transformations


$$\begin{aligned} R_1 &= \frac{R_b R_c}{(R_a + R_b + R_c)} & \Leftrightarrow & R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \\ R_2 &= \frac{R_c R_a}{(R_a + R_b + R_c)} & \Leftrightarrow & R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \\ R_3 &= \frac{R_a R_b}{(R_a + R_b + R_c)} & \Leftrightarrow & R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \end{aligned}$$



2.7 Problems(1)

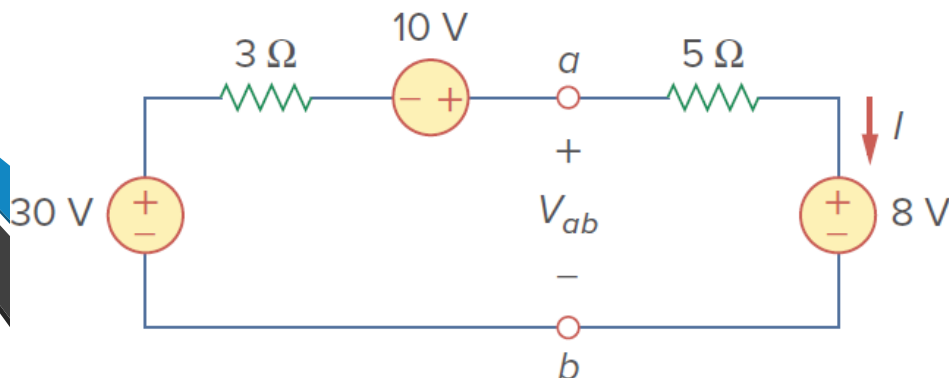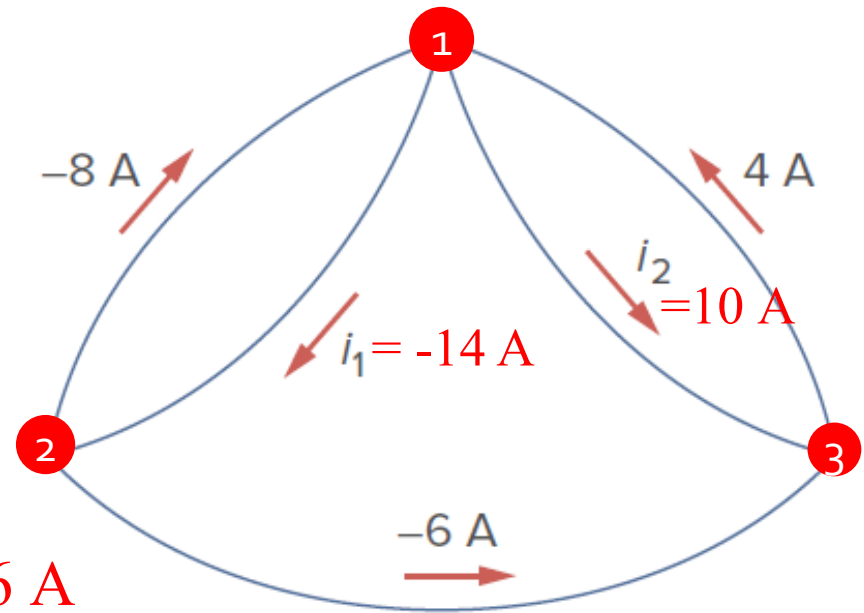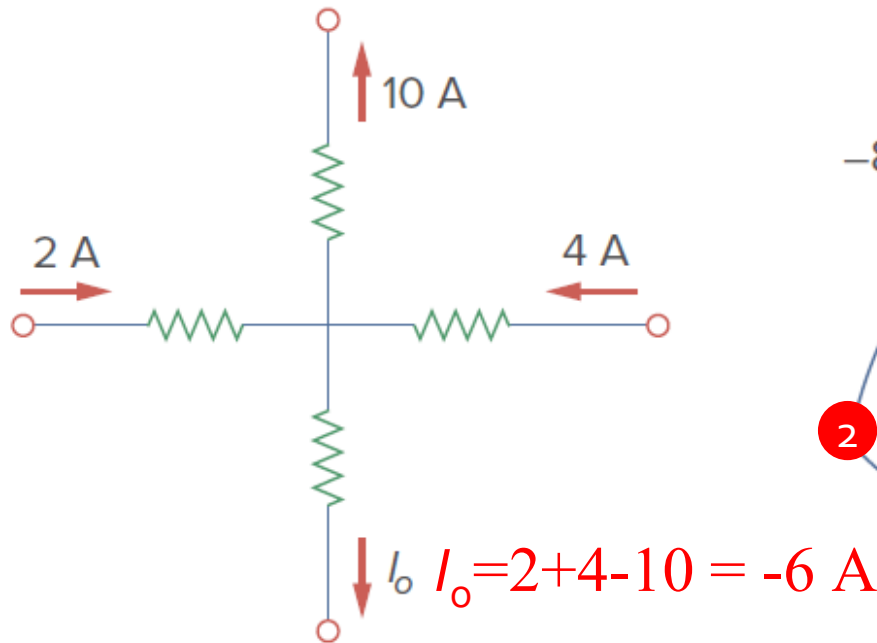


$I = 4 \text{ A}, V_{ab} = 28 \text{ V}$

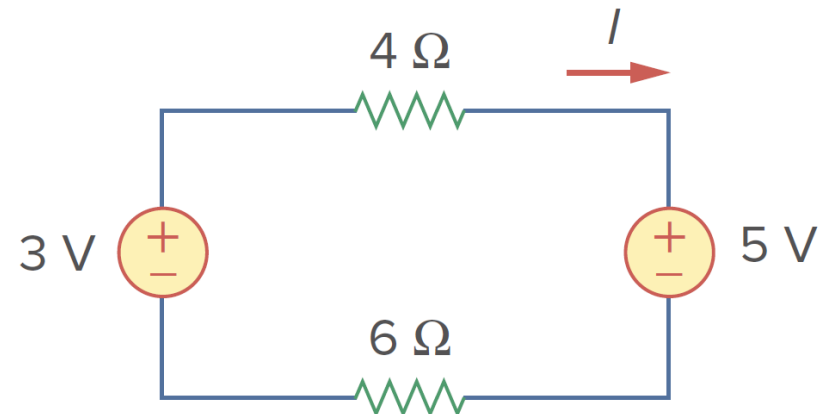

$5 - 3 + 10I = 0, I = -0.2 \text{ A}$

2.7 Problems(2)

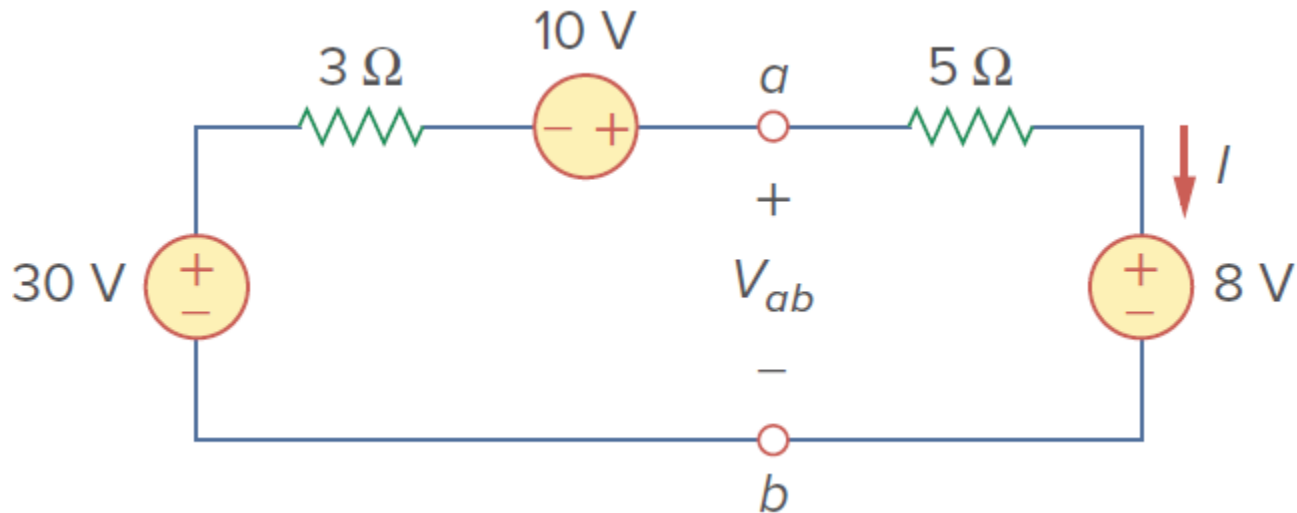

$$I = v/R = (-8 + 30 + 10)/(3 + 5) = 4 \text{ A}$$

$$V_{ab} = 30 - 12 + 10 = 28 \text{ V} \text{ , หรือ } V_{ab} = 20 + 8 = 28 \text{ V}$$