

$$F = G \frac{m_1 m_2}{d^2}$$

# Electrical Engineering 1

12026105

Chapter 4

Circuit Theorems

$$\frac{df}{dt} = \lim_{h \rightarrow 0} \frac{f(t+h) - f(t)}{h}$$

# Circuit Theorems - Chapter 4



Introduction



Linearity Property



Superposition



Source Transformation



Thevenin's Theorem




Norton's Theorem



Maximum Power Transfer
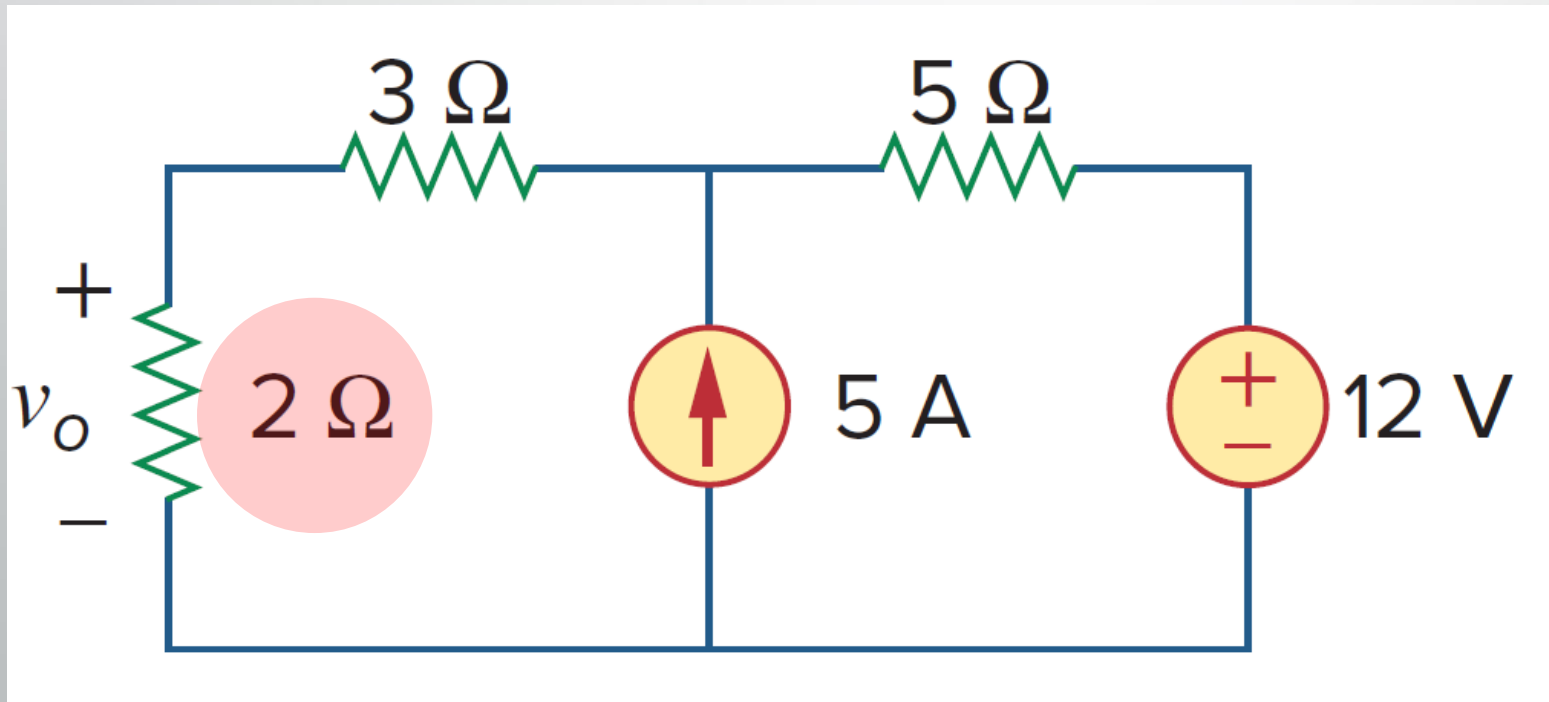
# 4.1 Introduction

Are there any other alters to find the voltage across  $2\Omega$  ?



What are they? And how?

Can you work it out by inspection?

$$v_o = 7.4\text{ V}$$

## 4.2 Linearity Property (1)

- It is the property of an element describing a linear relationship between cause and effect.
- A linear circuit is one whose output is linearly related (directly proportional) to its input.
- The property is a combination of both *homogeneity (scaling)* and *additivity*.

### Homogeneity (scaling) property:

(If  $i$  is increased by a constant  $k$ , then  $v$  increases correspondingly by  $k$ )

$$v = iR \rightarrow kv = kiR$$


### Additive property:

The response to a sum of inputs is the sum of the responses to each input applied separately.

$$\begin{aligned} v_1 &= i_1 R, \quad v_2 = i_2 R \\ \rightarrow v &= (i_1 + i_2) R = v_1 + v_2 \end{aligned}$$
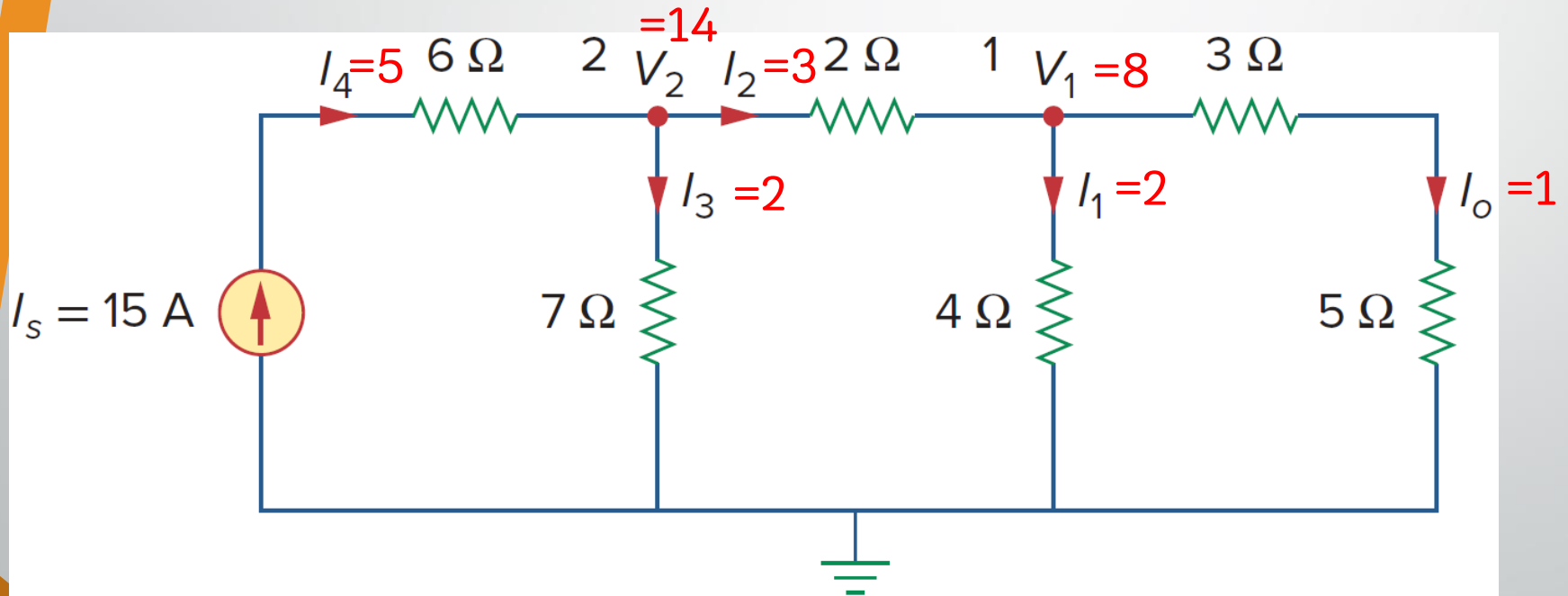
## 4.2 Linearity Property (2)


Ex.1 By assume  $I_o = 1$  A, use linearity to find the actual value of  $I_o$  in the circuit shown below.



$$I_o = 3\text{ A}$$
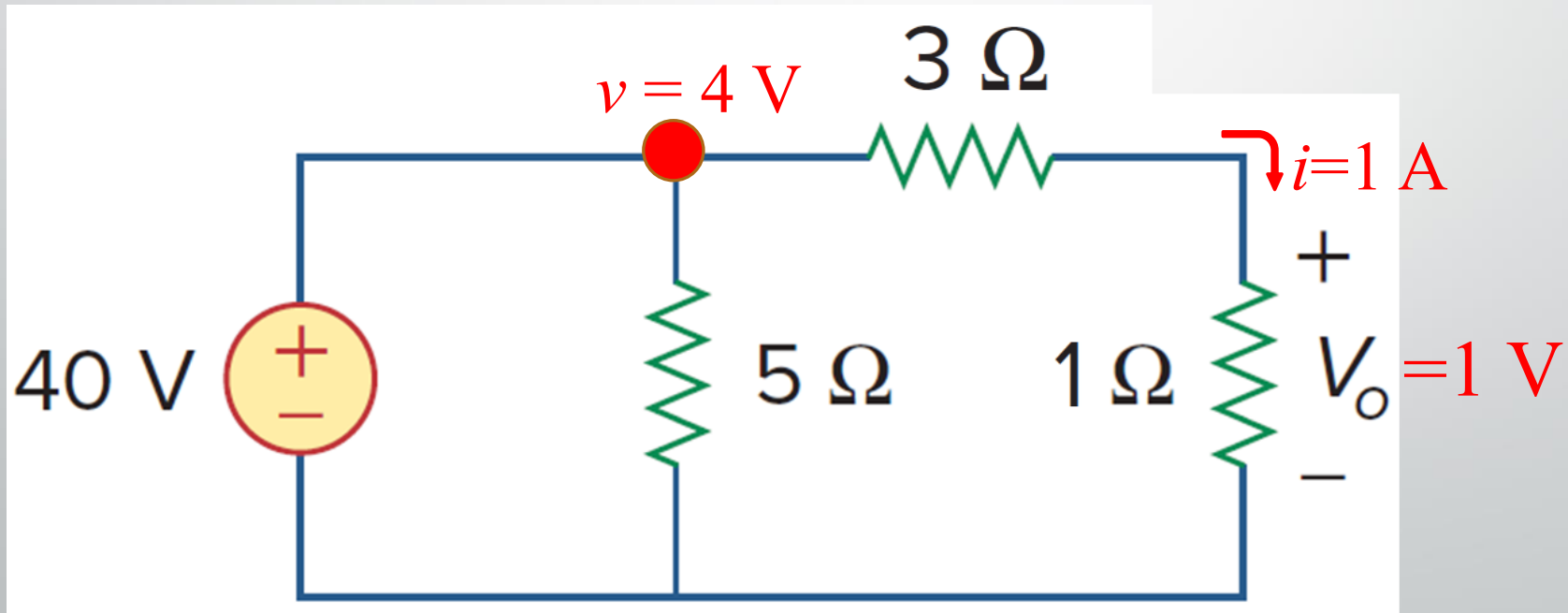
## 4.2 Linearity Property (3)


Ex.2 Assume that  $V_o = 1$  V and use linearity to calculate the actual value of  $V_o$  in the circuit of Fig.



$$V_o = 40 * 1/4 = 10 \text{ V}$$
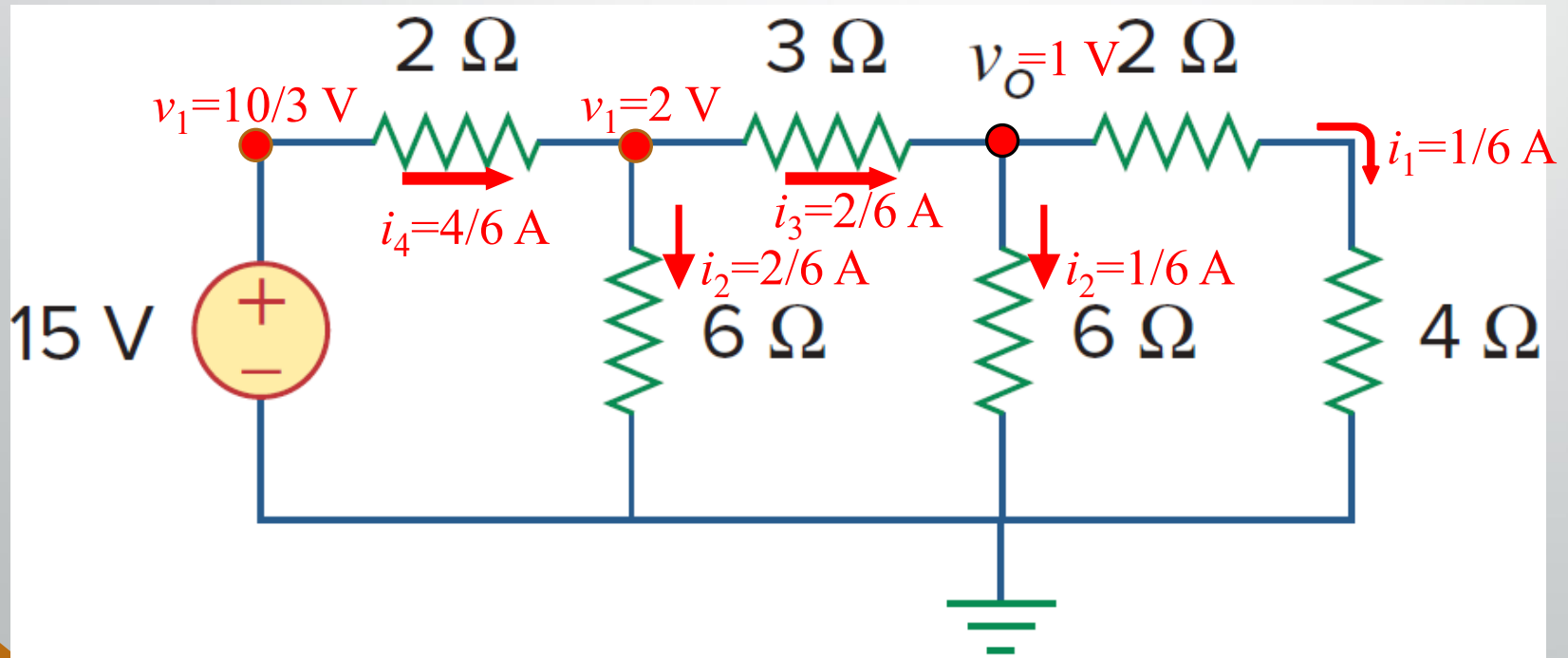
## 4.2 Linearity Property (4)

Ex.3 For the circuit in Fig., assume  $v_o = 1$  V, and use linearity to find the actual value of  $v_o$ .



$$v_o = 15 \cdot 3/10 = 4.5\text{ V}$$



## 4.3 Superposition Theorem (1)

It states that the  $V$  across (or  $I$  through) an element in a linear circuit is the algebraic sum of the voltage across (or currents through) that element due to EACH independent source acting alone.

( “ $V$  ที่ตกคล่อมหรือ  $I$  ที่ไหลผ่านอีลิเมนต์ใดๆ ในวงจรไฟฟ้าเชิงเส้น คือผลรวมพีชคณิตของ  $V$  หรือ  $I$  ที่อีลิเมนต์นั้นๆ อันเนื่องมาจากแหล่งกำเนิดแต่ละตัว” )

The principle of superposition helps us to analyze a linear circuit with more than one independent source by calculating the contribution of each independent source separately.

(หลักการซูเปอร์โพสิชัน ช่วยวิเคราะห์วงจรไฟฟ้าเชิงเส้นที่มีแหล่งกำเนิดอิสระมากกว่า 1 ตัวโดยการแยกคำนวณผลที่เกิดจากแหล่งกำเนิดแต่ละตัวแล้วนำมารวมกัน)




## 4.3 Superposition Theorem (2)

### Steps:

1. Turn off all independent sources except one source. Find the output ( $V$  or  $I$ ) due to that active source.
2. Repeat step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources.
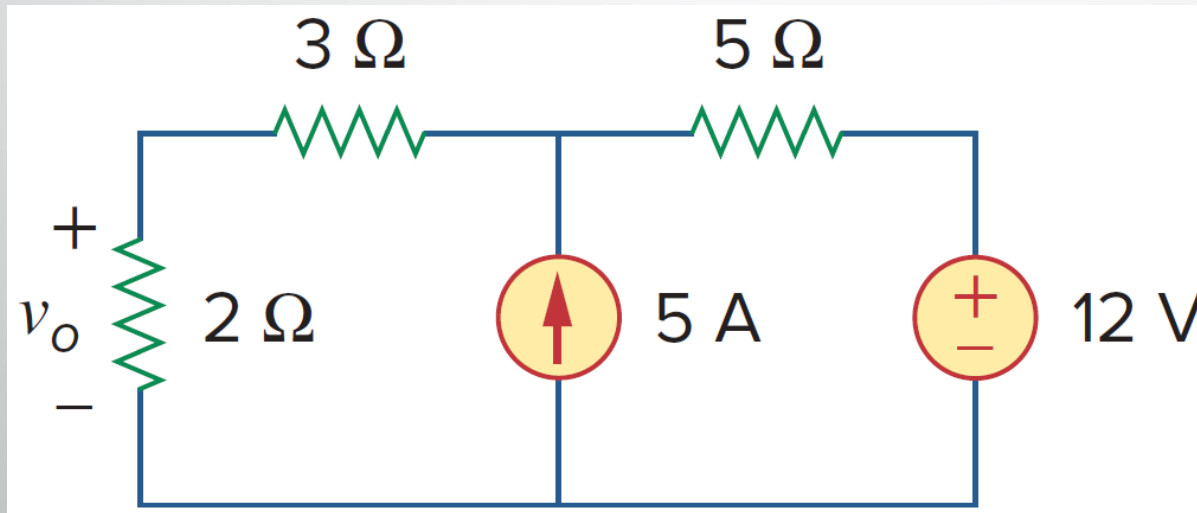
## 4.3 Superposition Theorem (3)




We consider the effects of 5A and 12V one by one, then add the two effects together for final  $v_o$ .



$$v_o = 7.4\text{ V}$$
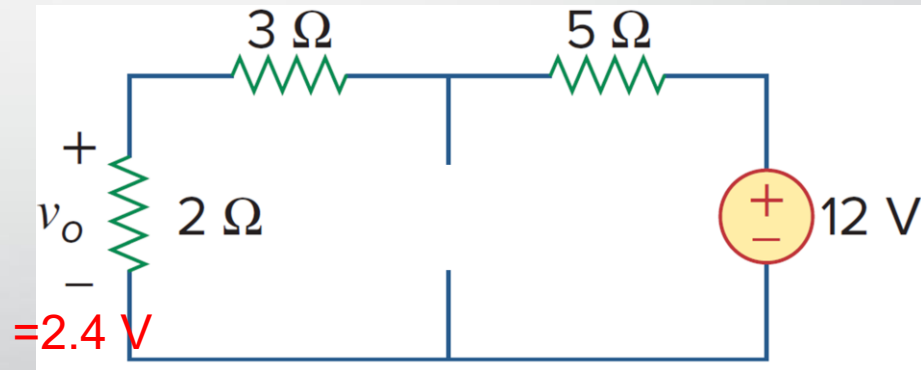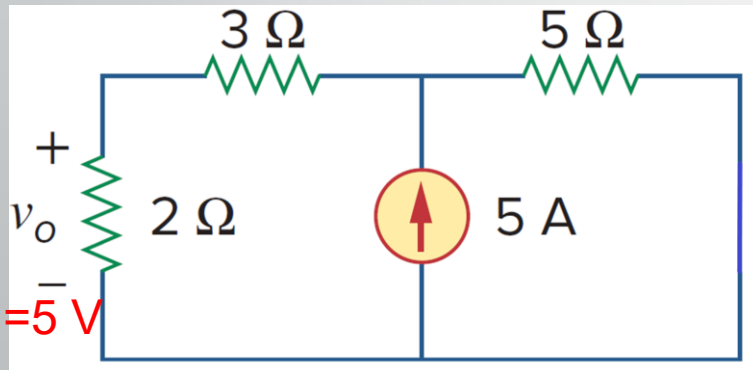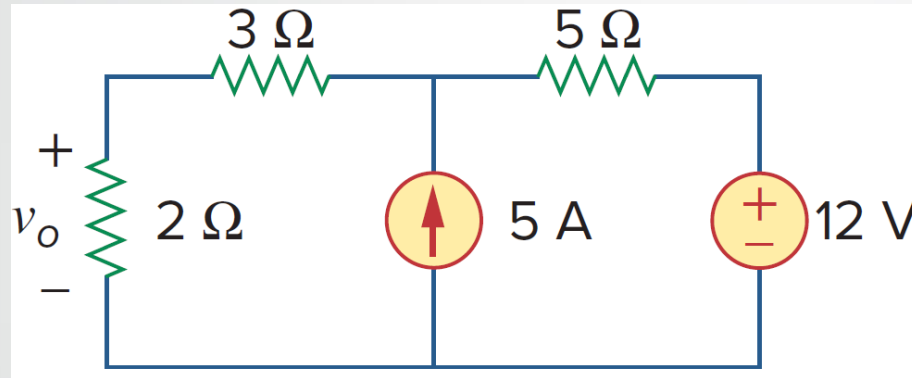
## 4.3 Superposition Theorem (4)


Ex.4 Use superposition to find  $v_x$  in the circuit below.





$$v_o = 7.4\text{ V}$$
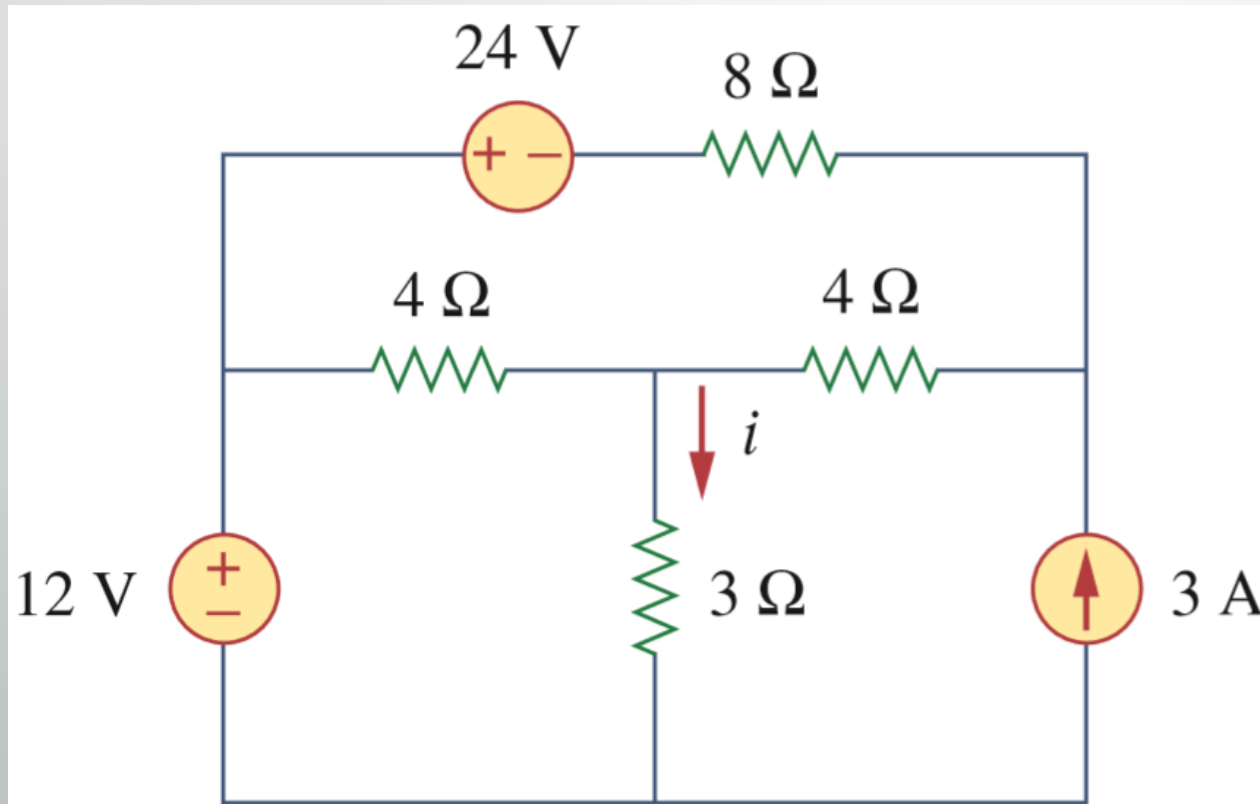
## 4.3 Superposition Theorem (5)


Ex.5 Use superposition to find  $i$  in the circuit below.




$$i = 2A$$

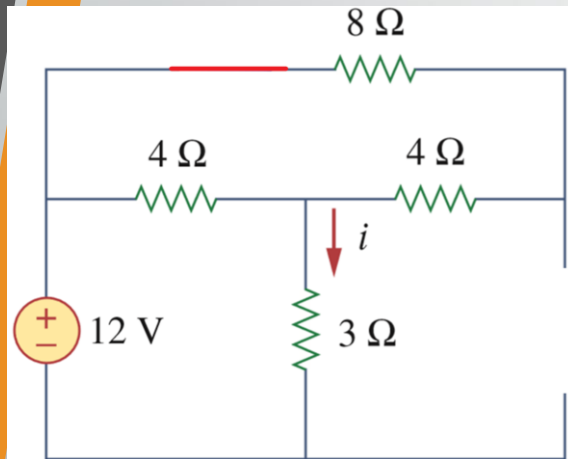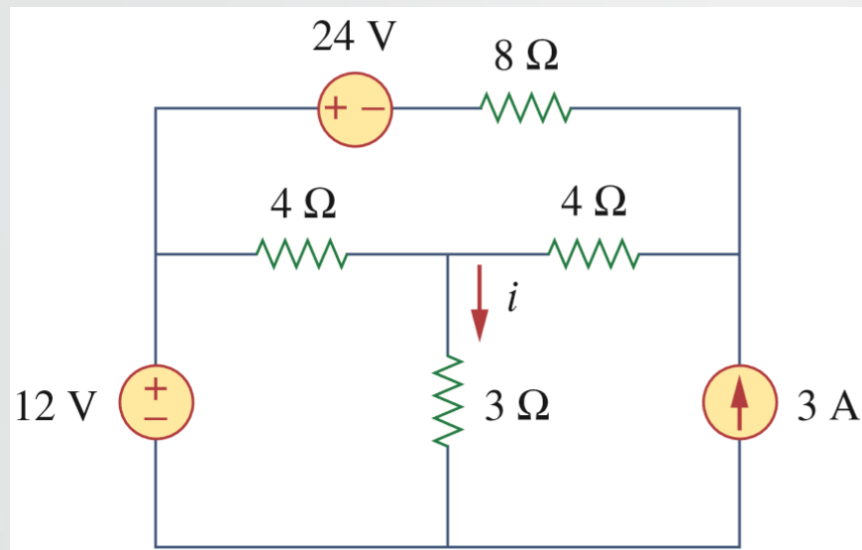
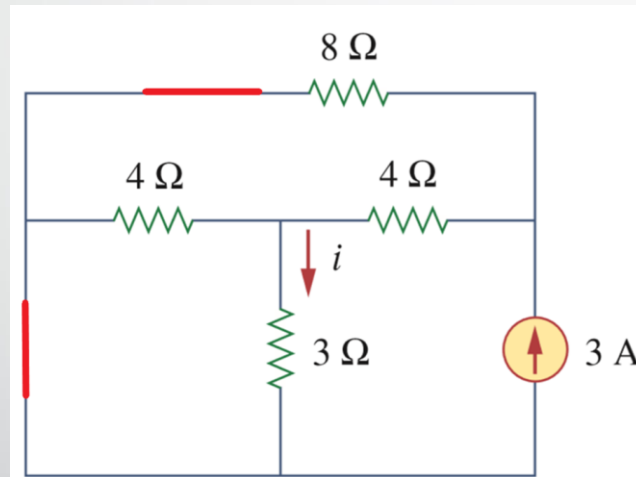
$$i_1 = \left( \frac{12}{3 + (4 \parallel 12)} \right) = 2A$$


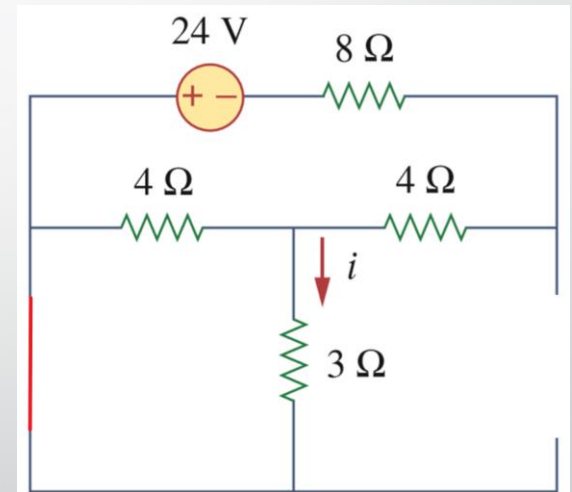
$$i_2 = \left( \frac{8}{8 + (4 + (4 \parallel 3))} \right) \left( \frac{4}{7} \right) 3 = 1A$$







$$i_3 = - \left( \frac{24}{8 + (4 + (4 \parallel 3))} \right) \left( \frac{4}{7} \right) = -1A$$

$$i = i_1 + i_2 + i_3 = 2 + 1 - 1 = 2A$$
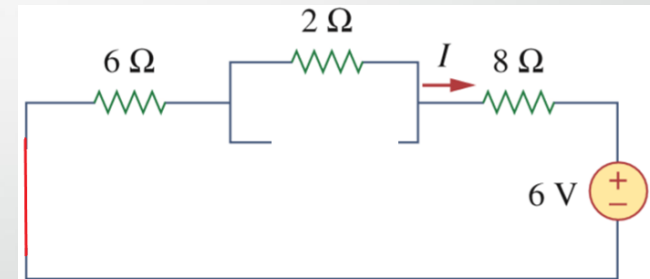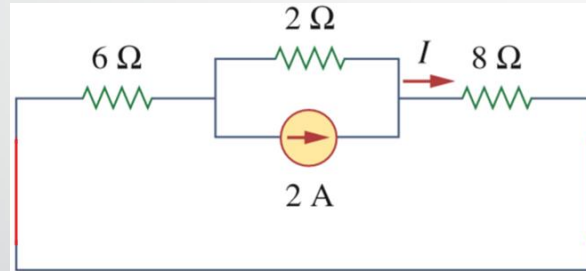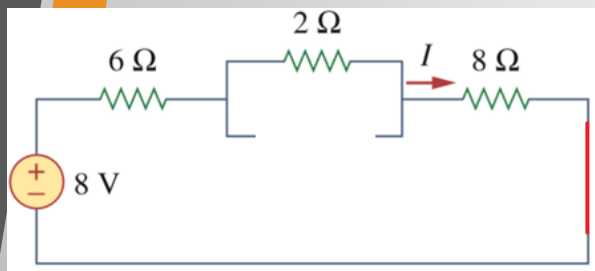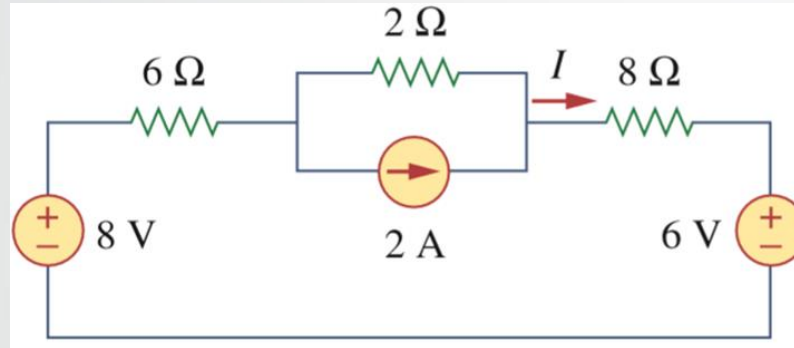
## 4.3 Superposition Theorem (6)

Ex.6 Use superposition to find  $I$  in the circuit below.



$$I = 375 \text{ mA}$$

## 4.3 Superposition Theorem (7)


2 things must keep in mind:

1. When we say turn off all other independent sources:
  - Independent *voltage* sources are replaced by 0 V (short circuit) and
  - Independent *current* sources are replaced by 0 A (open circuit).
2. Dependent sources are left intact because they are controlled by circuit variables.


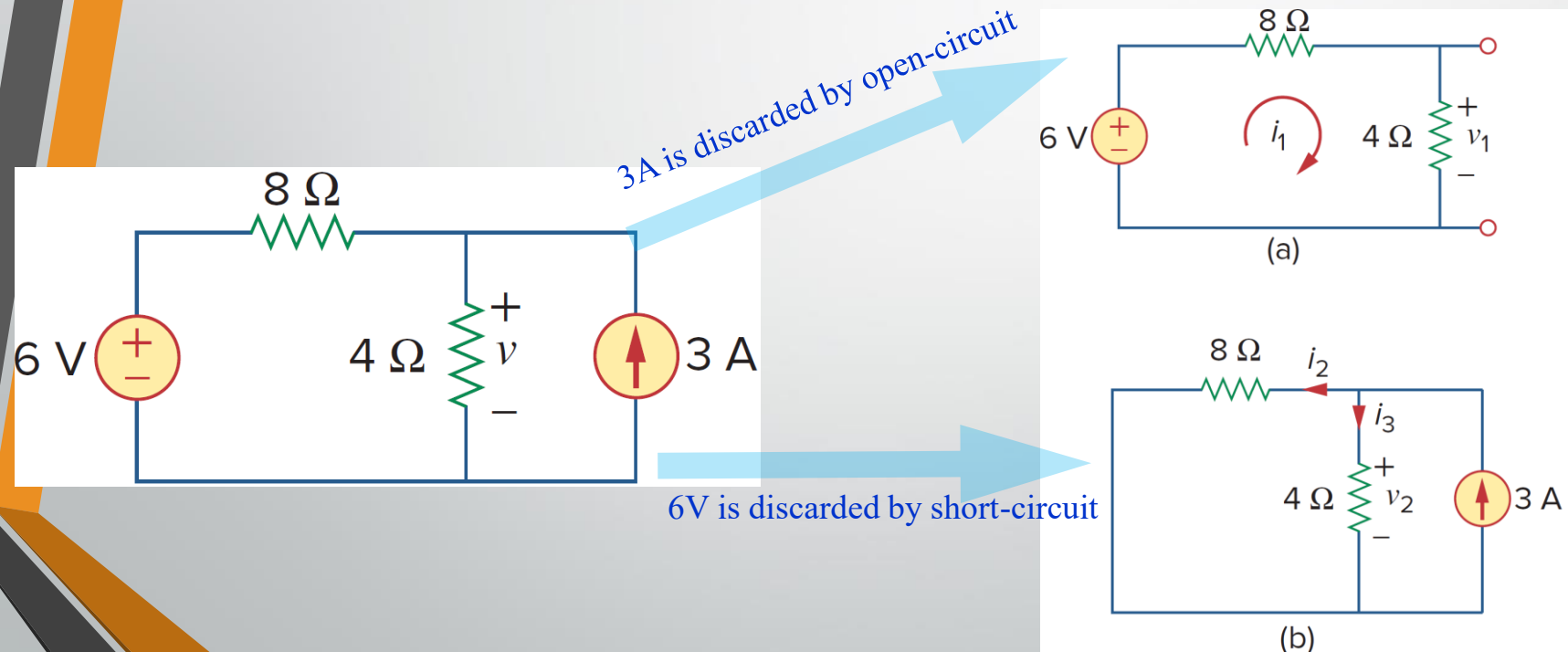
## 4.3 Superposition Theorem (8)


Ex.7 Use the superposition theorem to find  $v$  in the circuit shown below.



$$v = v_1 + v_2 = 2\text{ V} + 8\text{ V} = 10\text{ V}$$
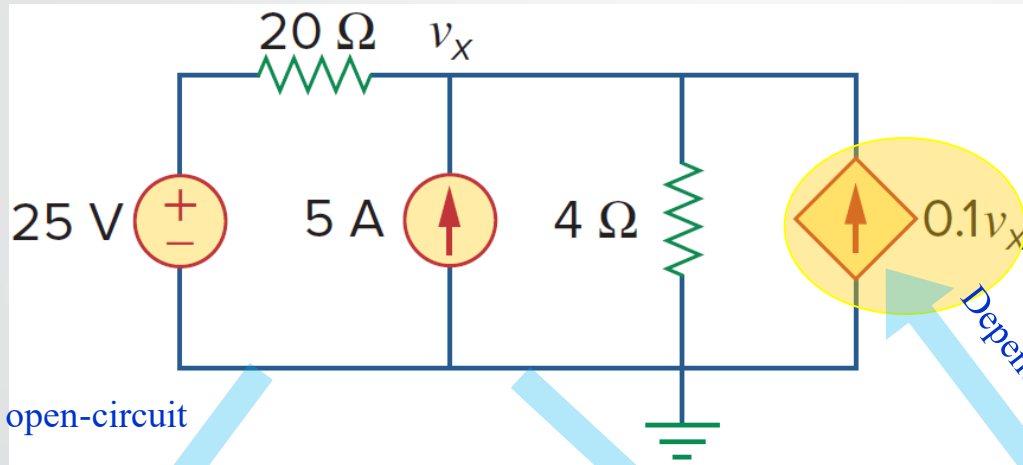
# 4.3 Superposition Theorem (9)



Ex.8 Use superposition to find  $v_x$  in the circuit below.




5A is discarded by open-circuit

25V is discarded by short-circuit

Dependent source keep unchanged

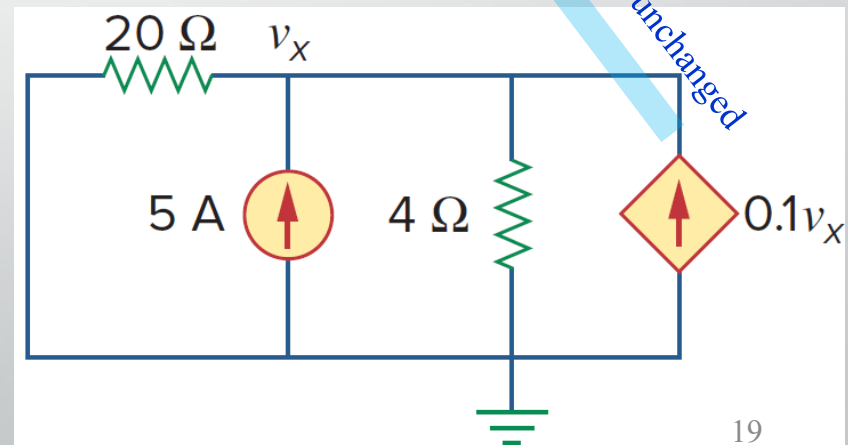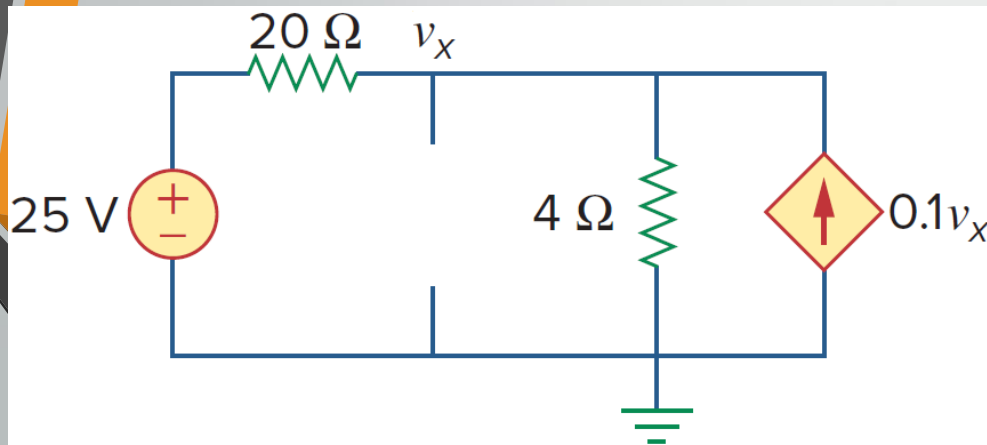

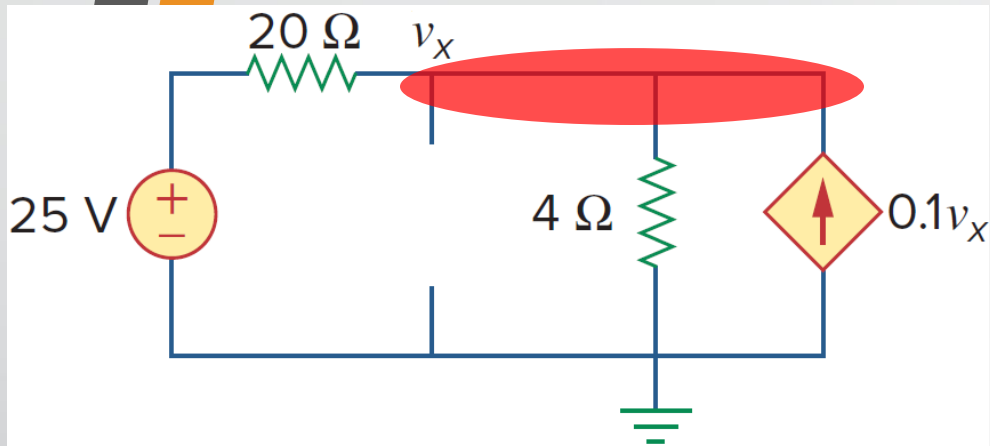
$$v_x = 6.25\text{V} + 25\text{V} = 31.25\text{ V}$$



$$\frac{v_x - 25}{20} + \frac{v_x}{4} = 0.1v_x$$

$$v_x - 25 + 5v_x = 2v_x$$

$$v_x = \frac{25}{4} = 6.25\text{V}$$

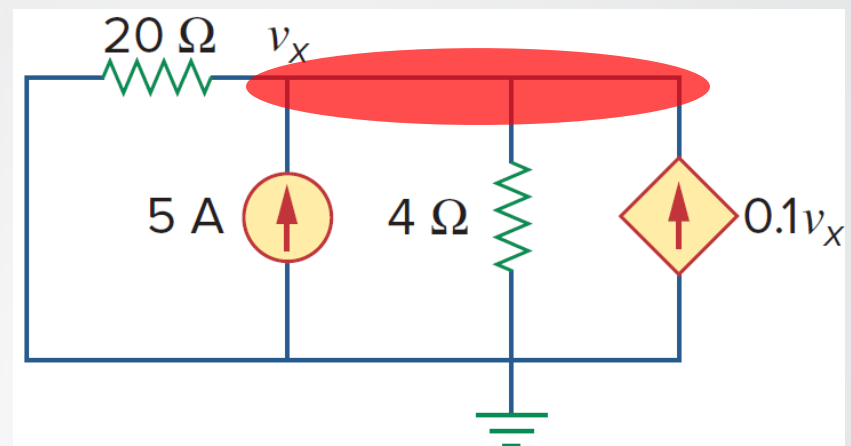

$$\frac{v_x}{20} + \frac{v_x}{4} = 5 + 0.1v_x$$


$$v_x + 5v_x = 100 + 2v_x$$

$$v_x = \frac{100}{4} = 25\text{V}$$

## 4.4 Source Transformation (1)


- An equivalent circuit is one whose  $V$ - $I$  characteristics are identical with the original circuit.
- It is the process of replacing a voltage source  $V_S$  in series with a resistor  $R$  by a current source  $I_S$  in parallel with a resistor  $R$ , or vice versa.

## 4.4 Source Transformation (2)

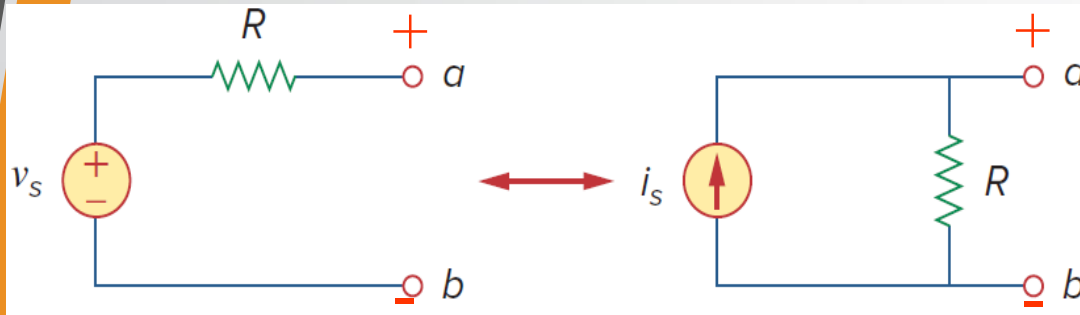

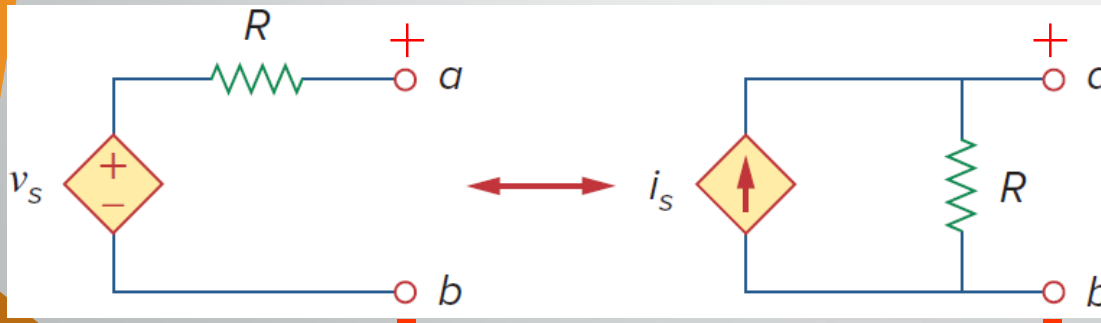(a) Independent source transform

- The arrow of the current source is directed toward the positive (+) terminal of the voltage source.





(b) Dependent source transform

- The transformation is not possible when  $R = 0$  for voltage source and  $R = \infty$  for current source.
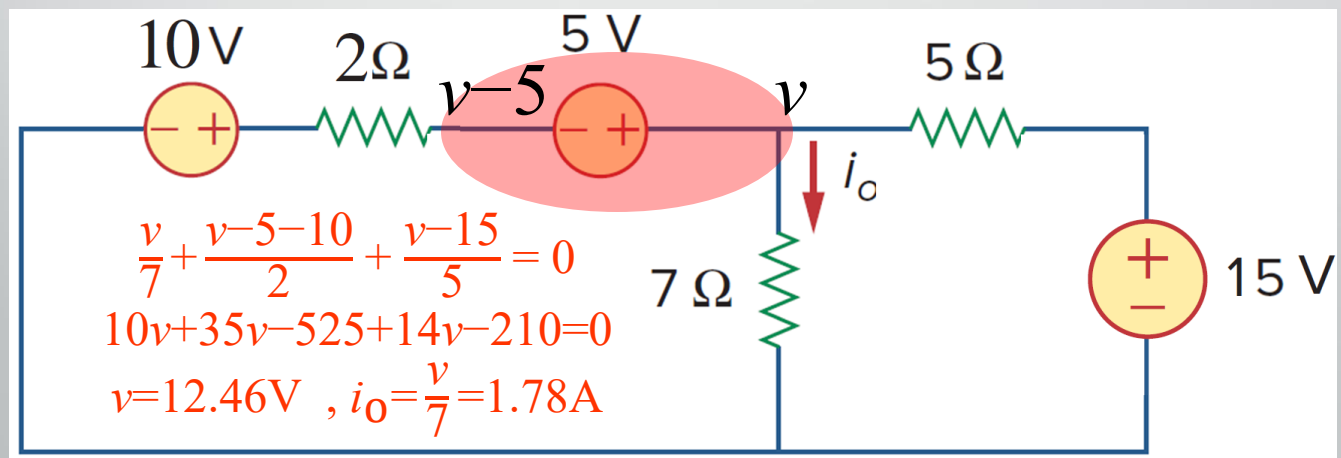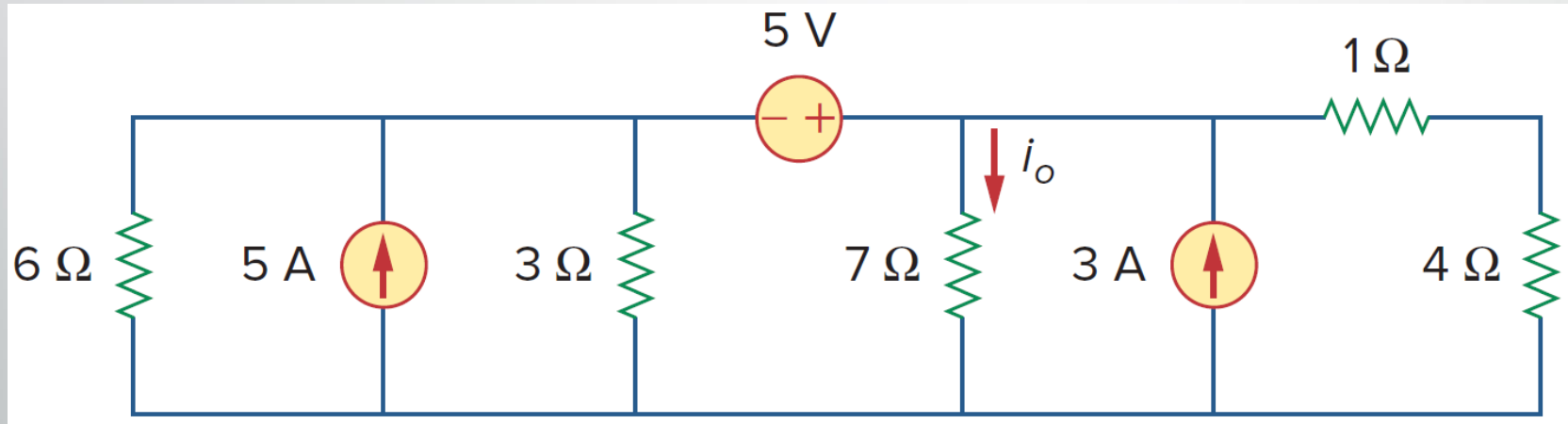
## 4.4 Source Transformation (3)

Ex.9 Find  $i_o$  in the circuit shown below using source transformation.




# 4.5 Thevenin's Theorem (1)

It states that a linear two-terminal circuit (a) can be replaced by an equivalent circuit

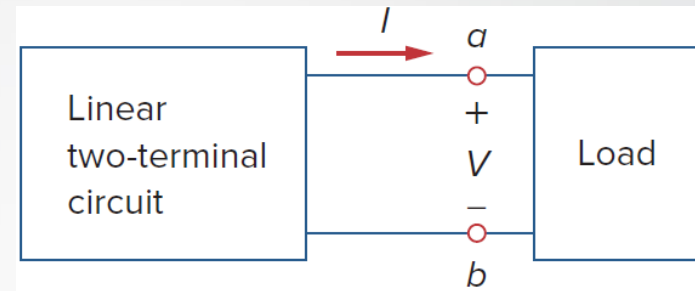
(b) consisting of a voltage source  $V_{Th}$  in series with a resistor  $R_{Th}$

, where

- $V_{Th}$  is the open-circuit voltage at the terminals.
- $R_{Th}$  is the input or equivalent resistance at the terminals when the independent sources are turned off.



(a)

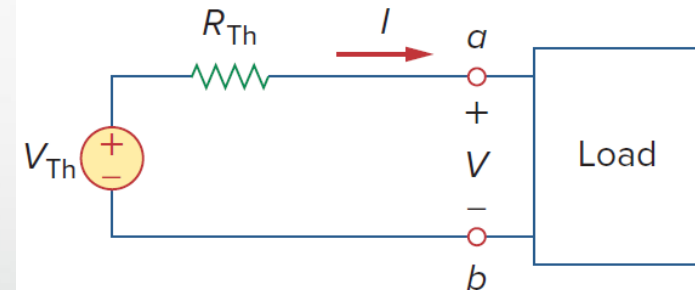


(b)


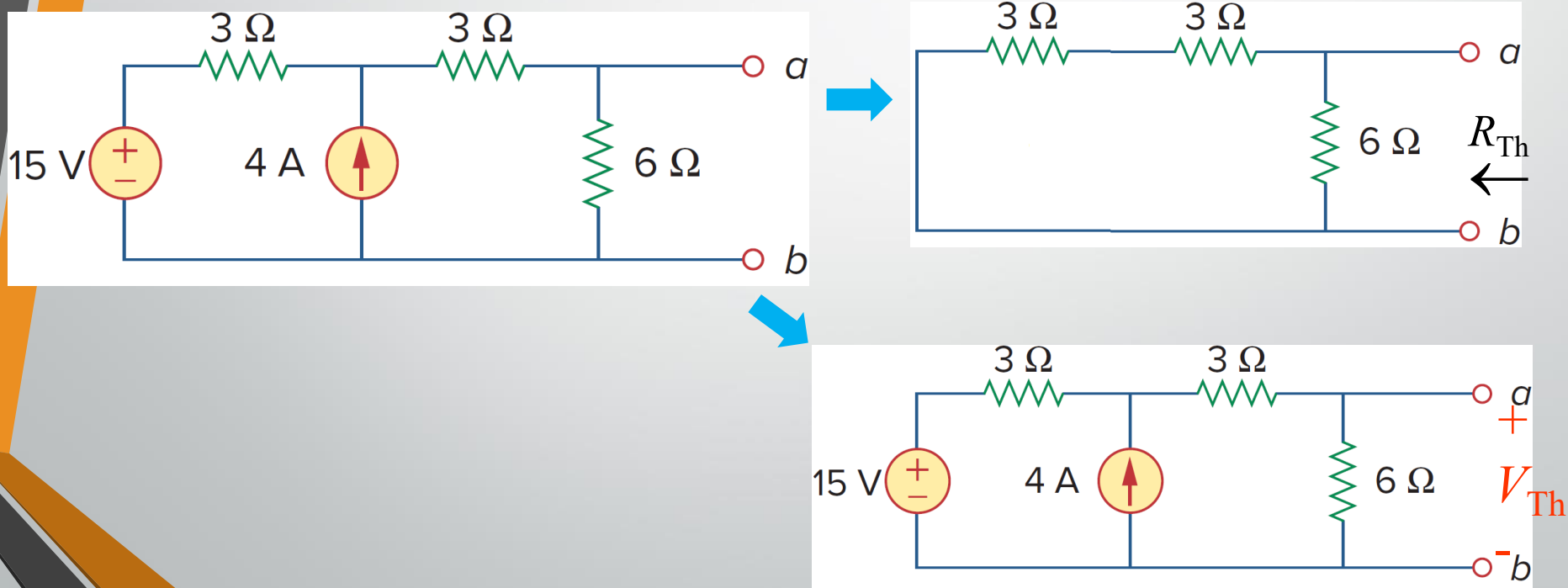
## 4.5 Thevenin's Theorem (2)


Ex.10 Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit shown below.



$$V_{Th} = 13.5V, R_{Th} = 3\Omega$$
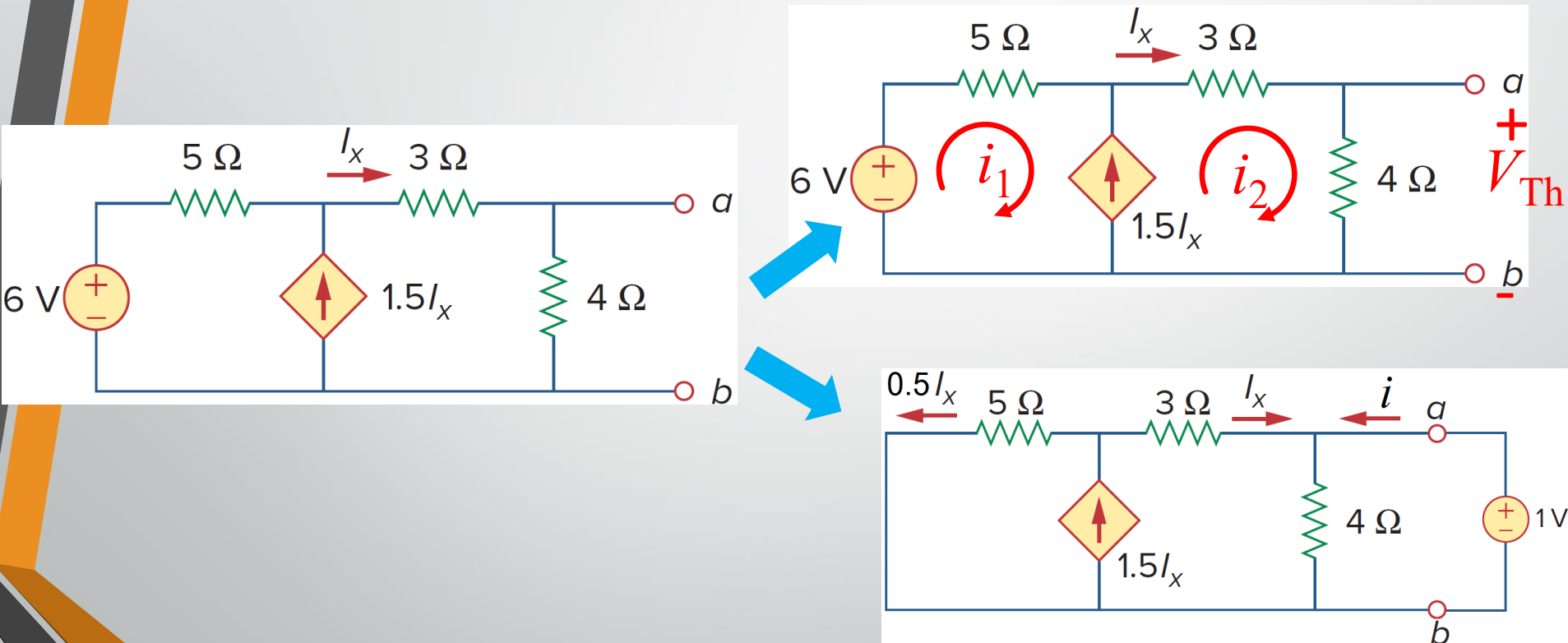
# 4.5 Thevenin's Theorem (3)

Ex.11 Find the Thevenin equivalent circuit of the circuit shown below to the left of the terminals.




$$V_{Th} = 16/3 = 5.333\text{ V}, R_{Th} = 4/9 = 0.444\ \Omega$$

## 4.6 Norton's Theorem (1)


It states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source  $I_N$  in parallel with a resistor  $R_N$ , where

- $I_N$  is the short circuit current through the terminals.
- $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off.

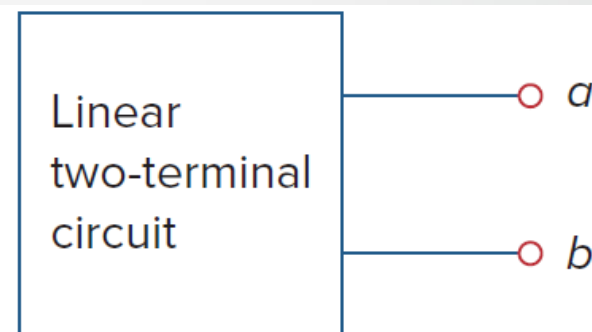
The Thevenin's and Norton equivalent circuits are related by a source transformation



(a) Original circuit

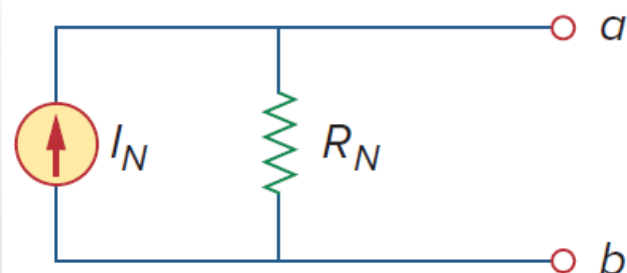



(b) Norton equivalent circuit.

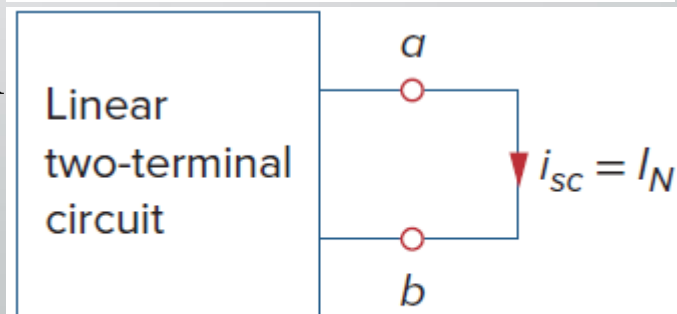

(c) Finding Norton current  $I_N$ .
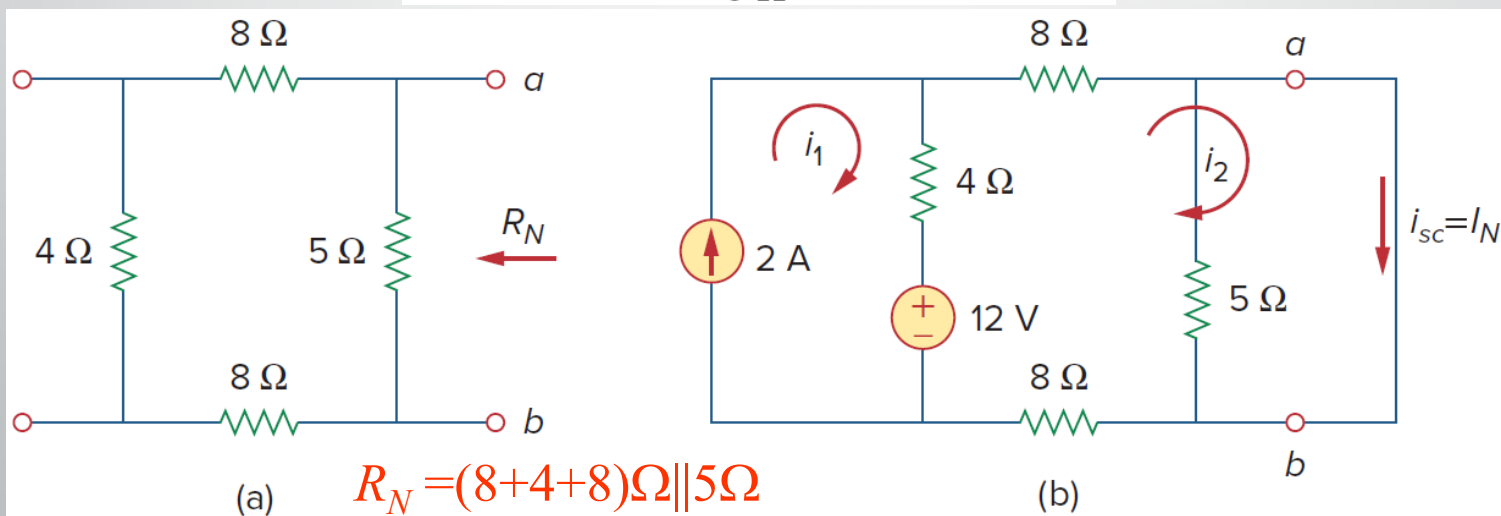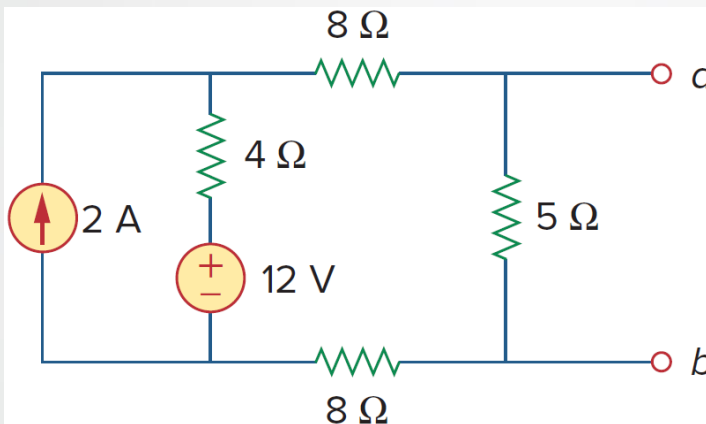
## 4.6 Norton's Theorem (2)

Ex.12 Find the Norton equivalent circuit of the circuit shown below.



$$R_N = 4\Omega, I_N = 1A.$$

# 4.6 Norton's Theorem (3)



Ex.13 Find the Norton equivalent circuit of the circuit shown below.

$$v_x = 1V$$

$$i_1 = 3v_x / 6 = 0.5A$$


$$i = i_1 + v_x / 2 = 1A$$

$$R_N = 1/i = 1\Omega$$

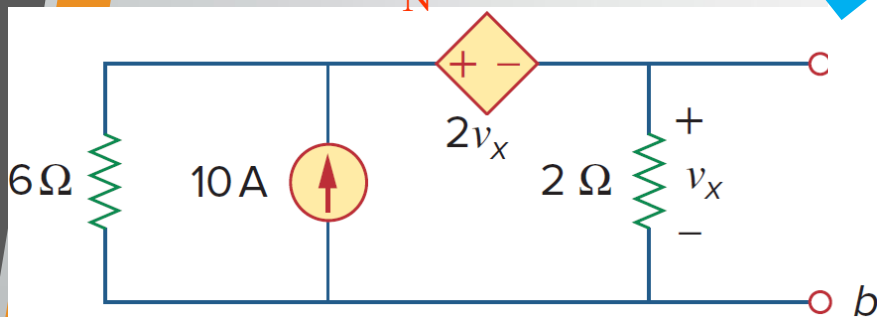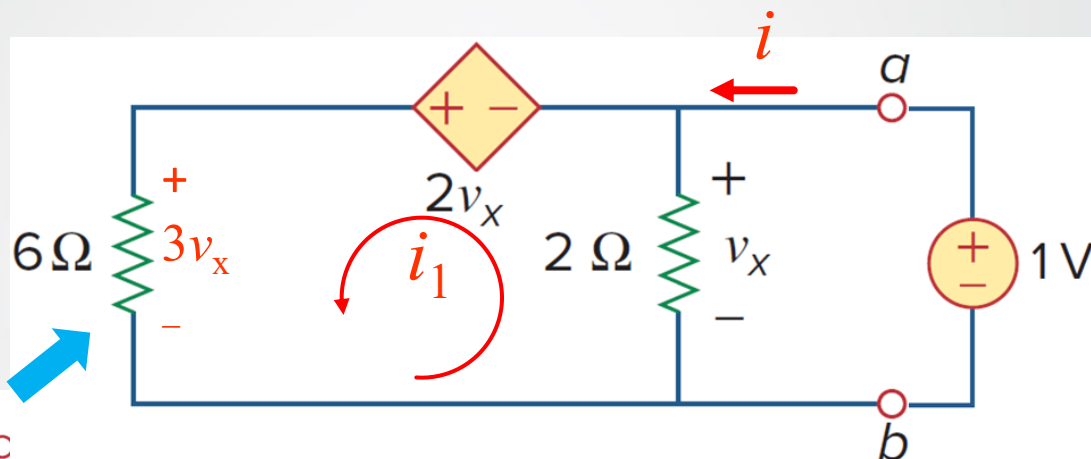


$$v_x = 0V$$


$$I_{sc} = 10A$$

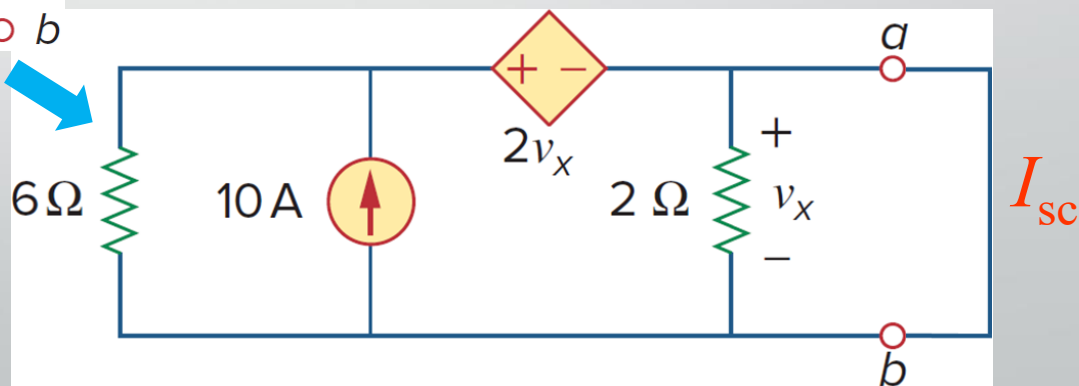

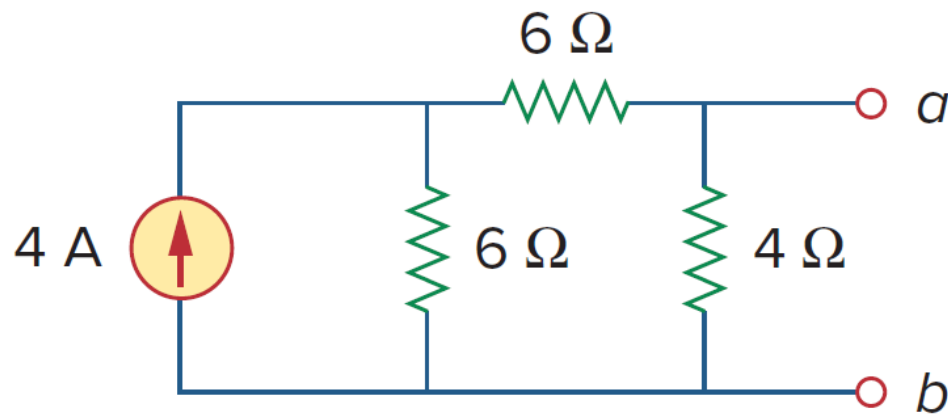**4.45** Find the Thevenin equivalent of the circuit in Fig. 4.112 as seen by looking into terminals  $a$  and  $b$ .



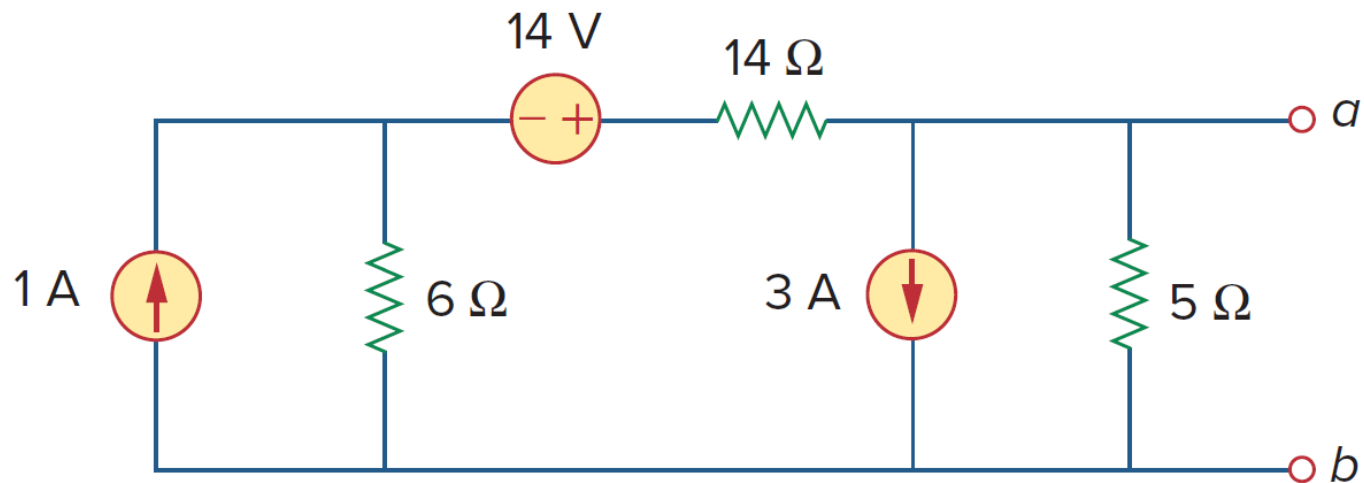**4.41** Find the Thevenin and Norton equivalents at terminals  $a$ - $b$  of the circuit shown in Fig. 4.108.




$4\ \Omega, -8\text{ V}, -2\text{ A}$



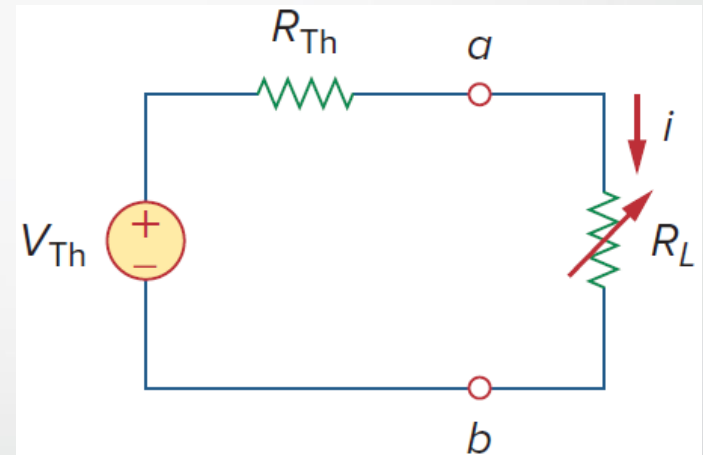
## 4.7 Maximum Power Transfer (1)

**Maximum power** is transferred to the load when the load resistance  $R_L$  equals the Thevenin resistance  $R_{TH}$  as seen from the load ( $R_L = R_{TH}$ ).

$$P = i^2 R_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$


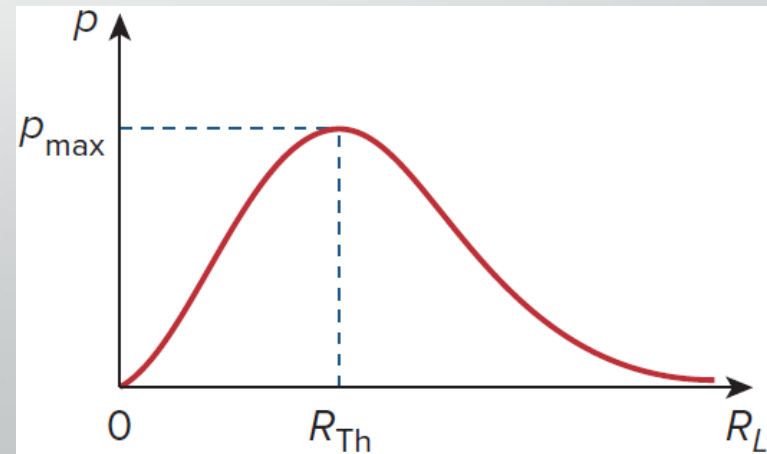
$$R_{TH} = R_L, \quad P_{\max} = \frac{V_{TH}^2}{4R_L}$$



Power delivered to the load as a function of  $R_L$

## 4.7 Maximum Power Transfer (2)

$$P = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$\frac{dP}{dR_L} = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 + 2 \left( \frac{V_{Th}}{R_{Th} + R_L} \right) \left( \frac{-V_{Th}}{(R_{Th} + R_L)^2} \right) R_L = 0$$


$$(R_{Th} + R_L) - 2R_L = 0$$

$$R_{Th} = R_L$$

## 4.7 Maximum Power Transfer (3)
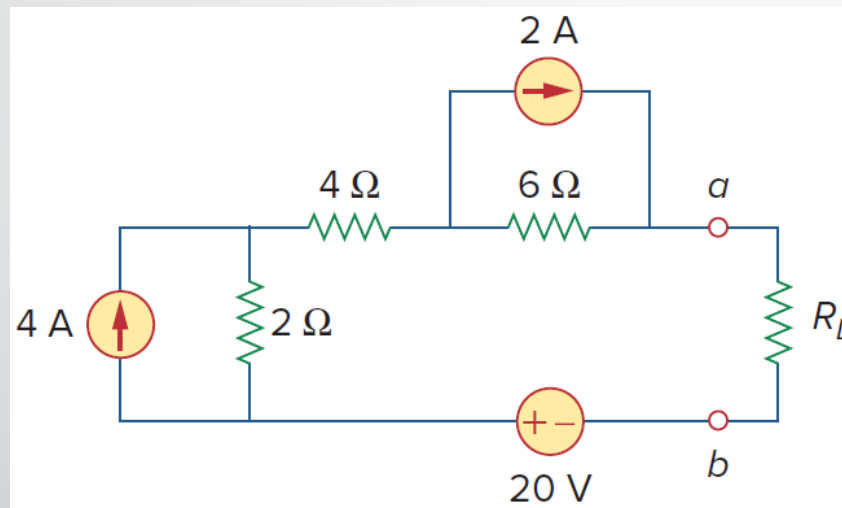
### •Ex.14




- Find  $R_L$  for maximum power deliverable to  $R_L$
- Determine that maximum power.



$$R_L = 12\ \Omega, V_{TH} = 40\text{ V}, P_{max} = 33.33\text{ W}$$

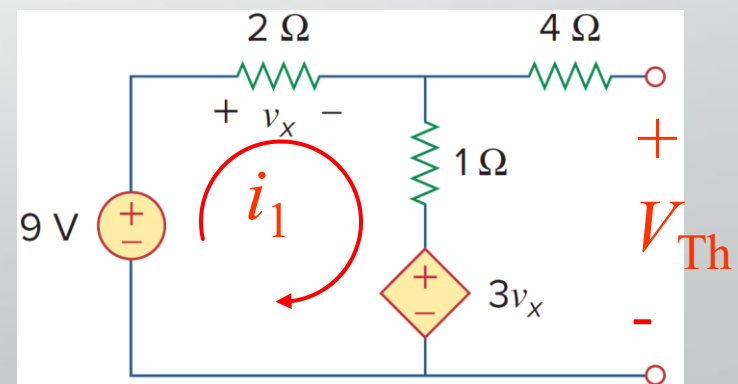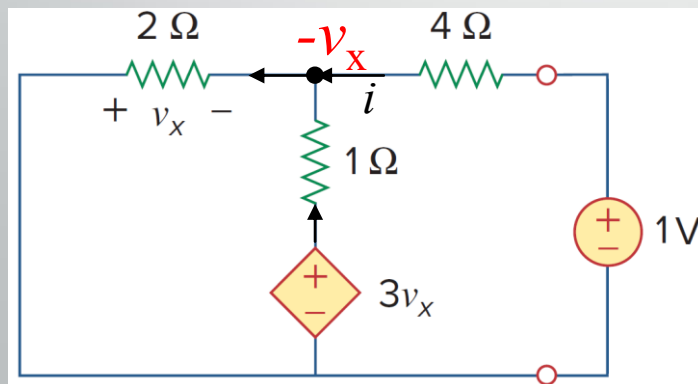
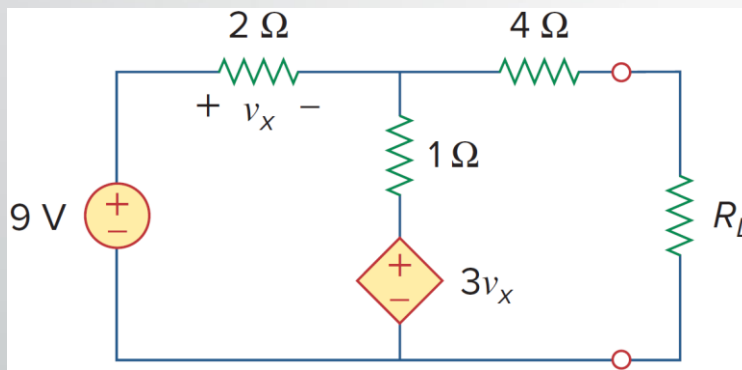
## 4.7 Maximum Power Transfer (4)

Ex.15 Determine the value of  $R_L$  that will draw the maximum power from the rest of the circuit shown below. Calculate the maximum power.



$$R_L = 4.22\Omega, P_m = 2.901\text{W}$$

## 4.7 Maximum Power Transfer (5)

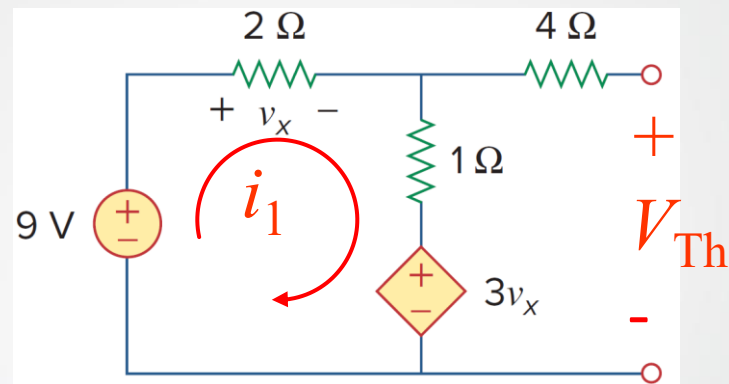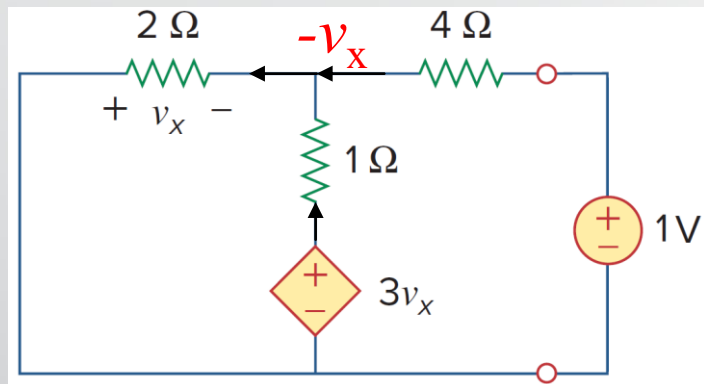

$$i = \frac{1 - (-v_x)}{4} = \frac{1 + v_x}{4}$$

$$\frac{1 + v_x}{4} + \frac{3v_x - (-v_x)}{1} = \frac{-v_x}{2}$$

$$v_x = -\frac{1}{19}, i = \frac{9}{38}, R_{Th} = \frac{38}{9} = 4.22 \Omega$$

$$v_x = 2i_1$$

$$-9 + v_x + 1i_1 + 3v_x = 0$$

$$i_1 = 1 \text{ A}, V_{Th} = 7 \text{ V}$$

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$

$$P_{\max} = 2.901 \text{ W}$$