

$$F = G \frac{m_1 m_2}{d^2}$$

Electrical Engineering 1

12026105

Chapter 7

First-Order Circuits

$$E = mc^2$$

$$ds \geq 0$$

$$\frac{df}{dt} = \lim_{h \rightarrow 0} \frac{f(t+h) - f(t)}{h}$$

$$\frac{1}{\sqrt{2\pi\sigma}} e^{-\frac{(x-\mu)^2}{2\sigma^2}}$$

$$\frac{\partial^2 u}{\partial x^2} = C$$

Learning Objectives

By using the information and exercises in this chapter you will be able to:

1. Understand solutions to unforced, first-order linear differential equations.
2. Comprehend singularity equations and know their importance in solving linear differential equations.
3. Understand the effect of unit step sources on first-order linear differential equations.
4. Explain how dependent sources and op amps influence simple first-order linear differential equations.
5. Use *PSpice* to solve simple transient circuits with an inductor or a capacitor.


First-Order Circuits

3

- 7.1 The Source-Free RC Circuit (วงจร RC ที่ไม่มีแหล่งจ่าย)
- 7.2 The Source-Free RL Circuit (วงจร RL ที่ไม่มีแหล่งจ่าย)
- 7.3 Singularity Functions (Switching Functions)
- 7.4 Step Response of an RC Circuit (วงจร RC ที่มีแหล่งจ่าย)
- 7.5 Step Response of an RL Circuit (วงจร RL ที่มีแหล่งจ่าย)

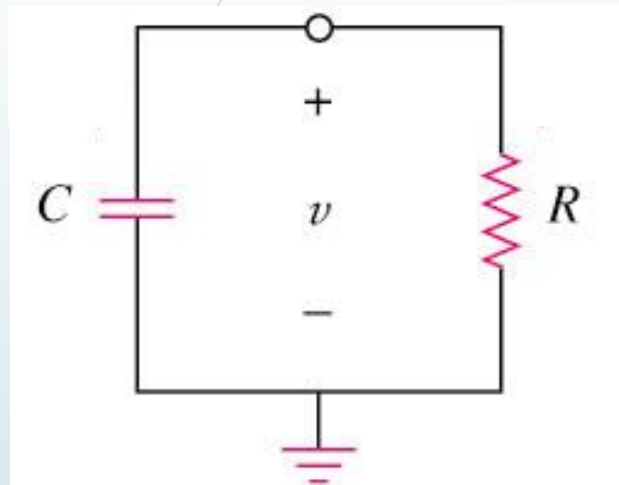7.1 The Source-Free RC Circuit (1)

A first-order circuit is characterized by a first-order differential equation.



By taking KCL at top node

$$i_R + i_C = 0 \rightarrow \frac{v}{R} + C \frac{dv}{dt} = 0$$

Ohms law

Capacitor law

$$\frac{dv}{v} = -\frac{dt}{RC}$$



$$\ln(v) = -\frac{t}{RC} + Cont$$

$$v = e^{\left(-\frac{t}{RC} + Cont\right)} = V_o e^{\left(-\frac{t}{RC}\right)}$$

- Apply Kirchhoff's laws to purely resistive circuit results in algebraic equations.
- Apply the laws to RC and RL circuits produces differential equations.

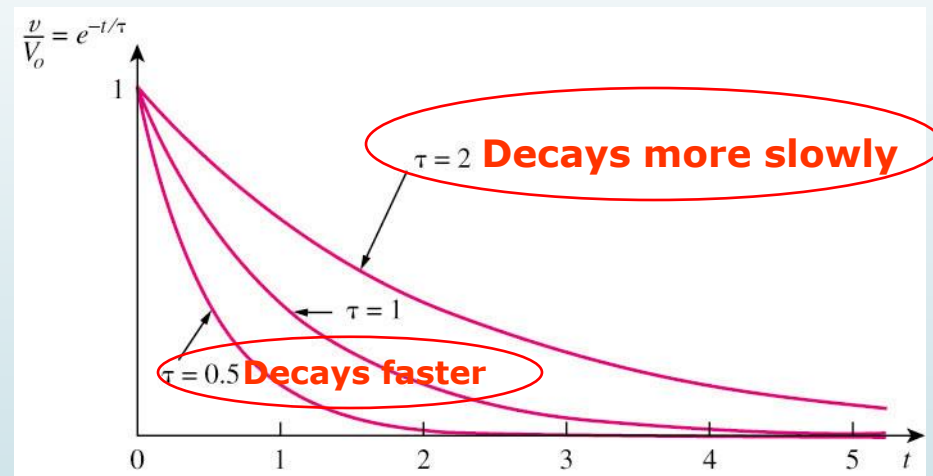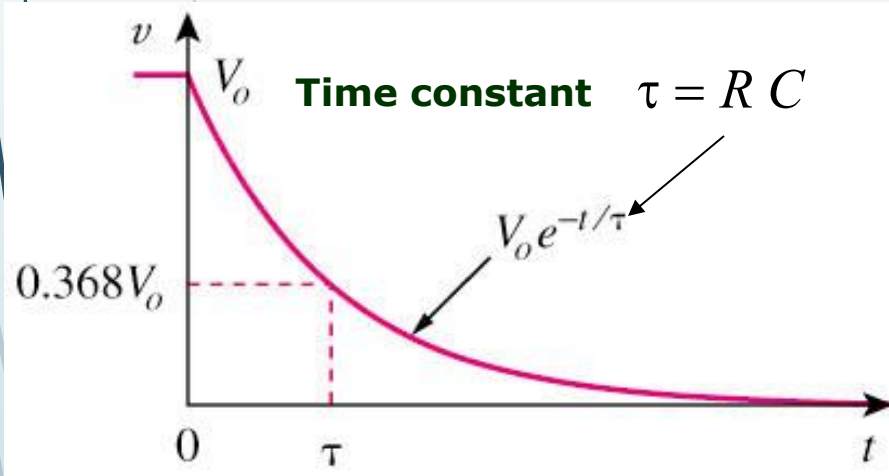7.1 The Source-Free RC Circuit (2)

- The natural response of a circuit refers to the behavior (in terms of voltages and currents) of the circuit itself, with no external sources of excitation.



- The time constant τ of a circuit is the time required for the response to decay by a factor of $1/e$ or 36.8% of its initial value.
- v decays **faster for small τ** and **slower for large τ** .


7.1 The Source-Free RC Circuit (3)

The key to working with a source-free RC circuit is finding:

$$v(t) = V_0 e^{-t/\tau}$$

where


$$\tau = RC$$

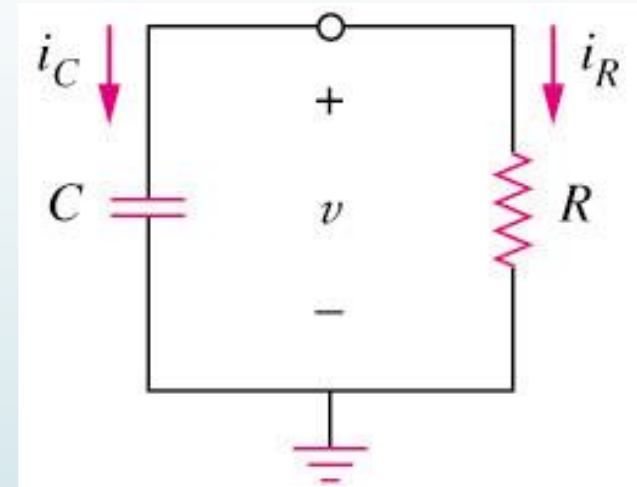

1. The initial voltage $v(0) = V_0$ across the capacitor.
2. $\tau = RC$

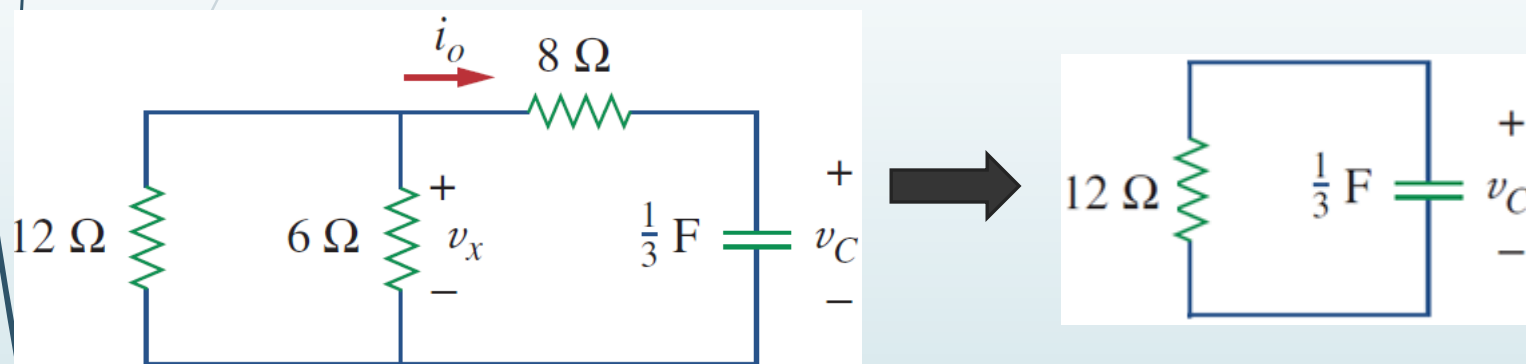7.1 The Source-Free RC Circuit (4)

Ex.1 Refer to the circuit below, determine v_C , v_x , and i_o for $t \geq 0$. Assume that $v_C(0) = 60$ V.



$$v_C(t) = V_o e^{-\frac{t}{\tau}} = 60e^{-\frac{t}{4}}$$


$$i_o(t) = C \frac{dv_C}{dt} = -5e^{-\frac{t}{4}}$$

$$\begin{aligned} v_x(t) &= 8i_o + v_C(t) \\ &= -40e^{-\frac{t}{4}} + 60e^{-\frac{t}{4}} = 20e^{-\frac{t}{4}} \end{aligned}$$



Answer: $v_C = 60e^{-0.25t}$ V ; $v_x = 20e^{-0.25t}$ V ; $i_o = -5e^{-0.25t}$ A

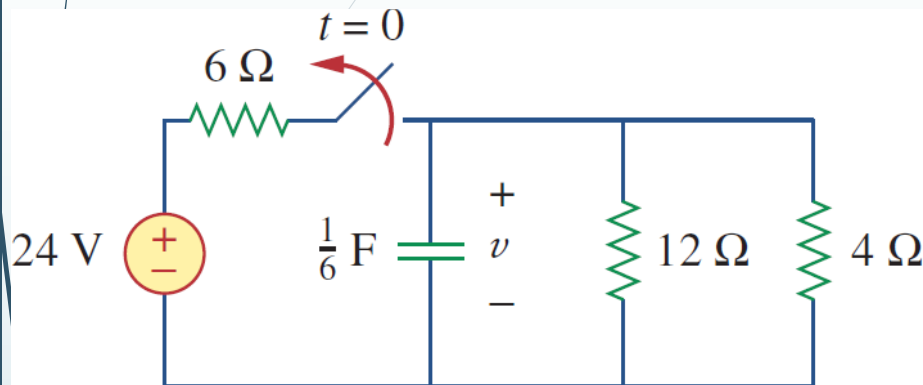7.1 The Source-Free RC Circuit (5)


Ex.2 The switch is opened at $t = 0$, find $v(t)$ for $t \geq 0$.



SW @ $t=0$

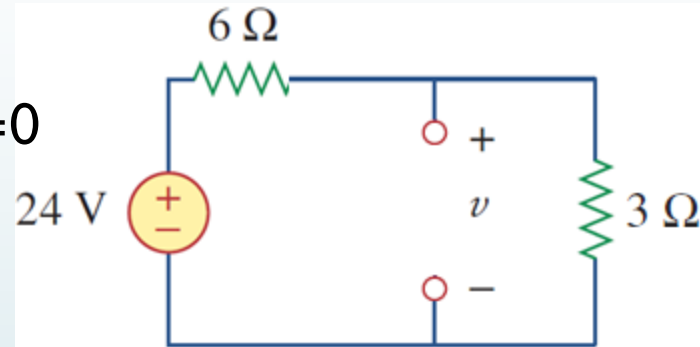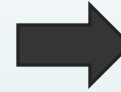

SW @ $t > 0$

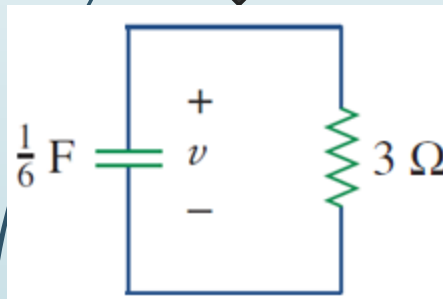


$$v(0) = V_0 = ? \rightarrow v(0) = \left(\frac{3}{3+6} \right) 24 = 8 \text{ V}$$


Answer: $v(t) = 8e^{-2t} \text{ V}$

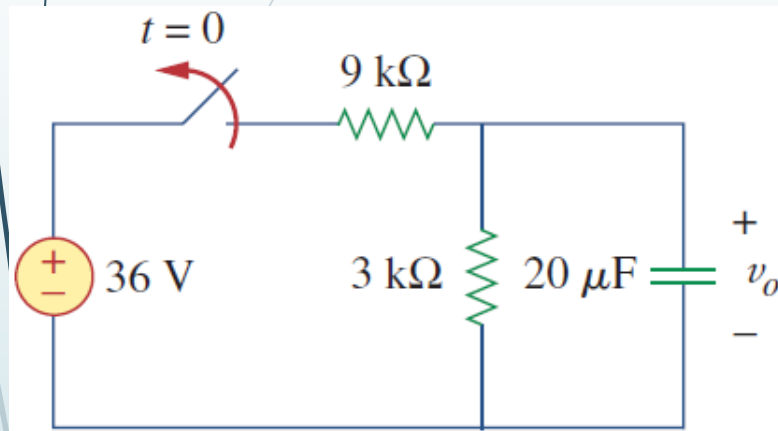7.1 The Source-Free RC Circuit (5)


Ex.3 Find for $v_o(t)$ for $t > 0$. Determine the time for the capacitor voltage to decay to one-third of its value at $t = 0$



SW @ $t = 0$

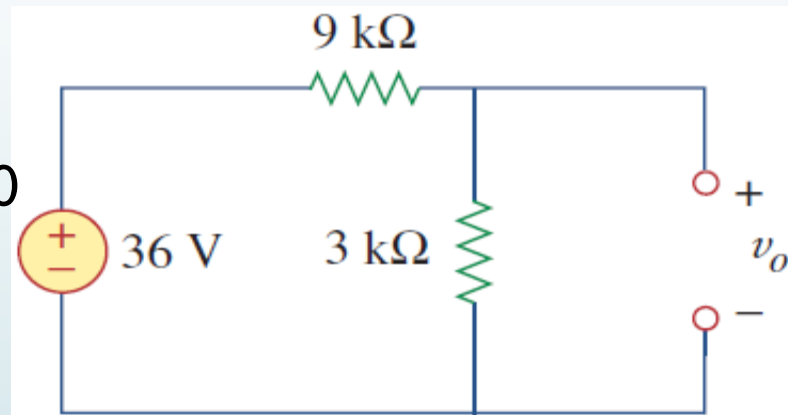

SW @ $t > 0$

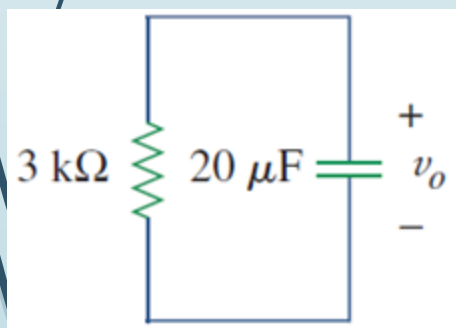

$$v(0) = V_0 = ? \rightarrow v(0) = \left(\frac{3}{3+9} \right) 36 = 9 \text{ V}$$


$$v(t) = 9e^{-t/0.06} \text{ V}$$

$$9/3 = 3 = 9e^{-t/0.06}; t = -0.06 \times \ln(3/9) = 0.066 \text{ s}$$

Answer: $v(t) = 9e^{-t/0.06} \text{ V}; t = 0.066 \text{ s}$

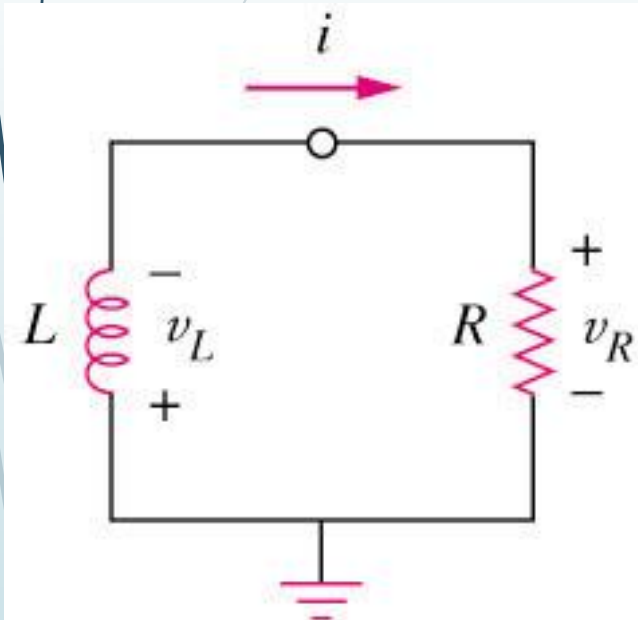7.2 The Source-Free RL Circuit (1)

➡ A first-order RL circuit consists of L and R (or their equivalent)



By KVL

$$v_L + v_R = 0 \rightarrow L \frac{di}{dt} + iR = 0$$


Inductors law

Ohms law

แก้สมการ 1st order
differential eq.

$$\rightarrow \frac{di}{i} = -\frac{R}{L} dt \rightarrow i(t) = I_0 e^{-\left(\frac{R}{L}t\right)}$$

7.2 The Source-Free RL Circuit (2)

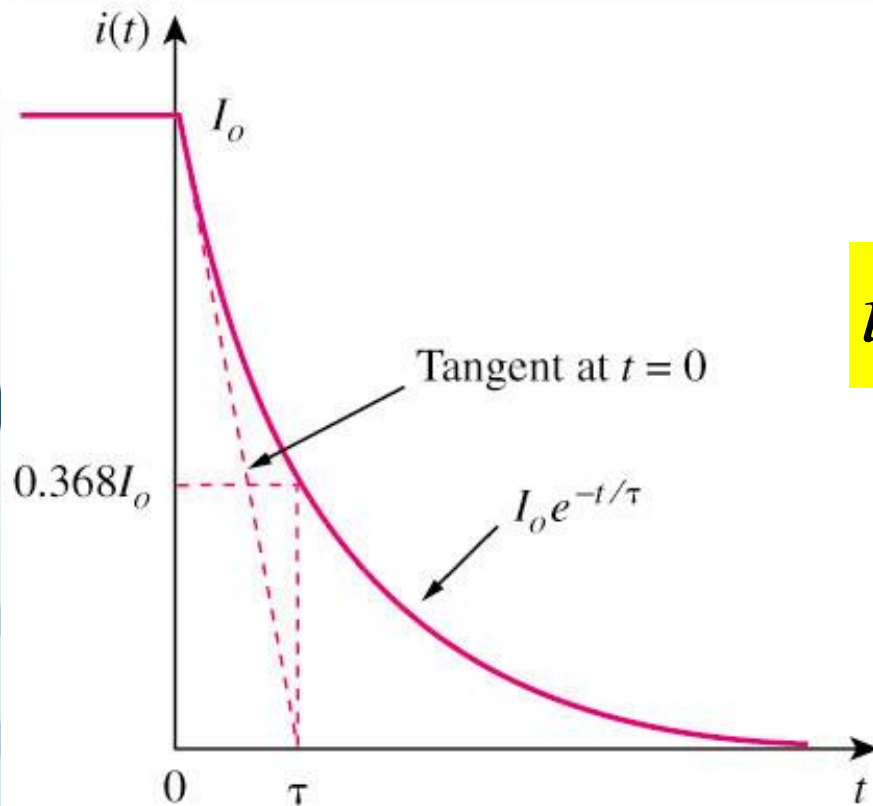

A general form representing RL

$$i(t) = I_0 e^{-t/\tau}$$

where

$$\tau = \frac{L}{R}$$

- The time constant τ of a circuit is the time required for the response to decay by a factor of $1/e$ or 36.8% of its initial value.
- $i(t)$ decays **faster for small t** and **slower for large t** .
- The general form is very similar to a RC source-free circuit.

7.2 The Source-Free RL Circuit (3)

12



Comparison between RL and RC circuit

RL source-free circuit

$$i(t) = I_0 e^{-t/\tau} \quad \text{where} \quad \tau = \frac{L}{R}$$

RC source-free circuit

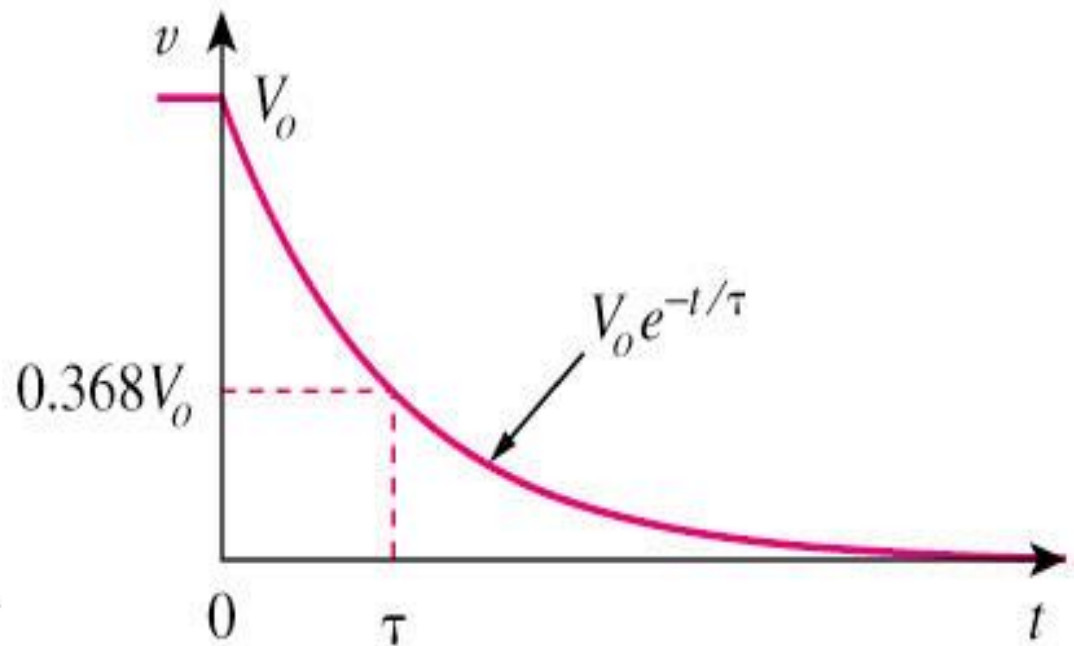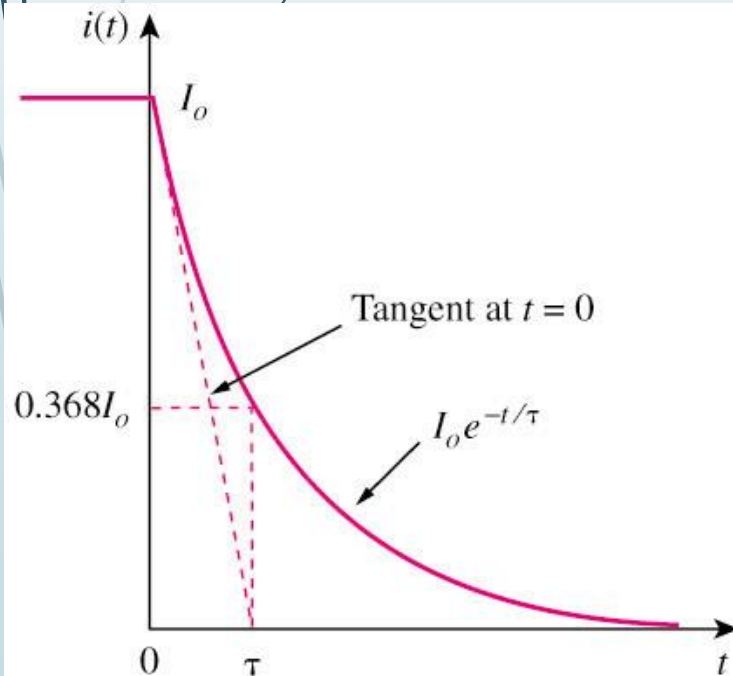
$$v(t) = V_0 e^{-t/\tau} \quad \text{where} \quad \tau = RC$$



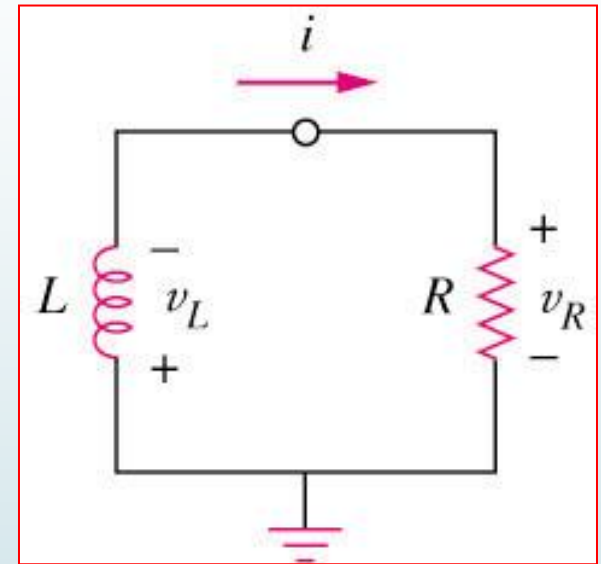7.2 The Source-Free RL Circuit (4)

The key to working with a source-free RL circuit is finding:



$$i(t) = I_0 e^{-t/\tau} \quad \text{where} \quad \tau = \frac{L}{R}$$



1. The initial current $i(0) = I_0$ through the inductor.
2. The time constant $\tau = L/R$.

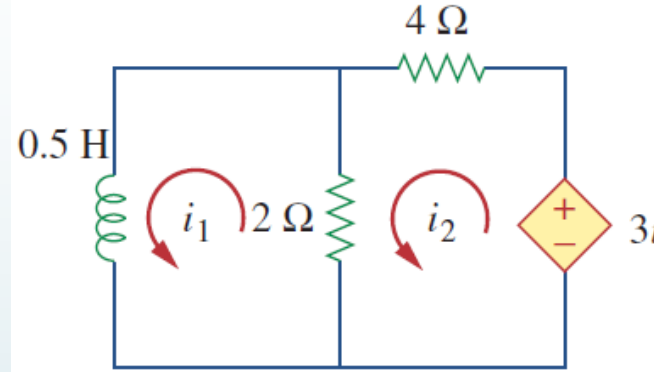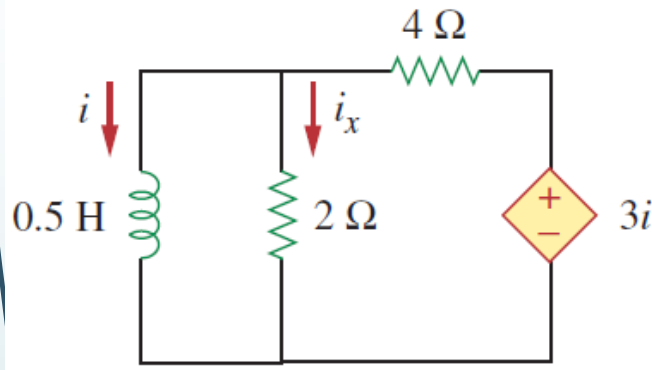7.2 The Source-Free RL Circuit (5)

Ex.4 Assume that $i(0) = 10$ A. Find $i(t)$ and $i_x(t)$.



วิธีที่ 1 ใช้ KVL

$$\text{loop 1, } \frac{1}{2} \frac{di_1}{dt} + 2(i_1 - i_2) = 0$$

$$\text{loop 2, } 6i_2 - 2i_1 - 3i_1 = 0 \Rightarrow i_2 = \frac{5}{6}i_1$$

$$\frac{di_1}{dt} + \frac{2}{3}i_1 = 0$$

Since $i_1 = i$



$$i(t) = i(0)e^{-(2/3)t} = 10e^{-(2/3)t} \text{ A, } t > 0$$

$$i_x(t) = i_2 - i_1 = -1.6667e^{-(2/3)t} \text{ A, } t > 0$$

Answer: $i_x(t) = 10e^{-2t/3} \text{ A}; i_x(t) = -1.6667e^{-2t/3} \text{ A}$

7.2 The Source-Free RL Circuit (5)

วิธีที่ 2 ใช้ R_{eq} และ KVL

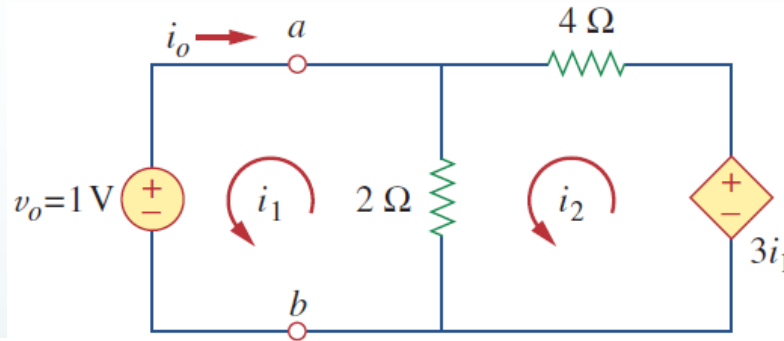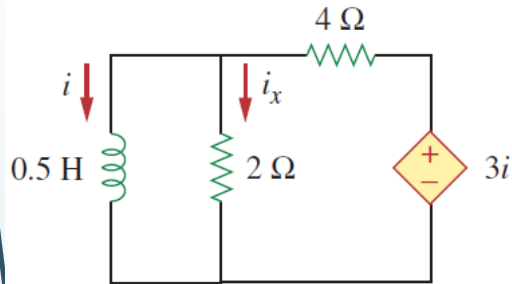

$$2(i_1 - i_2) + 1 = 0 \Rightarrow i_1 - i_2 = -\frac{1}{2}$$

$$6i_2 - 2i_1 - 3i_1 = 0 \Rightarrow i_2 = \frac{5}{6}i_1$$

$$i_1 = -3 \text{ A}, \quad i_o = -i_1 = 3 \text{ A}$$



$$R_{eq} = R_{Th} = \frac{v_o}{i_o} = \frac{1}{3} \Omega \quad \tau = \frac{L}{R_{eq}} = \frac{\frac{1}{2}}{\frac{1}{3}} = \frac{3}{2} \text{ s}$$

$$i(t) = i(0)e^{-(2/3)t} = 10e^{-(2/3)t} \text{ A}, \quad t > 0$$

$$i_x(t) = \frac{v}{2} = -1.6667e^{-(2/3)t} \text{ A}, \quad t > 0$$

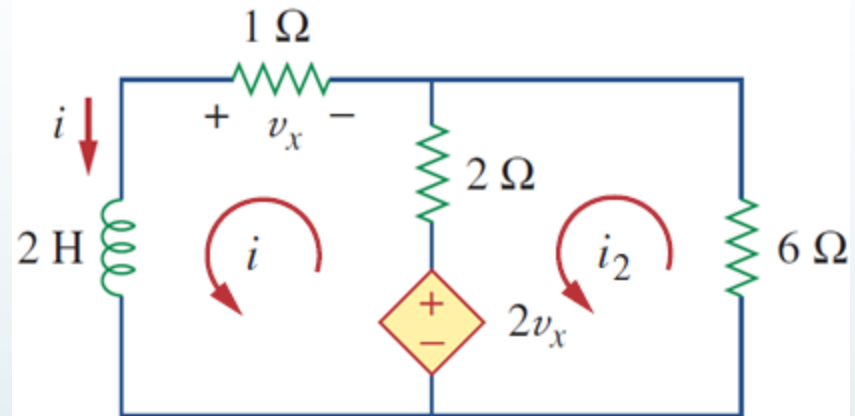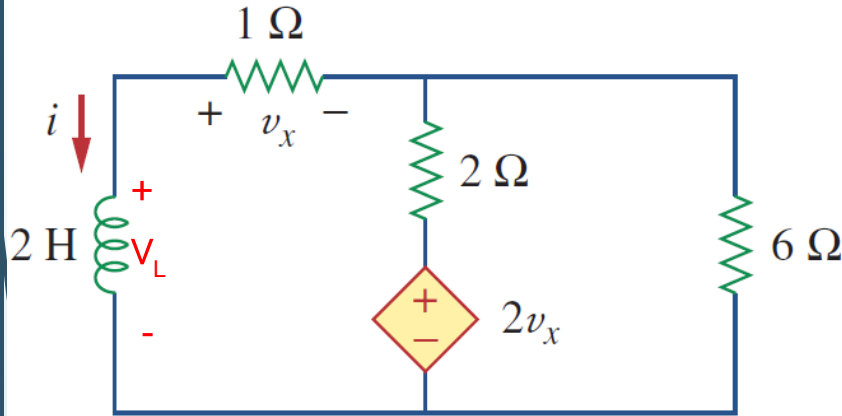7.2 The Source-Free RL Circuit (5)

Ex.5 Find i and v_x . Assume that $i(0) = 12$ A.



$$\text{loop 1, } 2 \frac{di}{dt} + 2(i - i_2) - 3v_x = 0$$

$$v_x = -i$$

$$\text{loop 2, } 8i_2 - 2i + 2v_x = 0 \quad , \quad 8i_2 + 4v_x = 0 \quad , \quad i_2 = -0.5 v_x = 0.5i$$



$$2 \frac{di}{dt} + 2(i - 0.5i) + 3i = 0 \Rightarrow 2 \frac{di}{dt} + 4i = 0 \Rightarrow \frac{di}{dt} + 2i = 0$$

$$\frac{di}{i} = -2dt \Rightarrow \ln(i) = -2t \Rightarrow i = I_o e^{-2t}$$

$$\text{Answer: } i(t) = 12e^{-2t} \text{ A; } v_x(t) = -i(t) = -12e^{-2t} \text{ V}$$

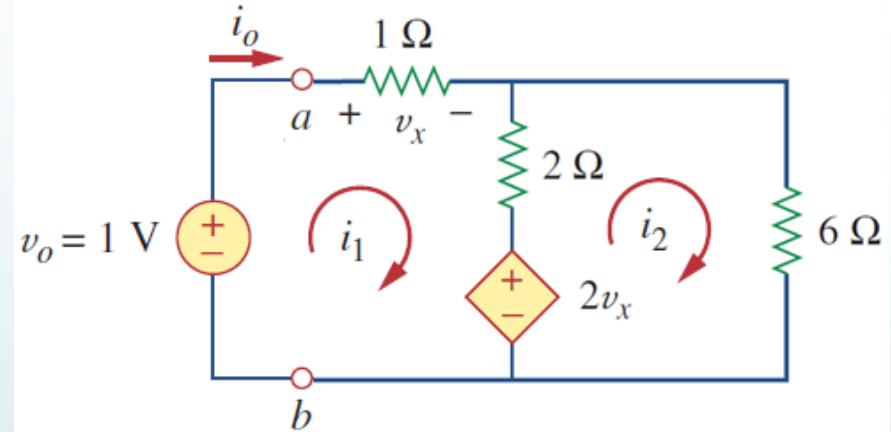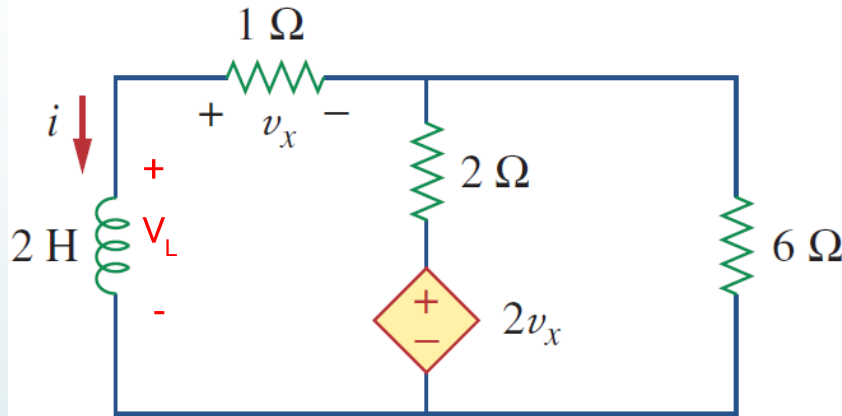7.2 The Source-Free RL Circuit (5)

Ex.5 Find i and v_x . Assume that $i(0) = 12$ A.



$$\text{loop 1, } 3i_1 - 2i_2 + 2i_1 = 5i_1 - 2i_2 = 1$$

$$\text{loop 2, } 2i_1 = -2i_1 + 8i_2 \quad i_1 = 2i_2$$


$$i_2 = \frac{1}{8}, i_1 = \frac{1}{4}$$

$$R_{eq} = \frac{v_o}{i_o} = 4\Omega, \quad \tau = \frac{L}{R_{eq}} = \frac{2}{4} = \frac{1}{2}$$



$$\text{Answer: } i(t) = 12e^{-2t} \text{ A; } v_x(t) = -i(t) = -12e^{-2t} \text{ V}$$

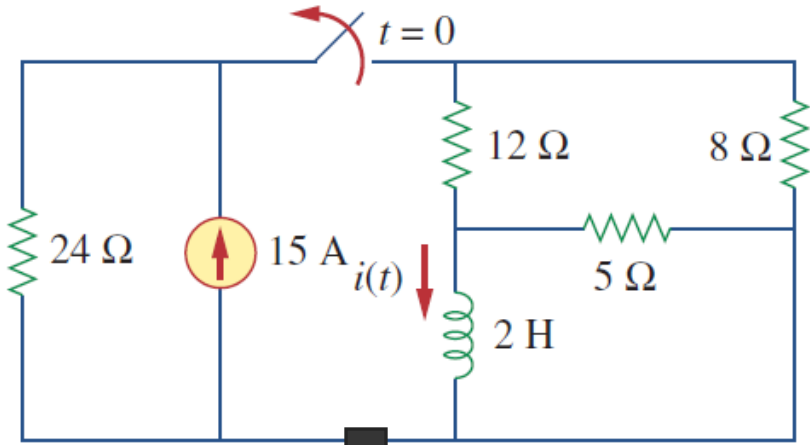7.2 The Source-Free RL Circuit (6)


Ex.6 For the circuit, find $i(t)$ for $t > 0$.



SW @ $t=0$

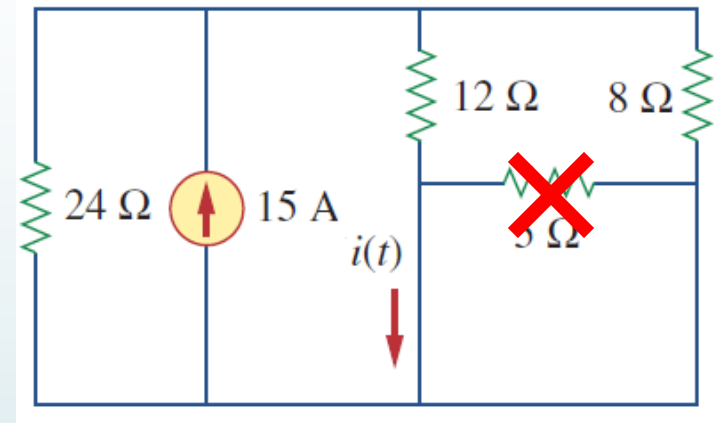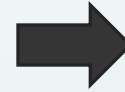

SW @ $t > 0$

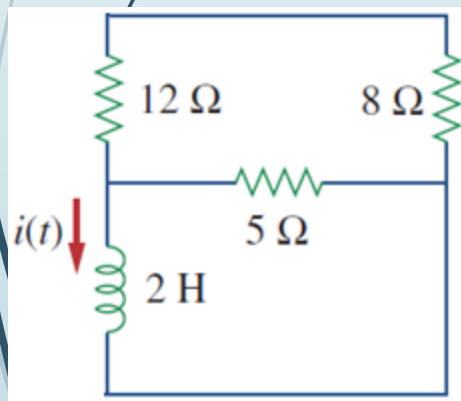

$$i(0) = I_0 = ? \rightarrow i(0) = \left(\frac{24 // 8}{(24 // 8) + 12} \right) 15 = 5 \text{ A}$$

$$R_{eq} = (12 + 8) // 5 = 4$$

Answer: $i(t) = 5e^{-2t} \text{ A}, t > 0$


7.3 Singularity Functions (1)

- **Singularity functions** are functions that either are discontinuous or have discontinuous derivatives.
- 3 most widely used singularity functions in circuit analysis are the **unit impulse $\delta(t)$** , the **unit ramp $r(t)$** , and the **unit step $u(t)$** functions.

7.3 Unit Impulse Function (2)

- The unit impulse function $\delta(t)$ is zero everywhere except at $t = 0$, where it is undefined.
- This may be expressed mathematically as

$$\int_{0^-}^{0^+} \delta(t) dt = 1$$

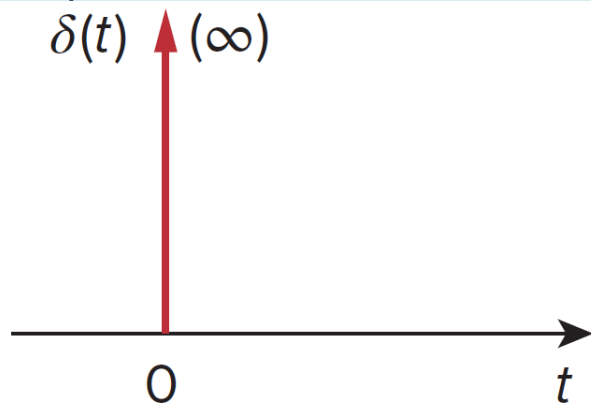


The unit impulse function.

$$\delta(t) = \frac{d}{dt}u(t) = \begin{cases} 0, & t < 0 \\ \text{Undefined}, & t = 0 \\ 0, & t > 0 \end{cases}$$

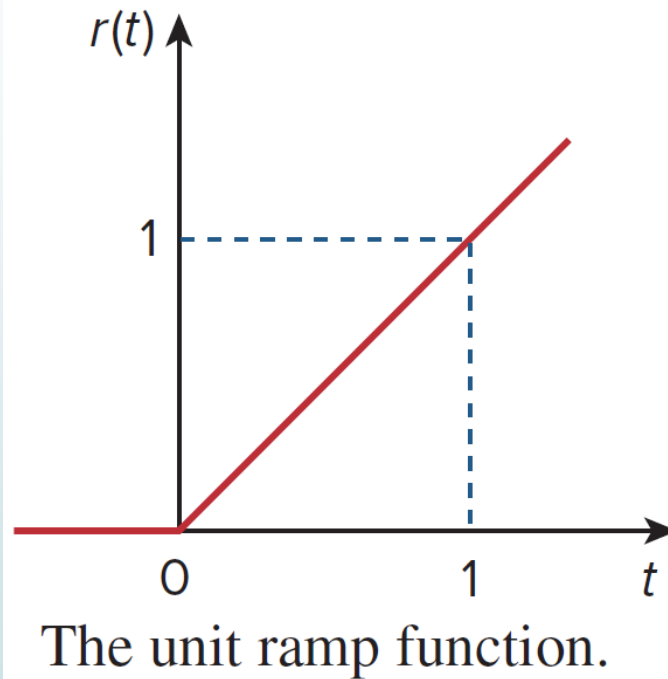7.3 Unit Ramp Function (3)

- The unit ramp function $r(t)$ is zero for negative values of t and has a unit slope for positive values of t .




$$r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t \geq 0 \end{cases}$$

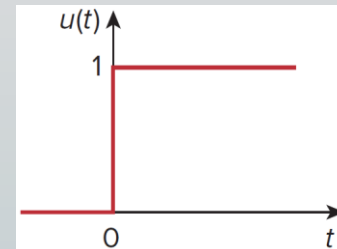
7.3 Unit Step Function (4)

► The unit step function $u(t)$ is 0 for negative values of t and 1 for positive values of t .


$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$


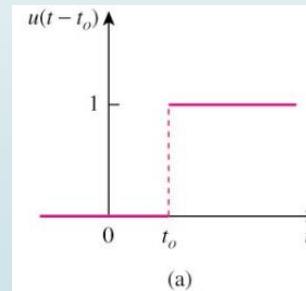
$$u(t - t_o) = \begin{cases} 0, & t < t_o \\ 1, & t > t_o \end{cases}$$



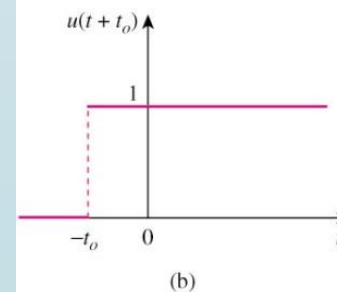
$$u(t + t_o) = \begin{cases} 0, & t < -t_o \\ 1, & t > -t_o \end{cases}$$




7.3 Unit Step Function (5)

Represent an abrupt change for:

1. voltage source:

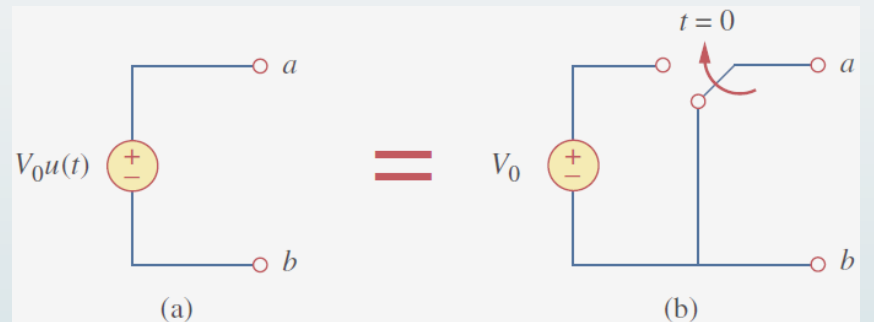


2. current source:

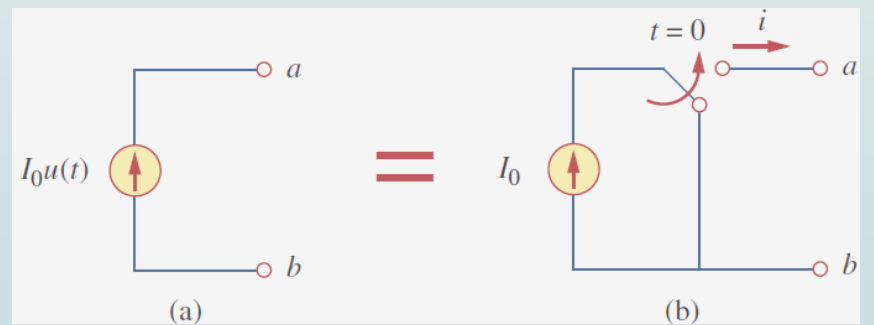

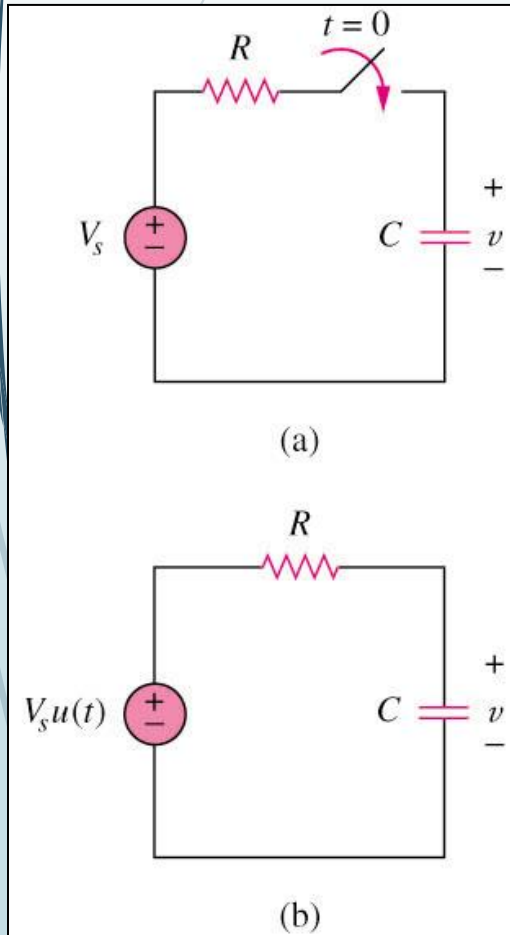7.4 The Step-Response of a RC Circuit (1)

The step response of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.



- Initial condition: $v(0^-) = v(0^+) = V_0$

- Applying KCL, $C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0$

or

$$\frac{dv}{dt} = - \frac{v - V_s u(t)}{RC}$$

- Where $u(t)$ is the unit-step function

$$\int \frac{dv}{v - V_s} = - \int \frac{dt}{RC}$$

$$\ln(v - V_s) \Big|_{V_0}^{v(t)} = - \frac{t}{RC} \Big|_0^t$$

7.4 The Step-Response of a RC Circuit (1)

$$\ln(v - V_s) \Big|_{V_0}^{v(t)} = - \frac{t}{RC} \Big|_0^t$$

$$\ln(v(t) - V_s) - \ln(V_0 - V_s) = - \frac{t}{RC}$$

$$\ln\left(\frac{v(t) - V_s}{V_0 - V_s}\right) = - \frac{t}{RC}$$


$$\frac{v(t) - V_s}{V_0 - V_s} = e^{-\frac{t}{RC}}$$

$$v(t) = V_s + (V_0 - V_s)e^{-\frac{t}{RC}}$$

$$v(t) = v(\infty) + (v(0) - v(\infty))e^{-\frac{t}{\tau}}$$

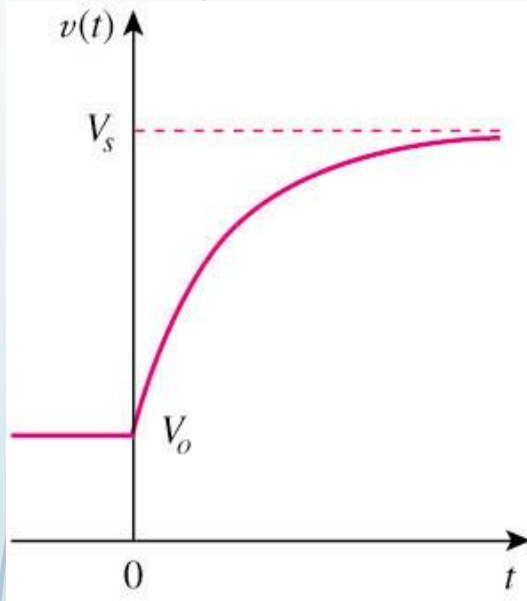7.4 The Step-Response of a RC Circuit (2)

- Integrating both sides and considering the initial conditions, the solution of the equation is:



$$v(t) = \begin{cases} V_o & t < 0 \\ V_s + (V_o - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

Steady-state Response (permanent part) Transient Response (temporary part)

Final value at $t \rightarrow \infty$ Initial value at $t = 0$ Source-free Response

Complete Response = Natural response + Forced Response
 (stored energy) (independent source)
 (เกิดจาก no source) (เกิดจาก source)

$$V_o e^{-t/\tau} + V_s (1 - e^{-t/\tau})$$

7.4 The Step-Response of a RC Circuit (3)

3 steps to find out the **step response of an RC circuit**:


1. Initial capacitor voltage $v(0)$.
2. Final capacitor voltage $v(\infty)$ — DC voltage across C.
3. Time constant τ .

$$v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-t/\tau}$$

Note: The above method is a **short-cut method**. You may also determine the solution by setting up the circuit formula directly using KCL, KVL, ohms law, capacitor and inductor VI laws.

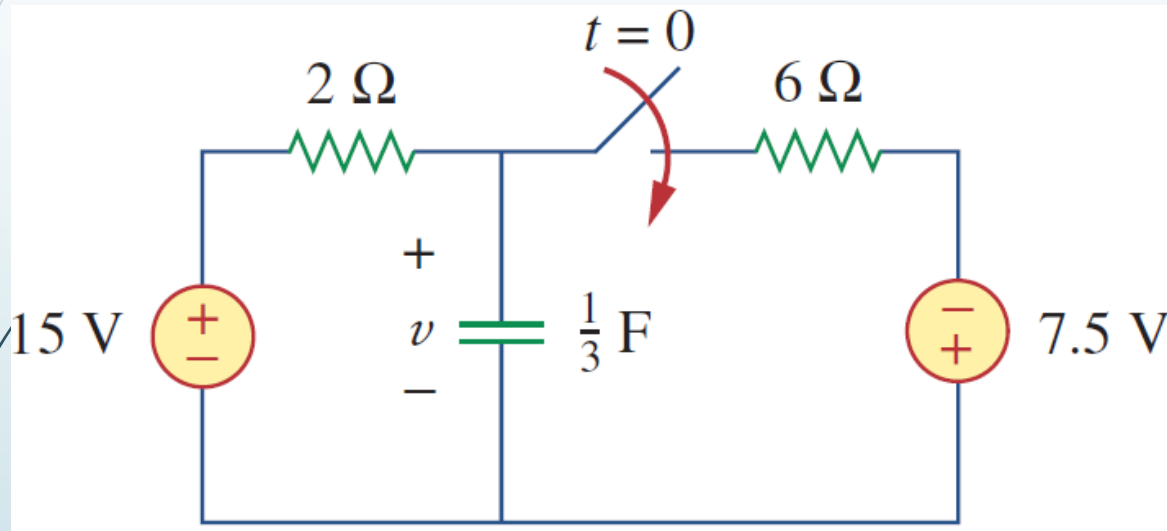
7.4 The Step-Response of a RC Circuit (4)

Ex.7 Find $v(t)$ for $t > 0$ in the circuit in below. Assume the switch has been open for a long time and is closed at $t = 0$. Calculate $v(t)$ at $t = 0.5$.



Answer: $v(t) = (5.625e^{-2t} + 9.375)V$ for $t > 0$, $v(0.5) = 11.44 V$

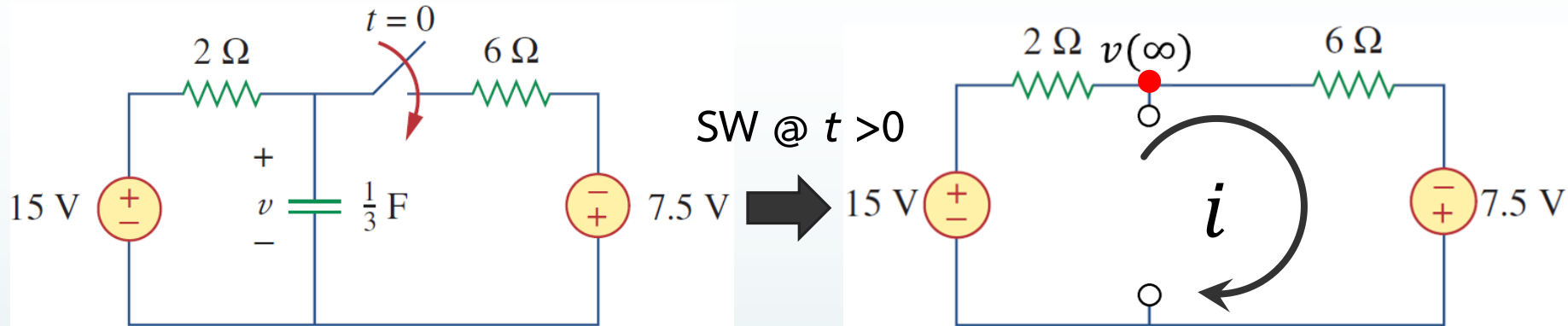7.4 The Step-Response of a RC Circuit (5)



$$v(t) = v(\infty) + [v(0^+) - v(\infty)]e^{-t/\tau}$$

$$v(0^-) = v(0^+) = 15\text{ Volts}$$

$$i = \frac{15 + 7.5}{6 + 2} = 2.8125\text{ A,}$$


$$v(\infty) = 15 - (2.8125 \times 2) = 9.375\text{ Volts}$$

$$R = 2 // 6 = \frac{3}{2}\ \Omega, \quad C = \frac{1}{3}, \quad RC = \frac{1}{2} \quad -\frac{t}{\tau} = -\frac{t}{RC} = -2t$$

Answer: $v(t) = (5.625e^{-2t} + 9.375)V$ เมื่อ $t > 0$, $v(0.5) = 11.44\text{ V}$ 29

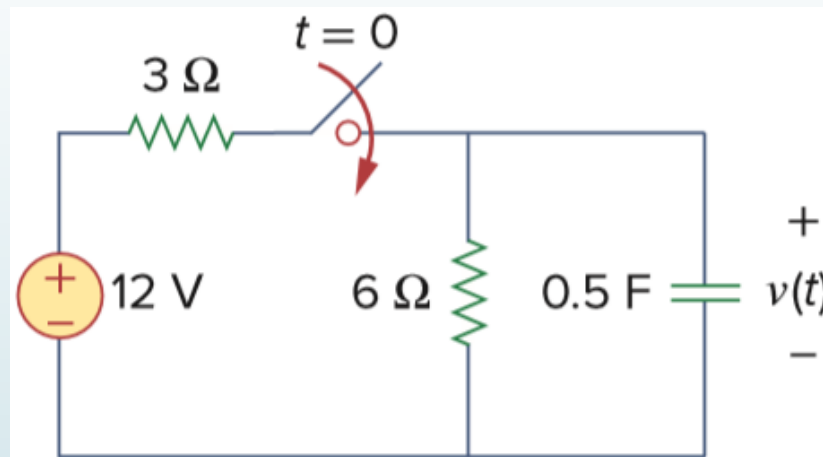7.4 The Step-Response of a RC Circuit (6)

Ex.8 Find $v(t)$ for $t > 0$ in the circuit in below. Assume the switch has been open for a long time and is closed at $t = 0$.





$$v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-t/\tau}$$

$$v(t) = \left(\frac{6}{3+6} \right) 12 + \left[0 - \left(\frac{6}{3+6} \right) 12 \right] e^{-t/\tau}$$



Answer : $v(t) = 8(1 - e^{-t}) \text{ V}, t > 0.$

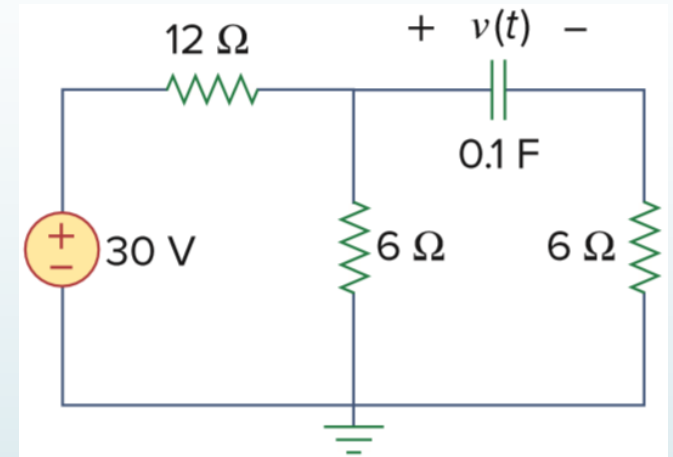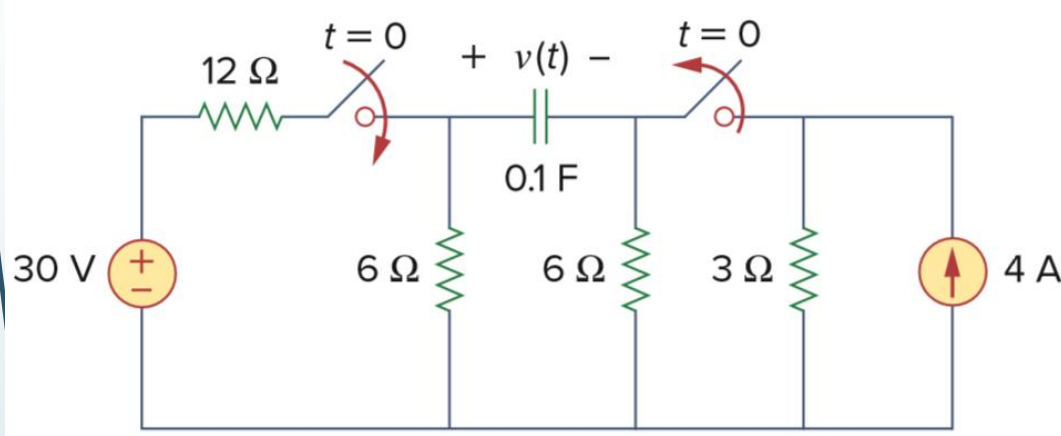7.4 The Step-Response of a RC Circuit (7)

Ex.9 Find $v(t)$ for $t > 0$ in the circuit in below.




เริ่มต้นหา $v(0^-)$

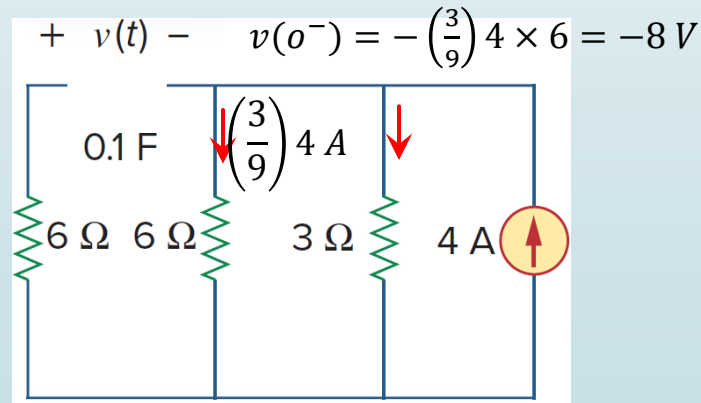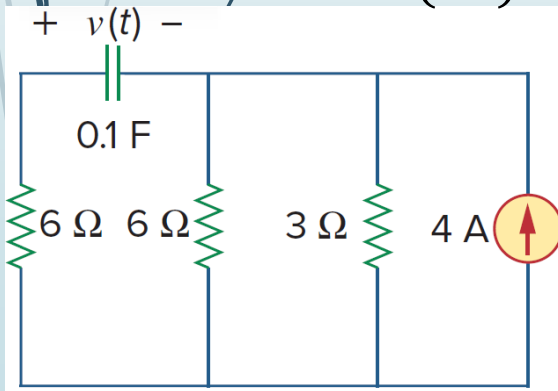


Answer : $v(t) = 10 - 18e^{-t} \text{ V}$

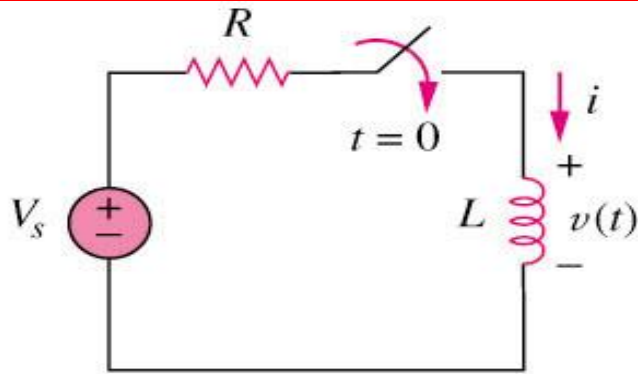7.5 The Step-response of a RL Circuit (1)

The step response of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.



(a)

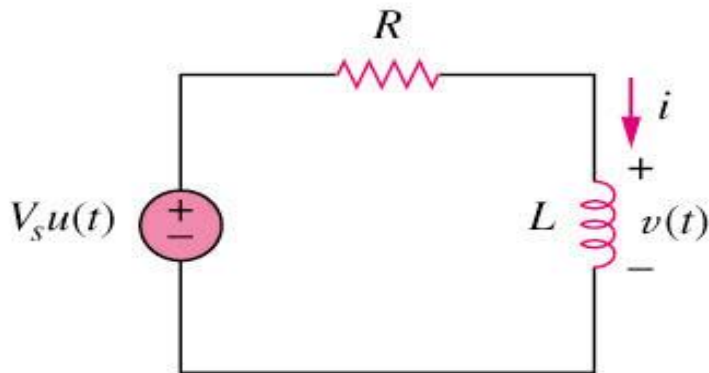

(b)

- Initial current $i(0^-) = i(0^+) = I_0$

- Final inductor current

$$i(\infty) = V_s / R$$

- Time constant $\tau = L / R$

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-\frac{t}{\tau}}$$

$$i(t) = i(\infty) + \left(i(0^+) - i(\infty) \right) e^{-\frac{t}{\tau}}$$

7.5 The Step-Response of a RL Circuit (2)

3 steps to find out the step response of an RL circuit:


1. Initial inductor current $i(0)$ at $t = 0^+$.
2. Final inductor current $i(\infty)$.
3. Time constant τ .

$$i(t) = i(\infty) + [i(0+) - i(\infty)] e^{-t/\tau}$$

Note: The above method is a short-cut method. You may also determine the solution by setting up the circuit formula directly using KCL, KVL, ohms law, capacitor and inductor VI laws.

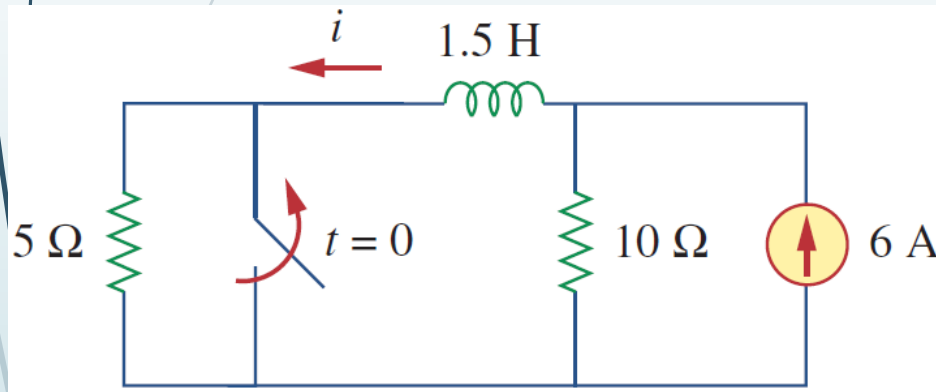7.5 The Step-Response of a RL Circuit (3)

Ex.10 The switch in the circuit shown below has been closed for a long time. It opens at $t = 0$. Find $i(t)$ for $t > 0$.



$$i(0) = \left(\frac{10}{10+0} \right) 6 = 6 \text{ A}$$

$$i(\infty) = \left(\frac{10}{5+10} \right) 6 = 4 \text{ A}$$


$$R_{eq} = 5 + 10 = 15 \Omega \quad ; \quad \tau = \left(\frac{L}{R_{eq}} \right) = \frac{1.5}{15} = \frac{1}{10}$$

$$i(t) = i(\infty) + [i(0+) - i(\infty)] e^{-t/\tau} = 4 + (6 - 4)e^{-10t} = 4 + 2e^{-10t}$$

Answer: $i(t) = 4 + 2e^{-10t}$

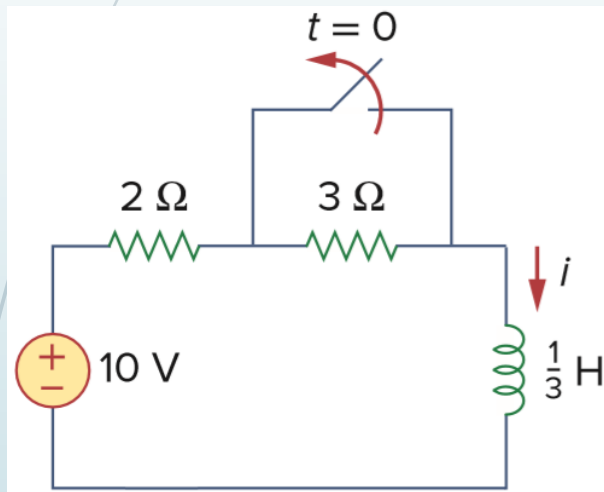7.5 The Step-Response of a RL Circuit (4)

Ex.11 The switch in the circuit shown below has been closed for a long time. It opens at $t = 0$. Find $i(t)$ for $t > 0$.



$$i(0^-) = \frac{10}{2} = 5\text{ A}$$

$$i(\infty) = \frac{10}{2 + 3} = 2\text{ A}$$

$$R_{\text{Th}} = 2 + 3 = 5\Omega$$

$$\tau = \frac{L}{R_{\text{Th}}} = \frac{\frac{1}{3}}{5} = \frac{1}{15}\text{ s}$$


$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$= 2 + (5 - 2)e^{-15t} = 2 + 3e^{-15t}\text{ A,}$$

Answer: $i(t) = 2 + 3e^{-15t}\text{ A}$

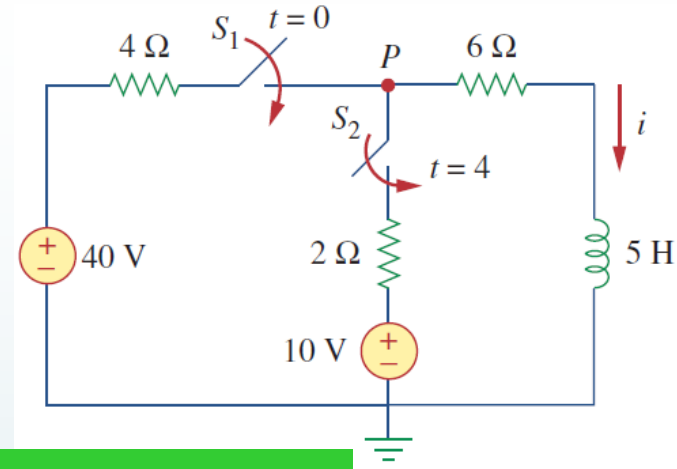7.5 The Step-Response of a RL Circuit (5)

Ex.12 At $t=0$, S_1 is closed and S_2 is closed 4s later. Find $i(t)$ for $t=0$. Calculate i for $t=2s$ and $t=5s$.



แบ่งเป็น 3 ช่วง : $t < 0$, $0 \leq t \leq 4$, $t > 4$

ช่วงที่ 1: $t < 0$: $i(0^-) = i(0^+) = 0$

ช่วงที่ 2: $0 \leq t \leq 4$: $i(4) = \frac{40}{4+6} = 4$, $R_{eq} = 10\Omega$ $\tau = \frac{L}{R_{eq}} = \frac{1}{2}s$

$$i(t) = i(4) + [i(0^+) - i(4)]e^{-t/\tau} = 4 + (0 - 4)e^{-2t} = 4(1 - e^{-2t})$$

ช่วงที่ 3: $t > 4$: $i(4) = i(4^-) = 4(1 - e^{-8}) \approx 4A$

KCL at node P :
$$\frac{40 - v}{4} + \frac{10 - v}{2} = \frac{v}{6} \rightarrow v = \frac{180}{11}$$

$$i(\infty) = \frac{v}{6} = \frac{30}{11} = 2.727A, R_{eq} = (4 // 2) + 6 = \frac{22}{3}\Omega \quad \tau = \frac{L}{R_{eq}} = \frac{15}{22}s$$

$$i(t) = i(\infty) + [i(4) - i(\infty)]e^{-(t-4)/\tau} = 2.727 + (4 - 2.727)e^{-(t-4)/\tau} = 2.727 + 1.273e^{-1.4667(t-4)}$$

Answer: $i(2) = 4(1 - e^{-4}) = 3.93A$, $i(5) = 2.727 + 1.273e^{-1.4667} = 3.02A$