

# Electrical Engineering 1

## 12026105

### Lecture 5

# Operational Amplifier

# Operational Amplifier

5.1 What is an Op Amp?

5.2 Ideal Op Amp

5.3 Configuration of Op Amp



5.4 Cascaded Op Amp

5.5 Appl : Digital-to Analog Converter

## 5.1 What is an Op Amp (1)

- It is an electronic unit that behaves like a voltage-controlled voltage source.
- It is an active circuit element designed to perform mathematical operations of *addition, subtraction, multiplication, division, differentiation* and *integration*.


# 5.1 What is an Op Amp (2)

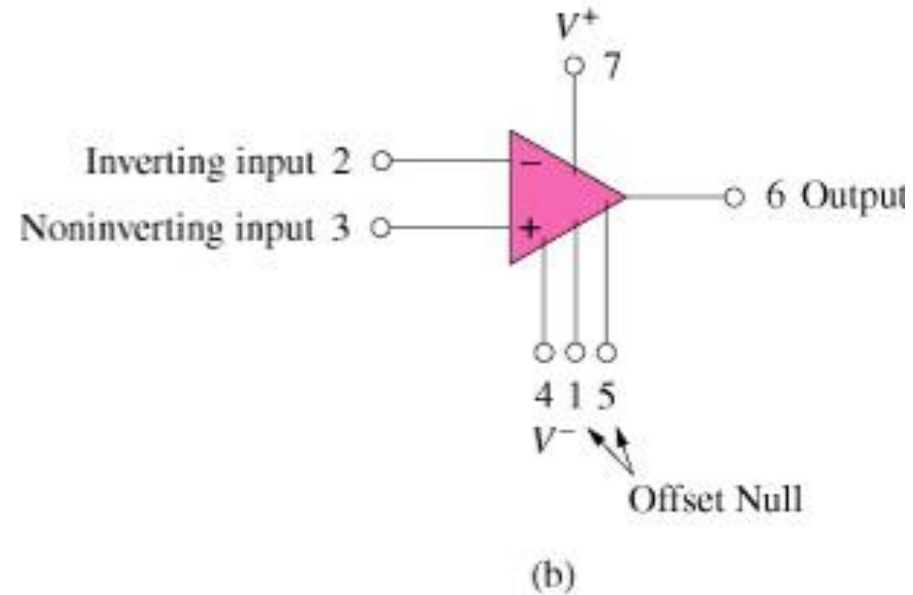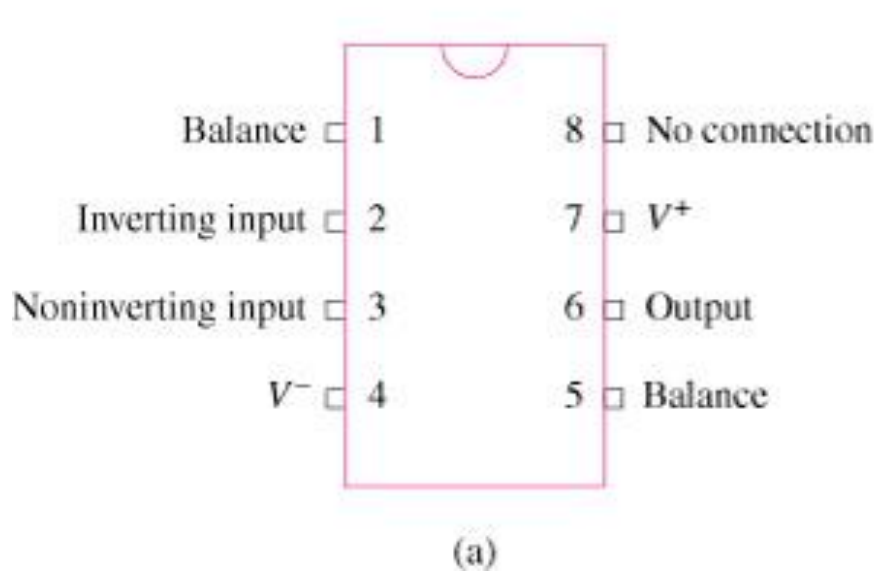


**A typical op amp: (a) pin configuration, (b) circuit symbol**
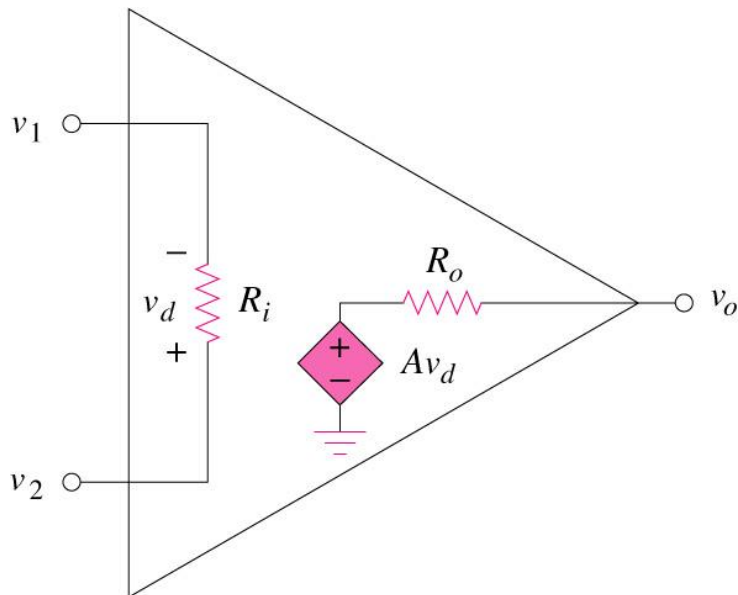
# 5.1 What is an Op Amp (3)

**The equivalent circuit  
Of the non-ideal op amp**



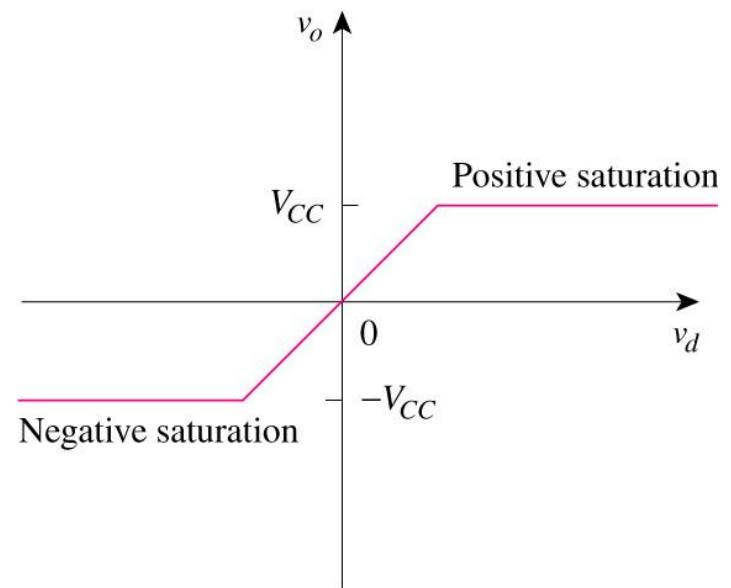**Op Amp output:  
 $v_o$  as a function of  $v_d$**



$$v_d = v_2 - v_1; \quad v_o = A v_d = A(v_2 - v_1)$$

## 5.1 What is an Op Amp (4)


### Typical ranges for op amp parameters

Parameter	Typical range	Ideal values
Open-loop gain, $A$	$10^5$ to $10^8 \Omega$	$\infty$
Input resistance, $R_i$	$10^5$ to $10^{13} \Omega$	$\infty$
Output resistance, $R_o$	10 to 100 $\Omega$	0 $\Omega$
Supply voltage, $V_{CC}$	5 to 24 V	

## 5.2 Ideal Op Amp (1)

An ideal op amp has the following characteristics:

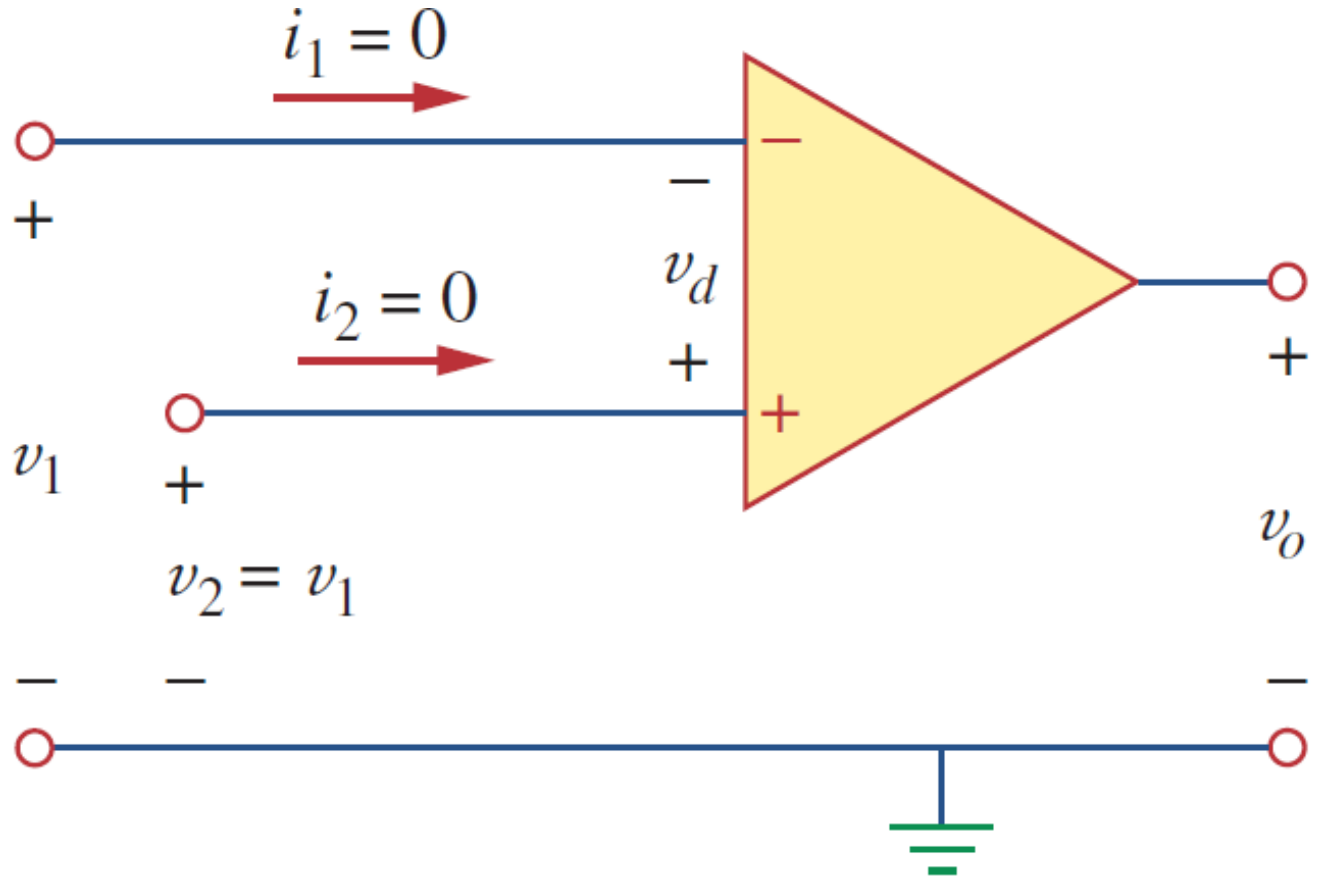
1.  $A \approx \infty$
2.  $R_i \approx \infty$
3.  $R_o \approx 0$



## 5.2 Ideal Op Amp (2)
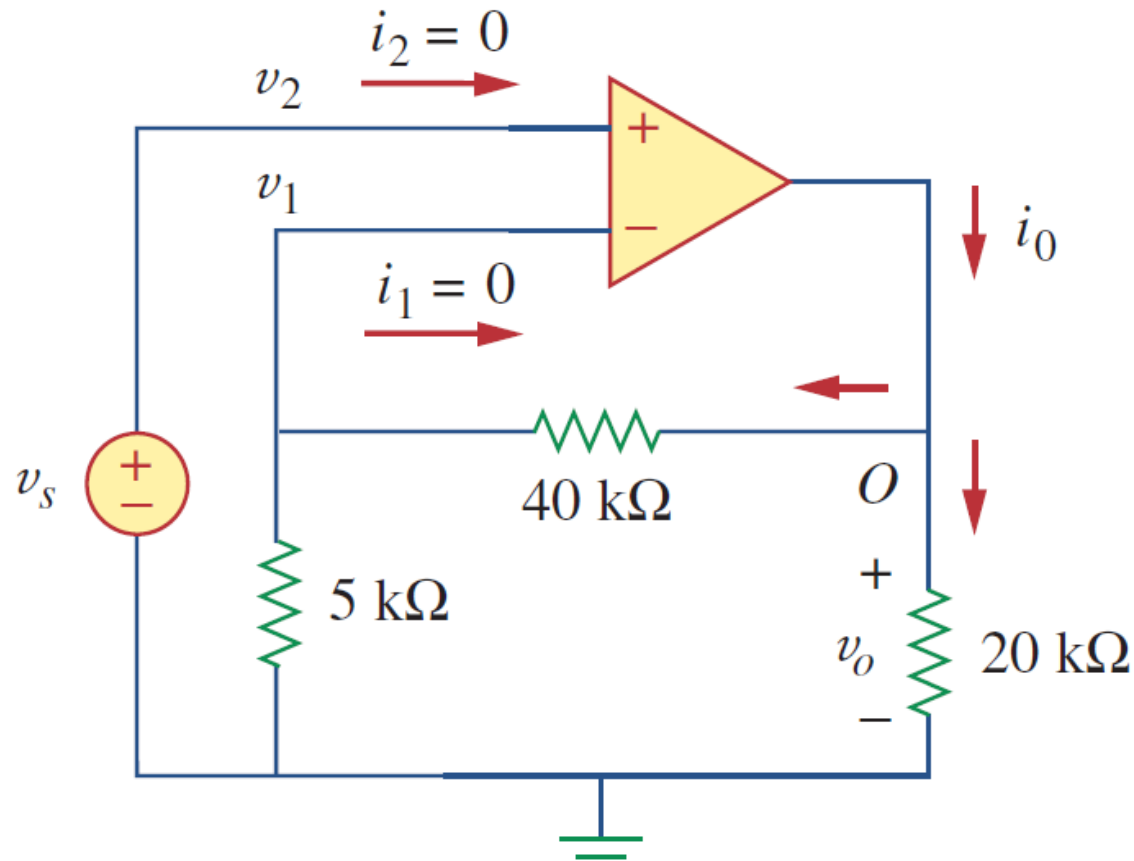
### Example 1:

Determine the value of  $i_o$  if  $v_s = 1 \text{ V}$




Ans:  $0.65 \text{ mA}$


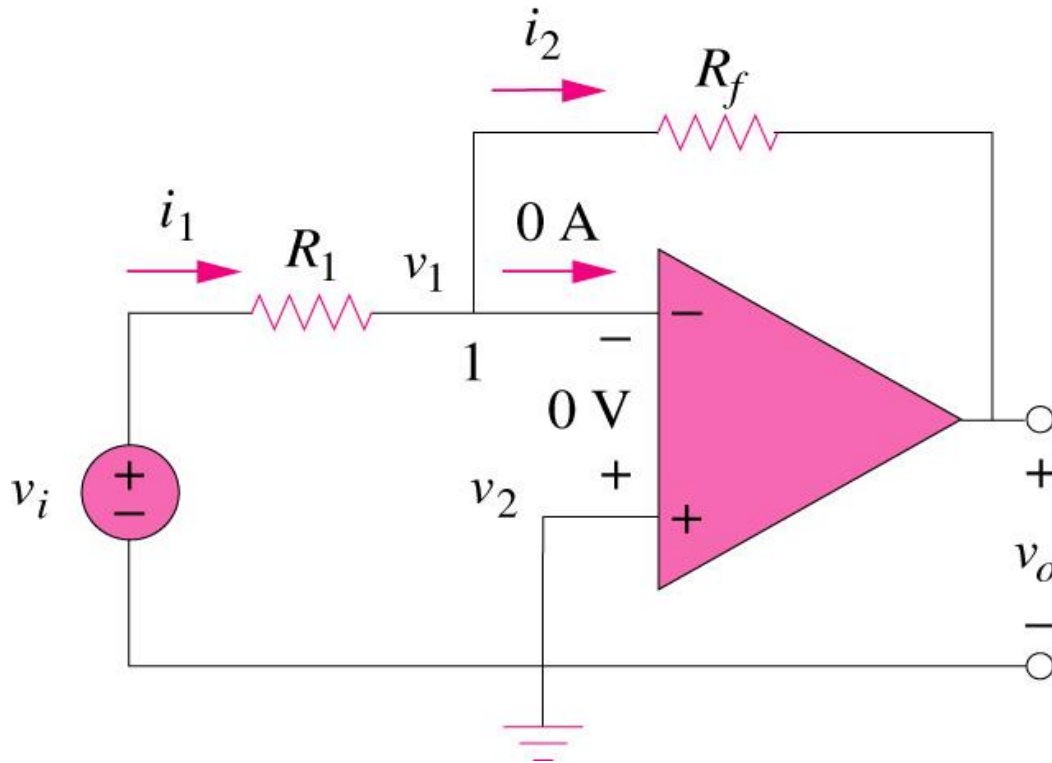
## 5.3 Configuration of Op amp (1)

- Inverting amplifier reverses the polarity of the input signal while amplifying it




$$v_o = -\frac{R_f}{R_1} v_i$$

## 5.3 Configuration of Op amp (2)
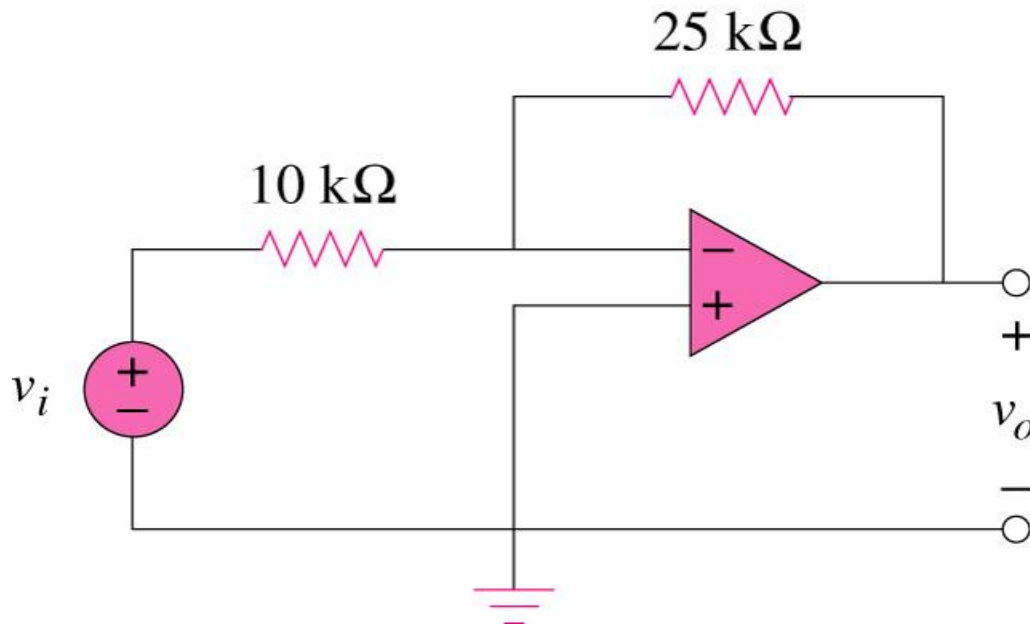
### Example 2


If  $v_i = 0.5\text{V}$ , calculate: (a) the output voltage,  $v_o$  and (b) the current in the  $10\text{k}\Omega$  resistor.



Ans: (a)  $-1.25\text{V}$ ; (b)  $50\mu\text{A}$
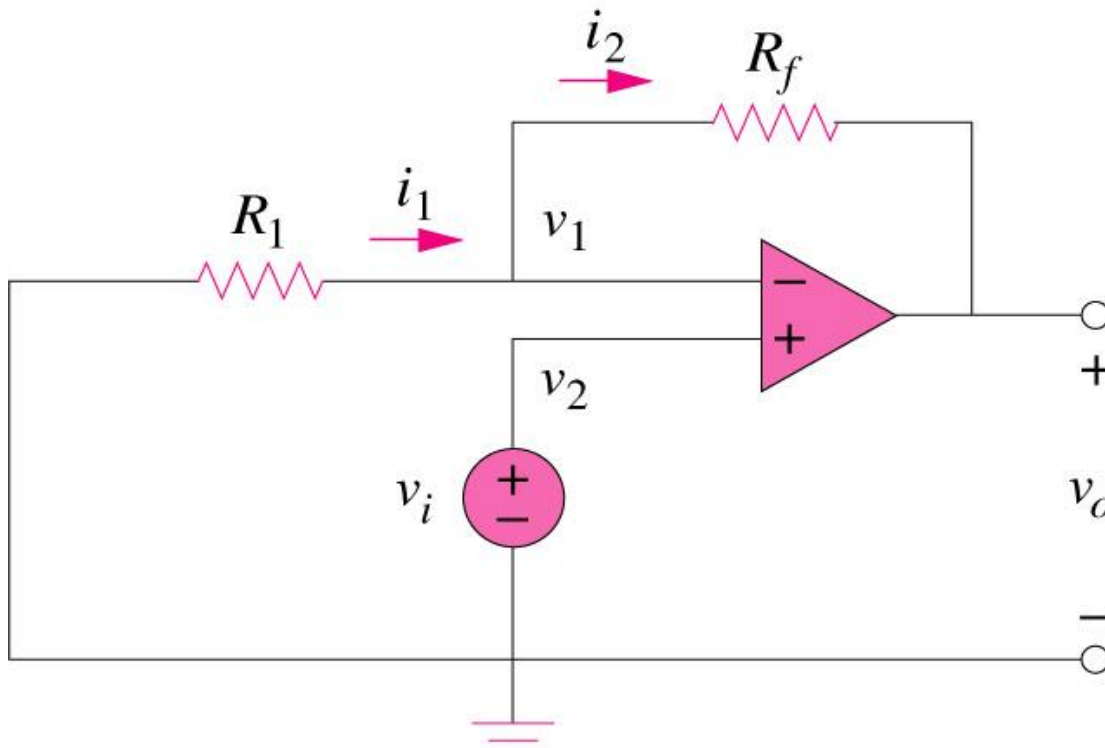
## 5.3 Configuration of Op amp (3)

- Non-inverting amplifier is designed to produce positive voltage gain




$$v_o = \left( 1 + \frac{R_f}{R_1} v_i \right)$$

## 5.3 Configuration of Op amp (4)
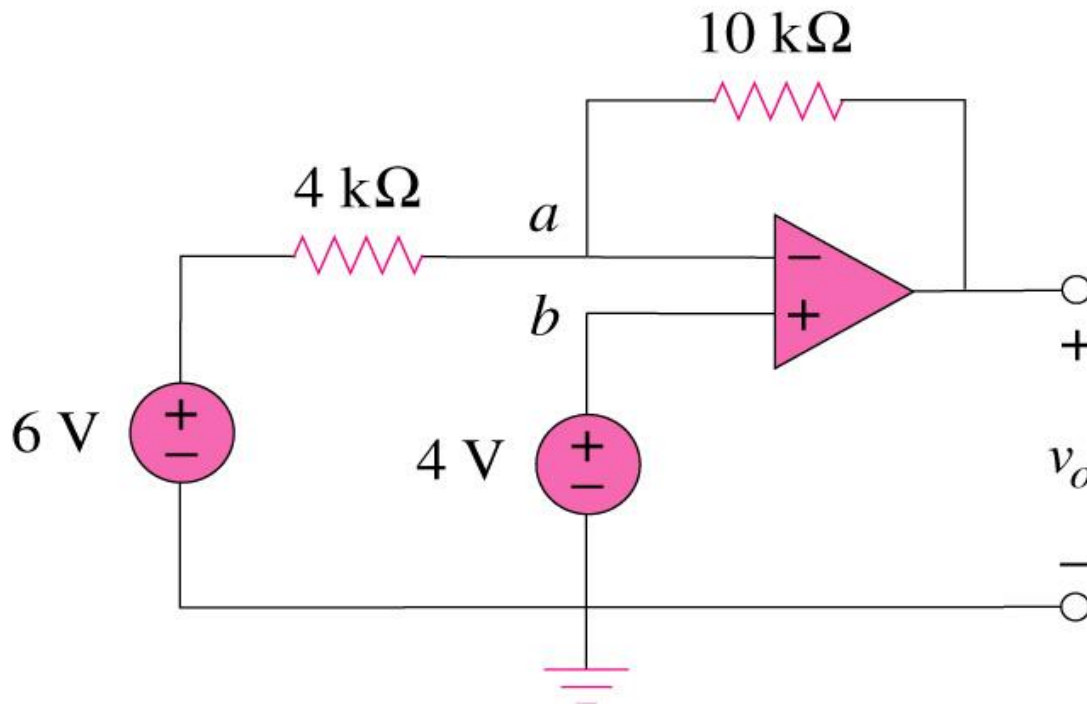
### Example 3


For the op amp shown below, calculate the output voltage  $v_o$ .



Ans: -1V
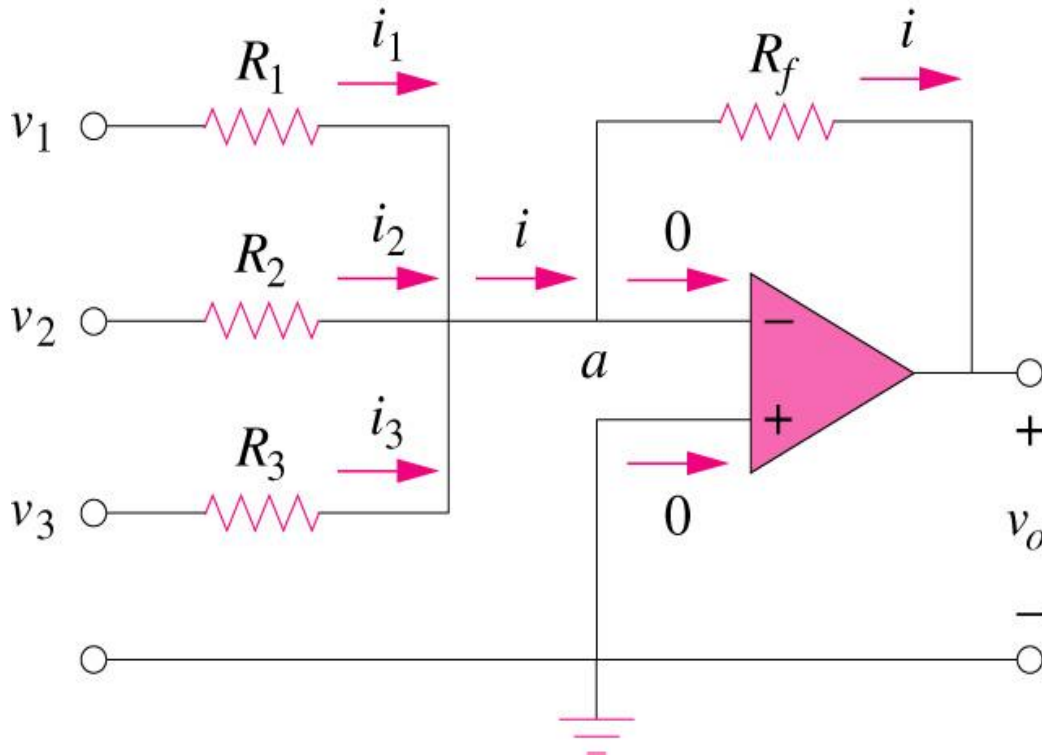
## 5.3 Configuration of Op amp (5)

- Summing Amplifier is an op amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs.




$$v_o = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3\right)$$

## 5.3 Configuration of Op amp (6)
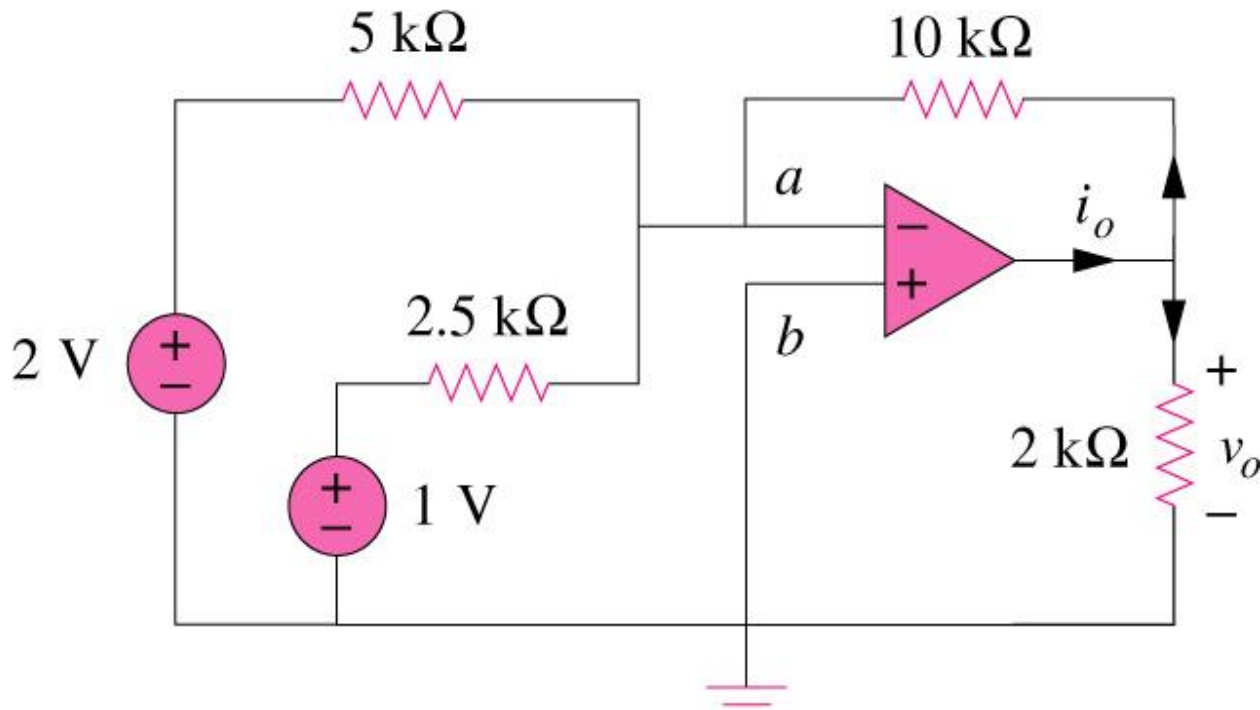
### Example 4


Calculate  $v_o$  and  $i_o$  in the op amp circuit.



Ans: -3.8V, -1.425mA
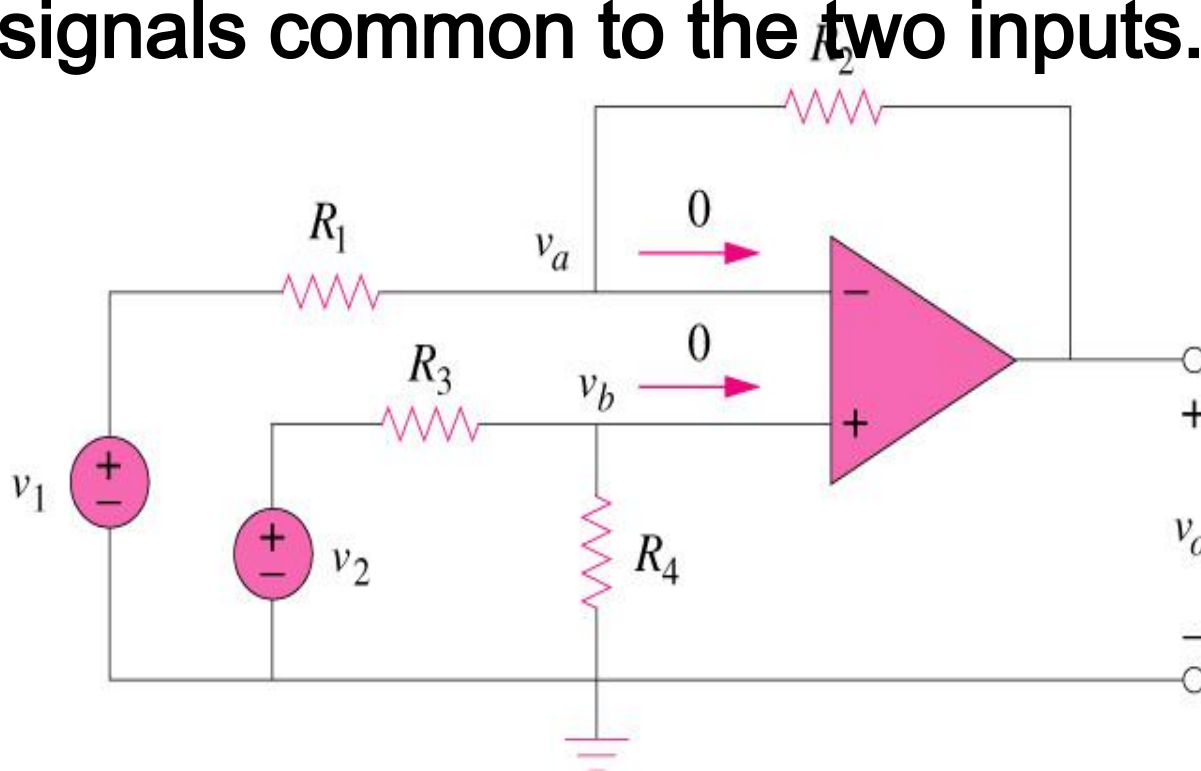
## 5.3 Configuration of Op amp (7)


Difference amplifier is a device that amplifies the difference between two inputs but rejects any signals common to the two inputs.



$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1 \Rightarrow v_o = v_2 - v_1, \text{ if } \frac{R_2}{R_1} = \frac{R_3}{R_4} = 1$$
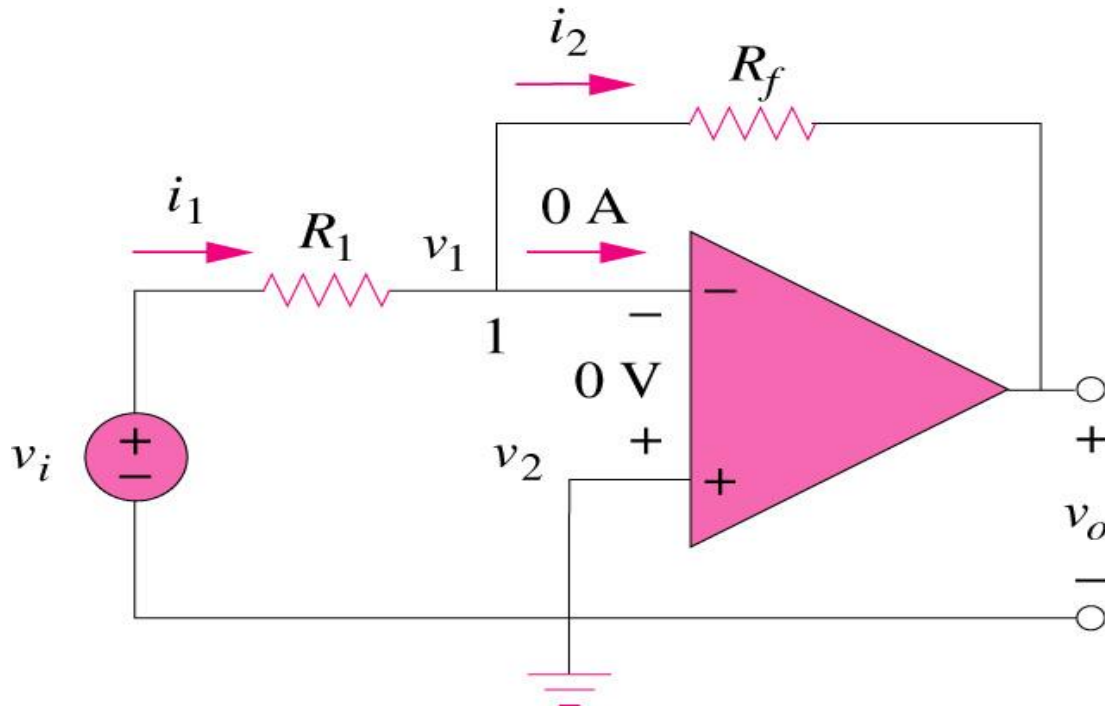
## 5.3 Configuration of Op amp (1)

- Inverting amplifier reverses the polarity of the input signal while amplifying it




$$v_o = -\frac{R_f}{R_1} v_i$$



## 5.3 Configuration of Op amp (6)
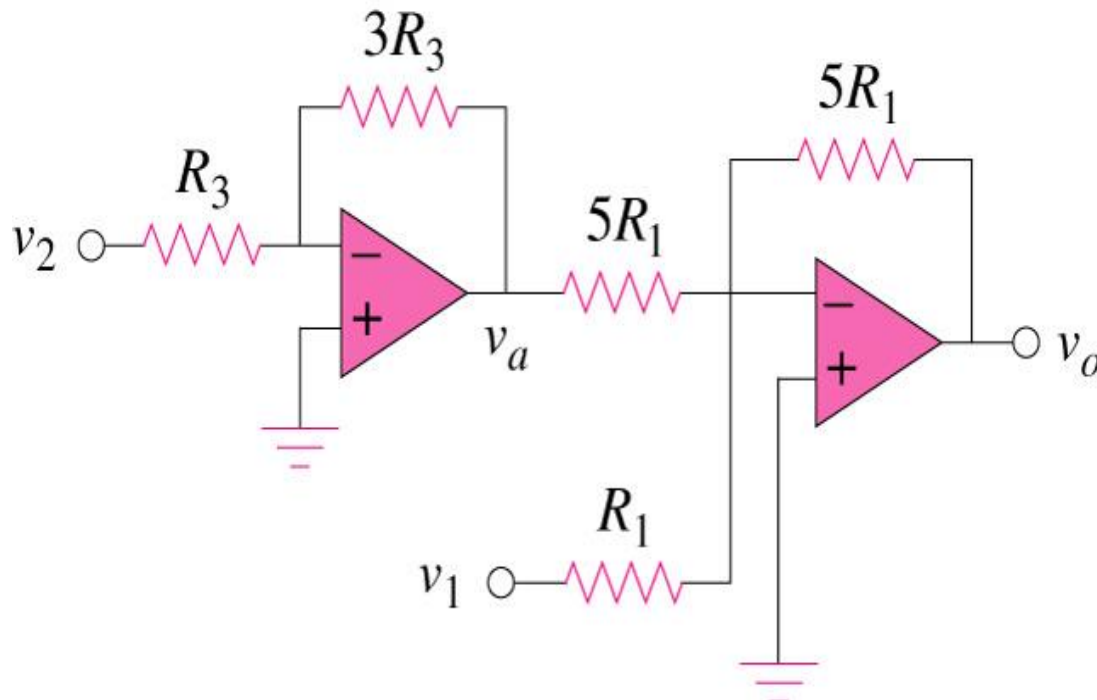
### Example 5

Determine  $R_1, R_2, R_3, R_4$  so that  $v_o = -5v_1 + 3v_2$  for the circuit shown below.



Ans:

$$R_1 = 10\text{k}\Omega$$


$$R_2 = 50\text{k}\Omega$$

$$R_3 = 20\text{k}\Omega$$

$$R_4 = 20\text{k}\Omega$$
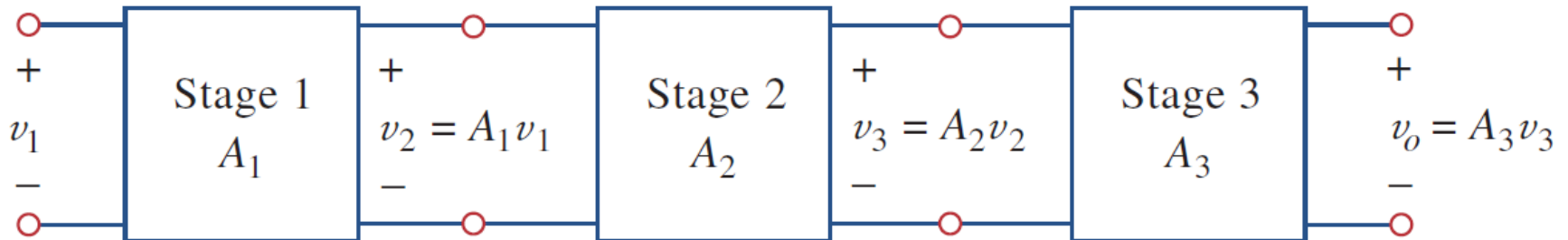
## 5.4 Cascaded Op Amp (1)


- It is a head-to-tail arrangement of two or more op amp circuits such that the output to one is the input of the next.



## 5.4 Cascaded Op Amp (2)
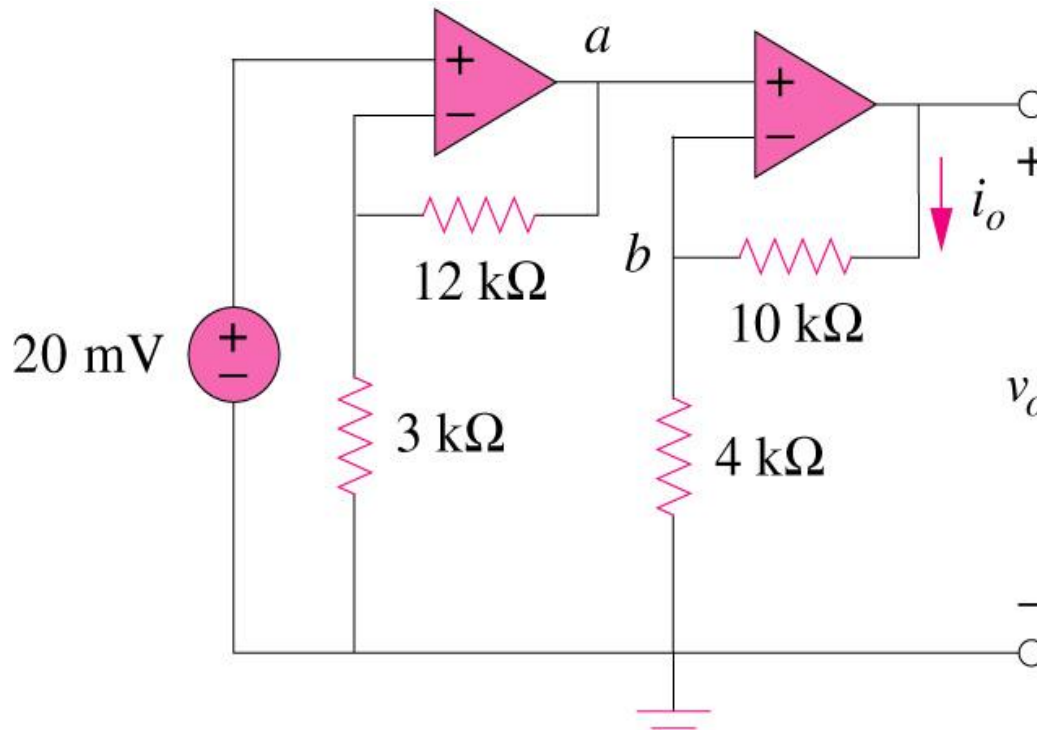
### Example 6

Find  $v_o$  and  $i_o$  in the circuit shown below.




Ans: 350mV, 25μA

## 5.4 Cascaded Op Amp (3)
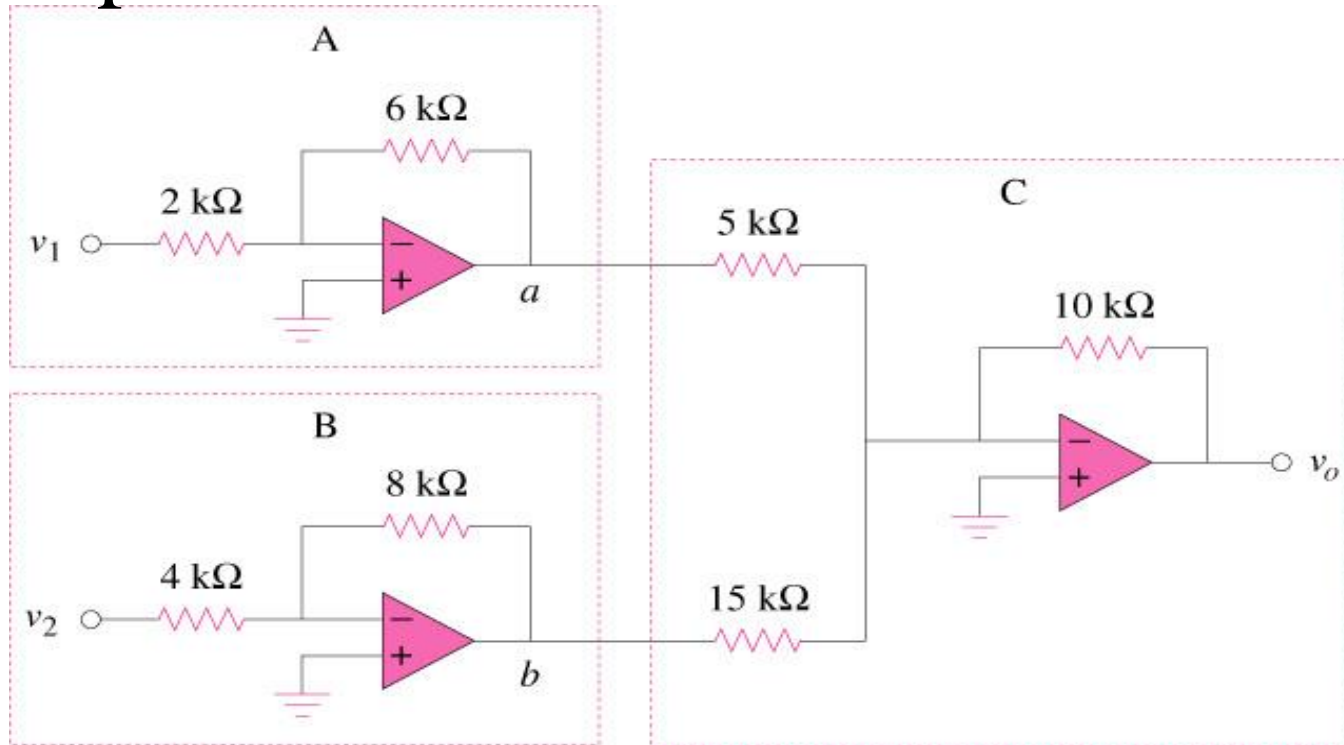
### Example 7

If  $v_1 = 1\text{ V}$  and  $v_2 = 2\text{ V}$ , find  $v_o$  in the op amp circuit shown below.




Ans:  $8.667\text{ V}$

# 5.5 Application (1)

- Digital-to Analog Converter (DAC) : it is a device which transforms digital signals into analog form.
- Four-bit DCA: (a) block diagram (b) binary weighted ladder type



(a)

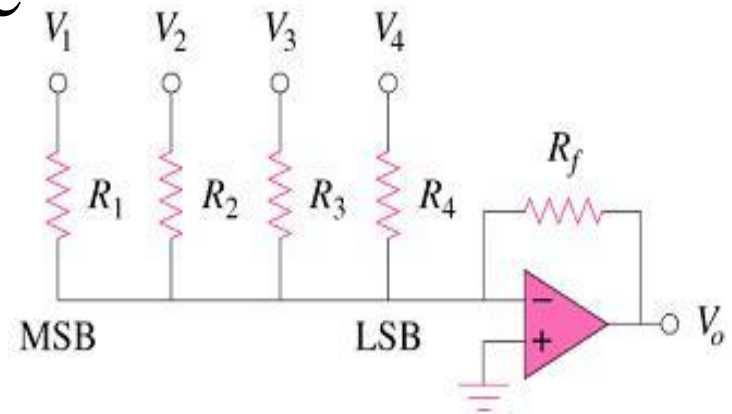

(b)

where

$V_1$  – MSB,  $V_4$  – LSB


$V_1$  to  $V_4$  are either 0 or 1 V

$$-V_0 = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4$$

## 5.5 Application(2)
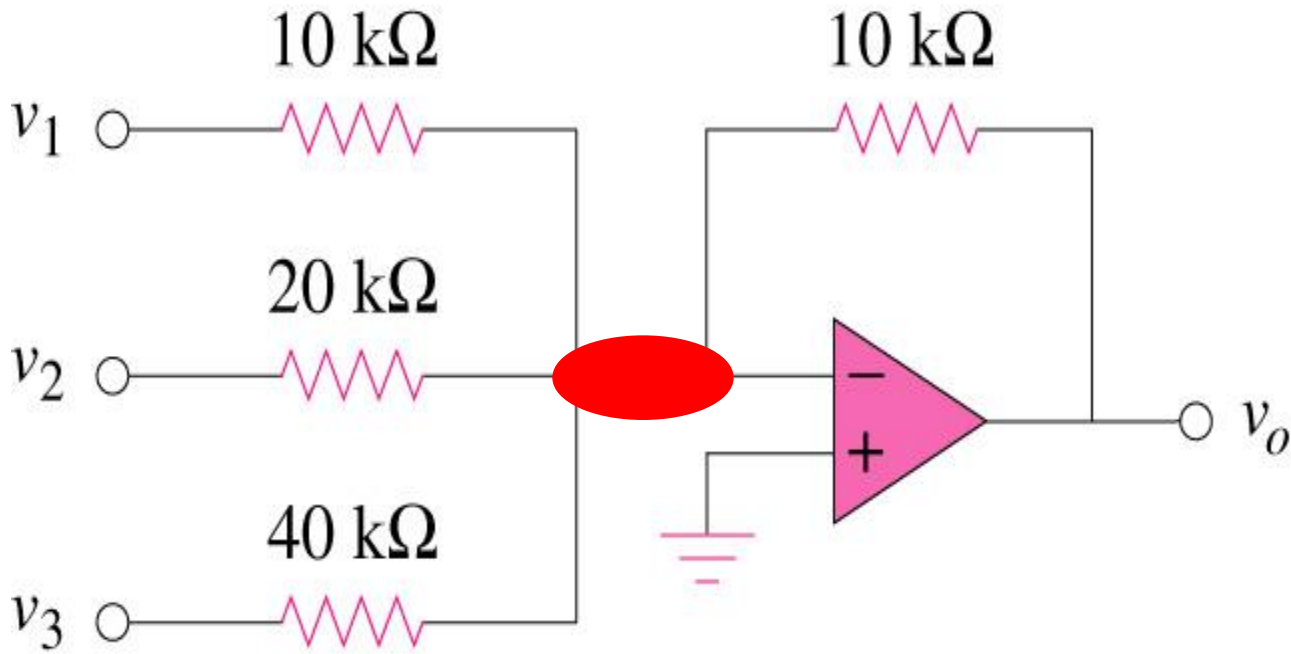
### Example 8

For the circuit shown below, calculate  $v_o$  if  $v_1=0V$ ,  $v_2=1V$  and  $v_3 = 1V$ .



Ans:-0.75V