

# Electrical Engineering 1

## 12026105

### Lecture 9

# Sinusoidal Steady- State Analysis

# Sinusoids and Phasor Chapter 9

9.1 Motivation

9.2 Sinusoids' features

9.3 Phasors


9.4 Phasor relationships for circuit elements

9.5 Impedance and admittance

9.6 Kirchhoff's laws in the frequency domain

9.7 Impedance combinations

# 9.1 Motivation

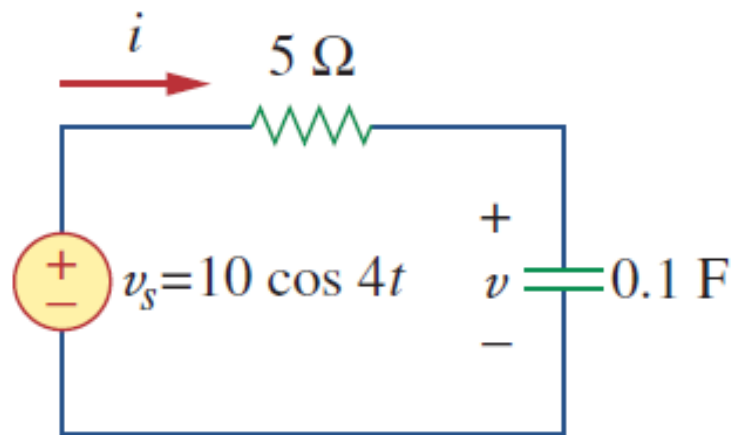


**How can we apply what we have learned before to determine  $i(t)$  and  $v(t)$  ?**

## 9.2 Sinusoids (1)

A sinusoid is a signal that has the form of the sine or cosine function. A general expression for the sinusoid,

$$v(t) = V_m \sin(\omega t + \phi)$$

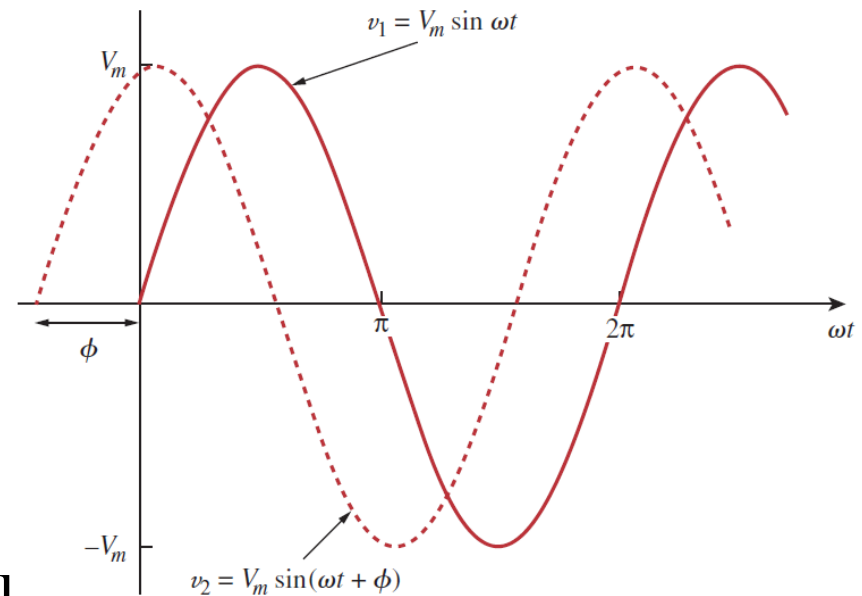

where


$V_m$  = the amplitude of the sinu

$\omega$  = the angular frequency in radians/s

$\phi$  = the phase
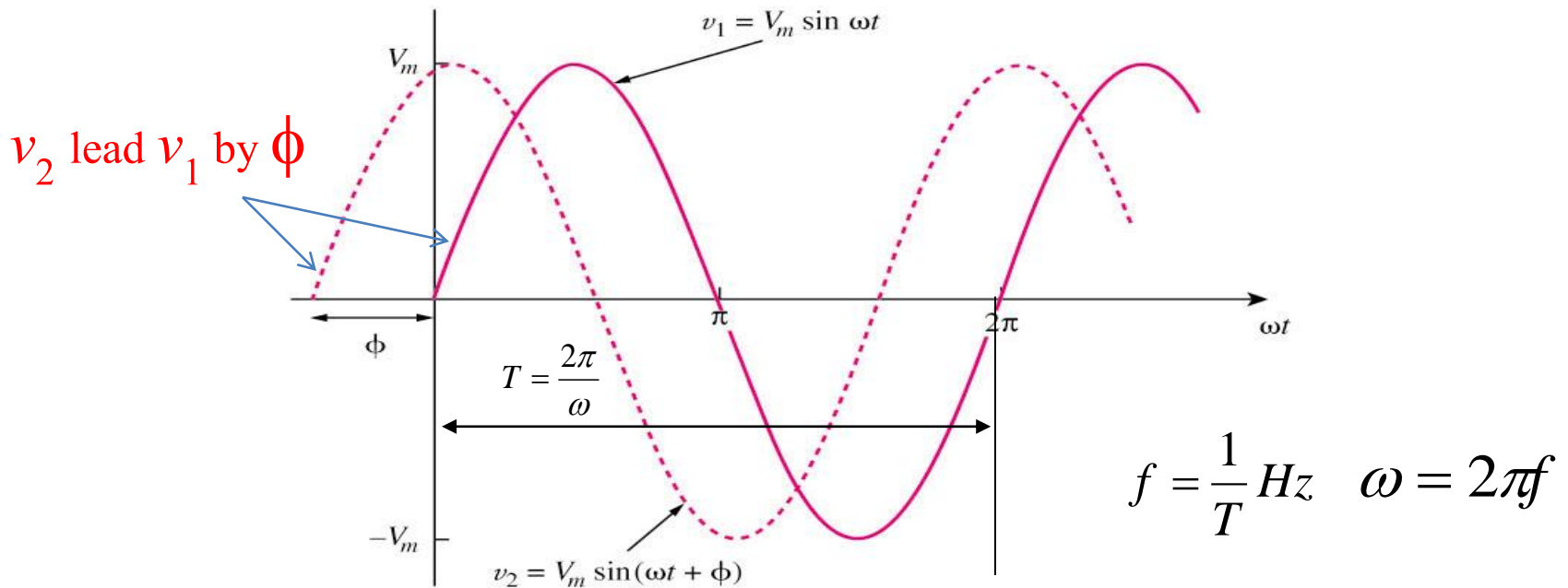
## 9.2 Sinusoids (2)

A periodic function is one that satisfies  $v(t) = v(t + nT)$ , for all  $t$  and for all integers  $n$ .



- Only two sinusoidal values with the same frequency can be compared by their amplitude and phase difference.
- If phase difference is zero, they are in phase; if phase difference is not zero, they are out of phase.

## 9.2 Sinusoids (3)

### Example 1

Given a sinusoid  $5\sin(4\pi t - 60^\circ)$ , calculate its amplitude, phase, angular frequency, period, and frequency.

$$5\sin(4\pi t - 60^\circ)$$

Amplitude=5    $\omega = 4\pi = \frac{2\pi}{T}$    Phase=-60°    $T = 0.5, f = \frac{1}{T} = 2$


### Solution:

Amplitude = 5, phase =  $-60^\circ$ , angular frequency =  $4\pi$  rad/s,  
Period = 0.5 s, frequency = 2 Hz.

## 9.2 Sinusoids (4)
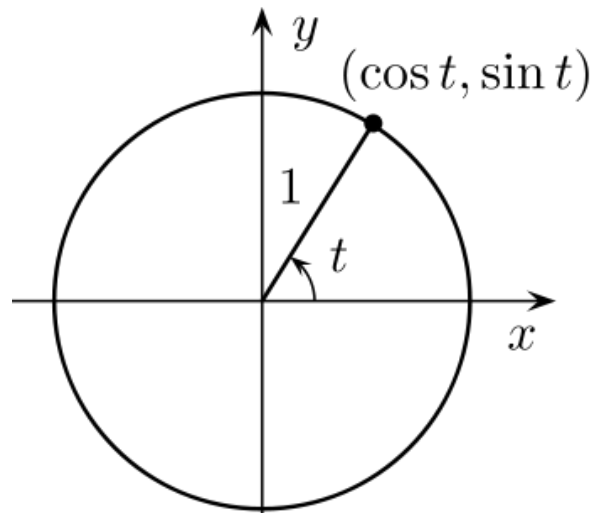
### Example 2

Find the phase angle between  $i_1 = -4\sin(377t + 25^\circ)$   
and  $i_2 = 5\cos(377t - 40^\circ)$ , does  $i_1$  lead or lag  $i_2$ ?



Complementary Angle:

- $\sin \theta = \cos(90^\circ - \theta)$
- $\cos \theta = \sin(90^\circ - \theta)$
- $\tan \theta = \cot(90^\circ - \theta)$
- $\cot \theta = \tan(90^\circ - \theta)$
- $\sec \theta = \operatorname{cosec}(90^\circ - \theta)$
- $\operatorname{cosec} \theta = \sec(90^\circ - \theta)$

Solution:

$$\sin(\omega t + 90^\circ) = \cos(\omega t)$$


$$i_1 = -4\sin(377t + 25^\circ) = 4\sin(377t + 180^\circ + 25^\circ) = 4\sin(377t + 205^\circ)$$

$$i_2 = 5\sin(377t - 40^\circ + 90^\circ) = 5\sin(377t + 50^\circ)$$

therefore,  $i_1$  leads  $i_2$   $155^\circ$ .
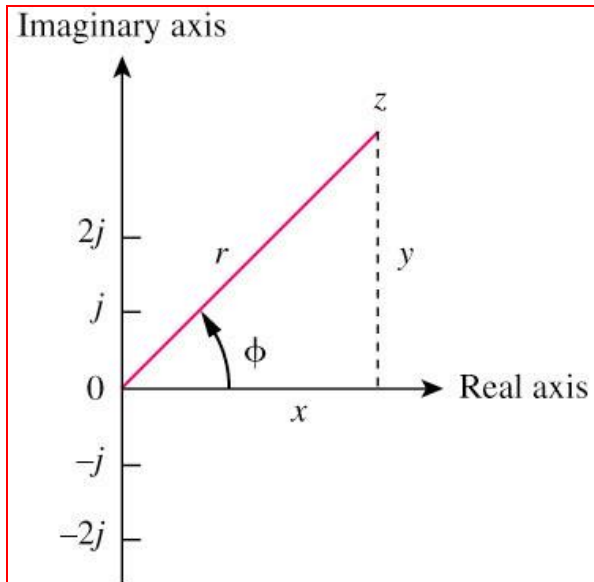
## 9.3 Phasor (1)

- A phasor is a complex number that represents the amplitude and phase of a sinusoid.
- It can be represented in one of the following three forms:



- Rectangular  $z = x + jy = r(\cos \phi + j \sin \phi)$
- Polar  $z = r \angle \phi$
- Exponential  $z = re^{j\phi}$

where

$$r = \sqrt{x^2 + y^2}$$
$$\phi = \tan^{-1} \frac{y}{x}$$



## 9.3 Phasor (2)

**Example 3** Evaluate the following complex numbers:

a.  $[(5 + j2)(-1 + j4) - 5 \angle 60^\circ]$

$-13 + j18$

$5(\cos(60^\circ) + j \sin(60^\circ)) = 2.5 + j4.33$

b.  $\frac{10 + j5 + 3 \angle 40^\circ}{-3 + j4} + 10 \angle 30^\circ$

$-0.3672 - j2.7996$

$10(\cos(30^\circ) + j \sin(30^\circ)) = 8.66 + j5$

Solution:

a.  $-15.5 + j13.67$

b.  $8.293 + j2.2$

## 9.3 Phasor (3)

### Mathematic operation of complex number:

1. Addition

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

2. Subtraction

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

3. Multiplication

$$z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

4. Division

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$$

5. Reciprocal

$$\frac{1}{z} = \frac{1}{r} \angle -\phi$$

6. Square root

$$\sqrt{z} = \sqrt{r} \angle \phi/2$$

7. Complex conjugate

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

8. Euler's identity

$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$

## 9.3 Phasor (4)

**Transform a sinusoid to and from the time domain to the phasor domain:**

$$\begin{array}{ccc} v(t) = V_m \cos(\omega t + \phi) & \longleftrightarrow & V = V_m \angle \phi \\ \text{(time domain)} & & \text{(phasor domain)} \end{array}$$

- Amplitude and phase difference are two principal concerns in the study of voltage and current sinusoids.
- **Phasor** will be defined from the cosine function in all our proceeding study.

## 9.3 Phasor (5)

**Example 4** *Transform the following sinusoids to phasors:*

$$i = 6\cos(50t - 40^\circ) \text{ A}$$

$$v = -4\sin(30t + 50^\circ) \text{ V}$$

**Solution:**

a)  $i = 6\angle -40^\circ \text{ A}$

b) since  $-\sin(A) = \cos(A + 90^\circ)$

$$v(t) = 4\cos(30t + 50^\circ + 90^\circ) = 4\cos(30t + 140^\circ) = 4\angle 140^\circ$$

## 9.3 Phasor (6)

**Example 5** Transform the sinusoids corresponding to phasors:

a.  $\mathbf{V} = -10\angle 30^\circ \text{ V}$

b.  $\mathbf{I} = j(5 - j12) \text{ A}$

Solution:

a).  $v(t) = 10\cos(\omega t + 210^\circ) \text{ V}$

Since  $\mathbf{I} = 12 + j5 = \sqrt{12^2 + 5^2} \angle \tan^{-1}\left(\frac{5}{12}\right) = 13\angle 22.62^\circ$

b).  $i(t) = 13\cos(\omega t + 22.62^\circ) \text{ V}$

## 9.3 Phasor (7)

The differences between  $v(t)$  and  $V$

- $v(t)$  is instantaneous or time-domain representation  
 $V$  is the frequency or phasor-domain representation.
- $v(t)$  is time dependent,  $V$  is not.
- $v(t)$  is always real with no complex term,  $V$  is generally complex.

Note: Phasor analysis applies only when frequency is constant; when it is applied to two or more sinusoid signals only if they have the same frequency.

## 9.3 Phasor (8)

Relationship between differential, integral operation in phasor listed as follow:

<b>Time domain</b>		<b>Phasor domain</b>
$v(t)$	$\longleftrightarrow$	$V = V \angle \phi$
$\frac{dv}{dt}$	$\longleftrightarrow$	$j\omega V$
$\int v dt$	$\longleftrightarrow$	$\frac{V}{j\omega}$

## 9.3 Phasor (9)

**Example 6** Use phasor approach, determine the current  $i(t)$  in a circuit described by the integrodifferential equation.

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

$$4I + 8 \frac{I}{j\omega} - 3j\omega I = 50 \angle 75^\circ$$

$$\omega = 2$$

$$4I - j4I - j6I = 50 \angle 75^\circ$$

$$4I(1 - j - j1.5) = 10.77 \angle -68.2^\circ I = 50 \angle 75^\circ$$



$$I = 4.642 \angle 143.2^\circ \longleftrightarrow i(t) = 4.642 \cos(2t + 143.2^\circ)$$

Answer:  $i(t) = 4.642 \cos(2t + 143.2^\circ)$  A


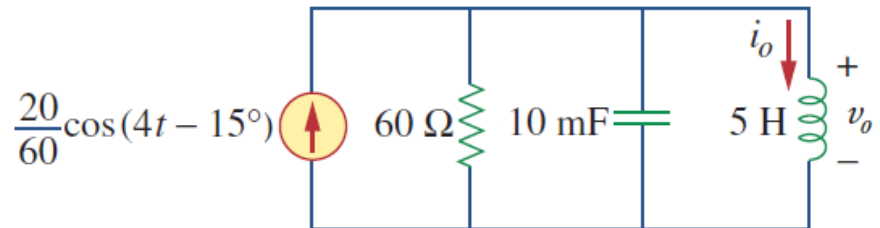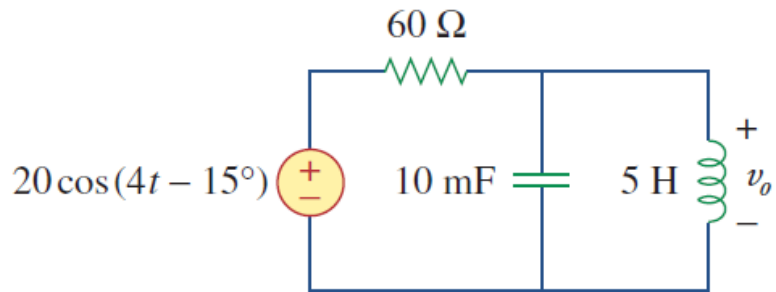
## 9.3 Phasor (10)

We can derive the differential equations for the following circuit in order to solve for  $v_o(t)$  in phasor domain  $V_o$ .



$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

$$\frac{d^2 i_o}{dt^2} + \frac{5}{3} \frac{di_o}{dt} + 20i_o = \frac{20}{3} \cos(4t - 15^\circ)$$

$$v_o = L \frac{di_o}{dt}$$

- However, the derivation may sometimes be very tedious.


Is there any quicker and more systematic methods to do it?

# The answer is YES!


Instead of first deriving the differential equation and then transforming it into phasor to solve for  $V_o$ , we can transform all the RLC components into phasor first, then apply the KCL laws and other theorems to set up a phasor equation involving  $V_o$  directly.

# 9.4 Phasor Relation for Circuit Elements(1)


## Resistor:

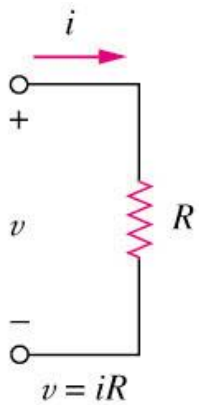


(a)

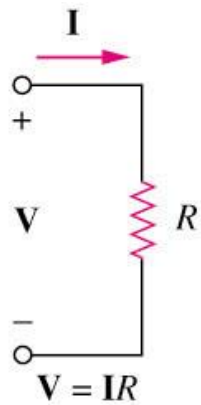


(b)

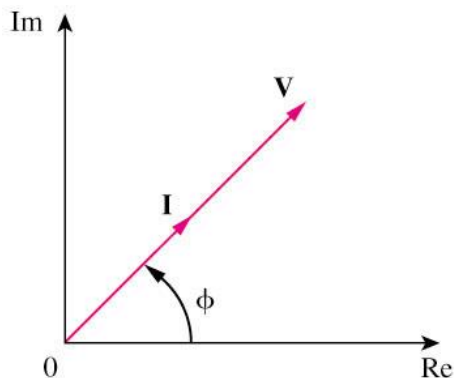


## Inductor:

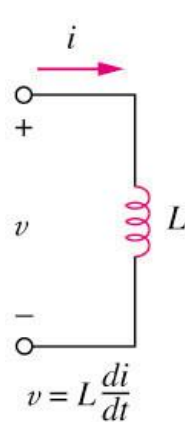


(a)

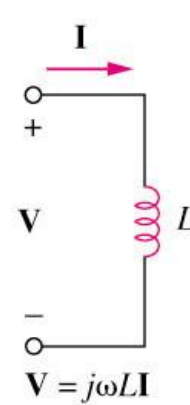


(b)

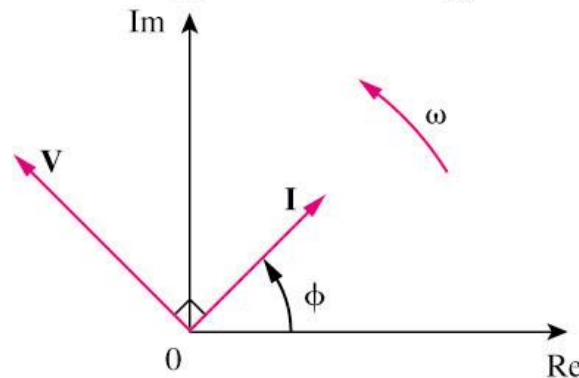


## Capacitor:

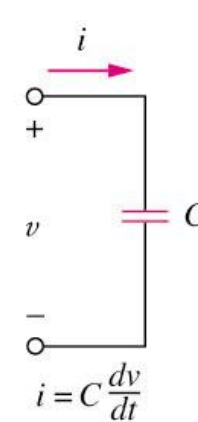

(a)

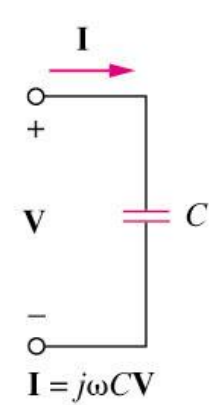

(b)

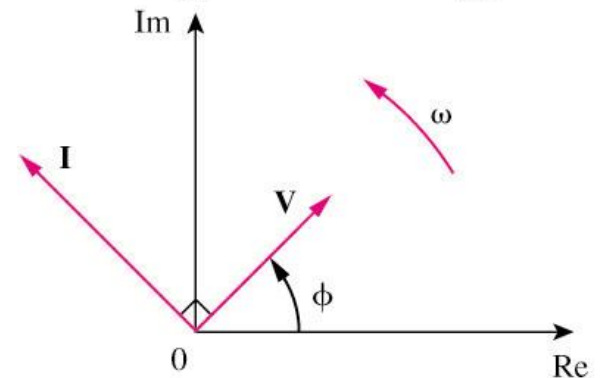

# 9.4 Phasor Relation for Circuit Elements(2)

## Summary of voltage-current relationship

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

## 9.4 Phasor Relation for Circuit Elements(3)

### Example 7

If  $v(t) = 6\cos(100t - 30^\circ)$  is applied to a  $50 \mu\text{F}$  capacitor, calculate the current,  $i(t)$ , through the capacitor

$$I = j\omega CV$$

$$I = j \times 100 \times 50 \times 10^{-6} \times 6 \angle -30^\circ = 0.03 \angle 90^\circ \times \angle -30^\circ = 0.03 \angle 60^\circ$$

$$i(t) = 0.03\cos(100t + 60^\circ)$$

**Answer:  $i(t) = 30 \cos(100t + 60^\circ) \text{ mA}$**

## 9.5 Impedance and Admittance (1)

- The impedance  $Z$  of a circuit is the ratio of the phasor voltage  $V$  to the phasor current  $I$ , measured in ohms  $\Omega$ .

$$Z = \frac{V}{I} = R + jX$$

where  $R = \text{Re}(Z)$  is the resistance and  $X = \text{Im}(Z)$  is the reactance. **Positive  $X$  is for L** and **negative  $X$  is for C**.


- The admittance  $Y$  is the reciprocal of impedance ( $Z$ ), measured in siemens (S).  $Y = \frac{1}{Z} = \frac{I}{V}$

## 9.5 Impedance and Admittance (2)

### Impedances and admittances of passive elements

Element	Impedance	Admittance
<b>R</b>	$Z = R$	$Y = \frac{1}{R}$
<b>L</b>	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
<b>C</b>	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

# 9.5 Impedance and Admittance (3)




$Z = j\omega L$

Short circuit at dc  $\Rightarrow \omega = 0; Z = 0$

Open circuit at high frequencies  $\Rightarrow \omega \rightarrow \infty; Z \rightarrow \infty$

(a)



$Z = \frac{1}{j\omega C}$

Open circuit at dc  $\Rightarrow \omega = 0; Z \rightarrow \infty$

Short circuit at high frequencies  $\Rightarrow \omega \rightarrow \infty; Z = 0$

(b)




## 9.5 Impedance and Admittance (4)

After we know how to convert RLC components from time to phasor domain, we can **transform** a time domain circuit into a phasor/frequency domain circuit.

Hence, we can apply the KCL laws and other theorems to **directly** set up phasor equations involving our target variable(s) for solving.

## 9.5 Impedance and Admittance (5)

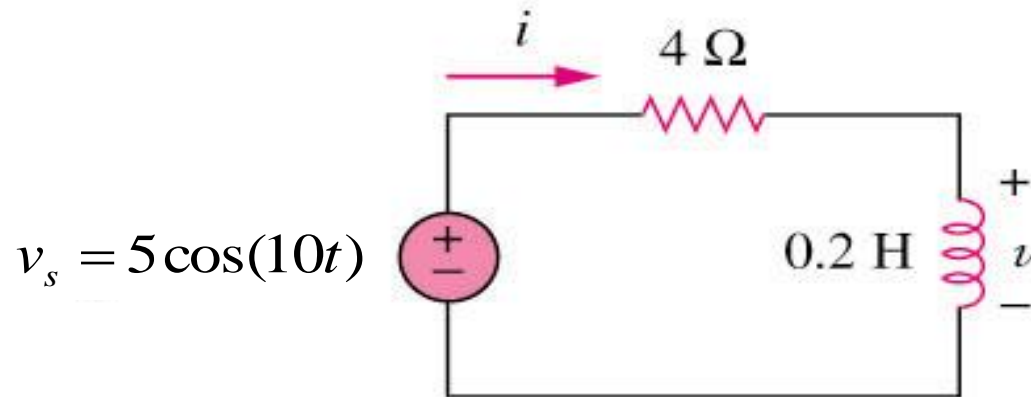**Example 8** Refer to Figure below, determine  $v(t)$  and  $i(t)$ .



**Answers:**  $i(t) = 1.118 \cos(10t - 26.56^\circ) \text{ A}$ ;  $v(t) = 2.236 \cos(10t + 63.43^\circ) \text{ V}$

## 9.6 Kirchhoff's Laws in the FreqDomain(1)


- Both KVL and KCL are hold in the phasor(frequency) domain.
- Moreover, the variables to be handled are phasors, which are complex numbers.

# 9.7 Impedance Combinations (1)

- The following principles used for DC circuit analysis all apply to AC circuit.
- For example:
  - a. voltage division
  - b. current division
  - c. circuit reduction
  - d. impedance equivalence
  - e. Y- $\Delta$  transformation

## 9.7 Impedance Combinations (2)

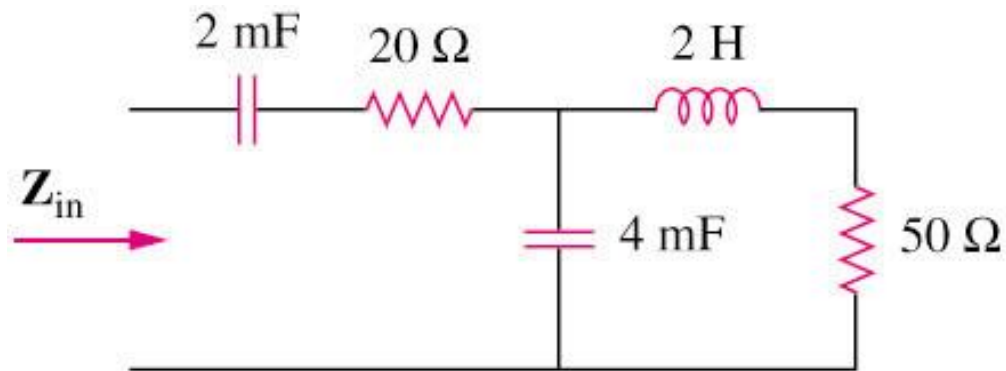**Example 9** Determine the input impedance of the circuit in figure below at  $\omega = 10$  rad/s.



Answer:  $Z_{in} = 32.38 - j73.76$