

# Electrical Engineering 1

## 12026105

### Chapter 9

## Sinusoids and Phasors

## Learning Objectives

*By using the information and exercises in this chapter you will be able to:*

1. Better understand sinusoids.
2. Understand phasors.
3. Understand the phasor relationships for circuit elements.
4. Know and understand the concepts of impedance and admittance.
5. Understand Kirchhoff's laws in the frequency domain.
6. Comprehend the concept of phase-shift.
7. Understand the concept of AC bridges.


# Sinusoids and Phasor Chapter 9

- 9.1 Motivation
- 9.2 Sinusoids' features
- 9.3 Phasors
- 9.4 Phasor relationships for circuit elements
- 9.5 Impedance and admittance
- 9.6 Kirchhoff's laws in the frequency domain
- 9.7 Impedance combinations

# Schrödinger Equation

$$i\hbar \frac{\partial}{\partial t} |\Psi(t)\rangle = \hat{H} |\Psi(t)\rangle$$

## How to determine $v(t)$ and $i(t)$ ?

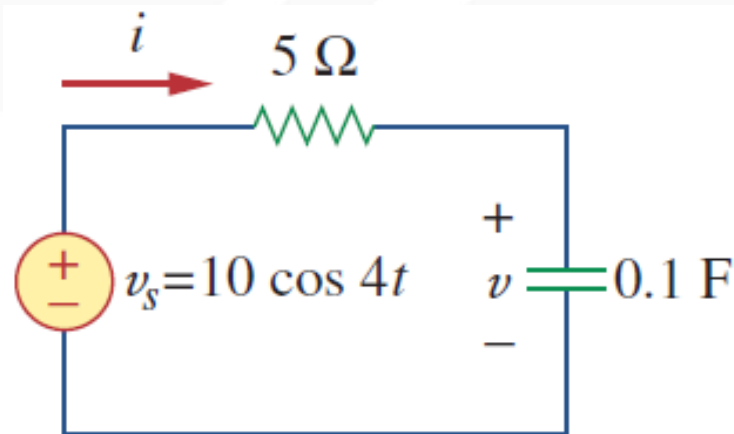

How can we apply what we have learned before to determine  $i(t)$  and  $v(t)$  ?

# 9.2 Sinusoids (1)

A sinusoid is a signal that has the form of the sine or cosine function.


A general expression for the sinusoid,  $v(t) = V_m \sin(\omega t + \phi)$

where

$V_m$  = the amplitude of the sinusoid


$\omega$  = the angular frequency in radians/s

$\phi$  = the phase

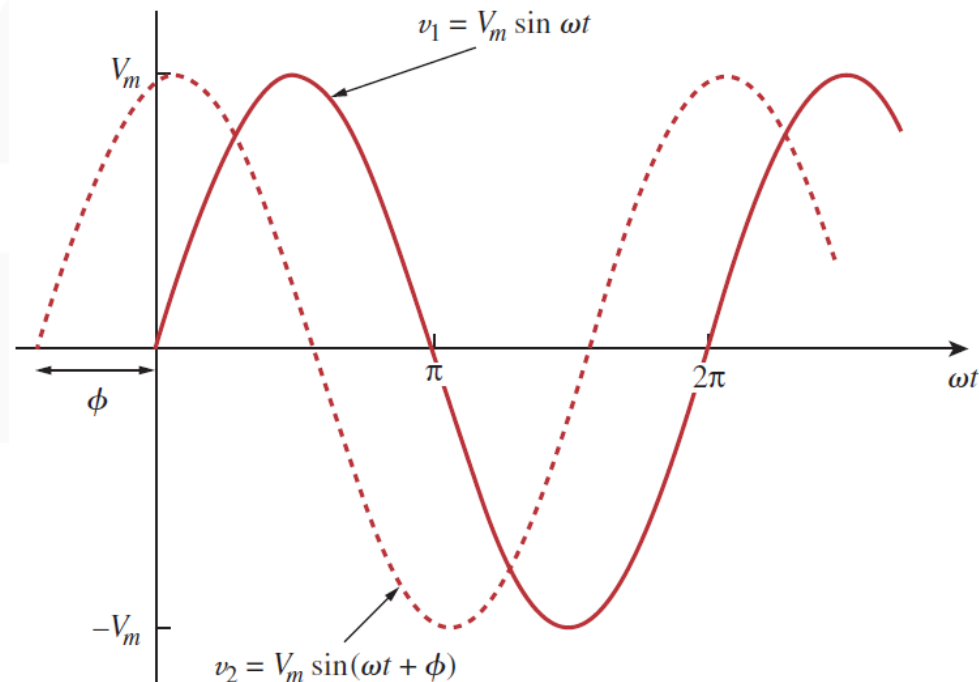
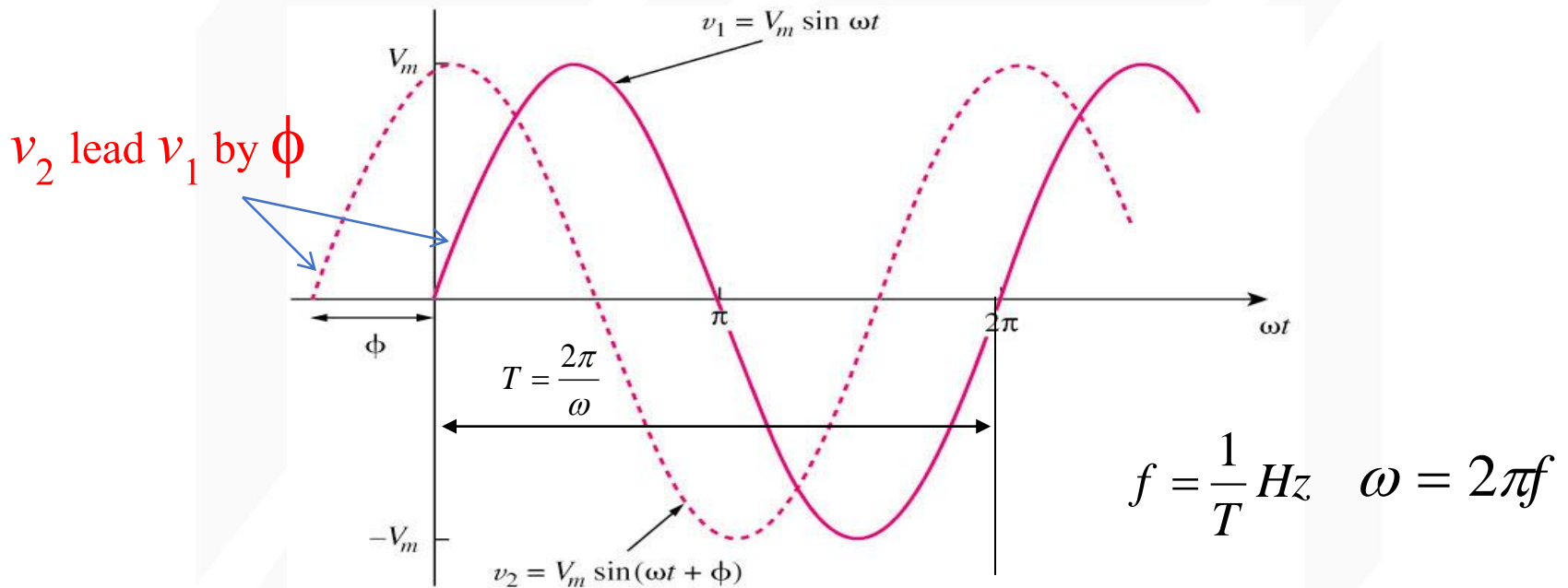
# 9.2 Sinusoids (2)

A periodic function is one that satisfies  $v(t) = v(t + nT)$ , for all  $t$  and for all integers  $n$ .



- Only two sinusoidal values with the same frequency can be compared by their amplitude and phase difference.
- If phase difference is zero, they are in phase; if phase difference is not zero, they are out of phase.

# 9.2 Sinusoids (3)

## Example 1

Given a sinusoid  $5 \sin(4\pi t - 60^\circ)$ , calculate its amplitude, phase, angular frequency, period, and frequency.

$5 \sin(4\pi t - 60^\circ)$

Amplitude=5       $\omega = 4\pi = \frac{2\pi}{T}$       Phase=-60°       $T = 0.5, f = \frac{1}{T} = 2$

## Solution:

Amplitude = 5, phase =  $-60^\circ$ , angular frequency =  $4\pi$  rad/s,  
 Period = 0.5 s, frequency = 2 Hz.




# 9.2 Sinusoids (4)
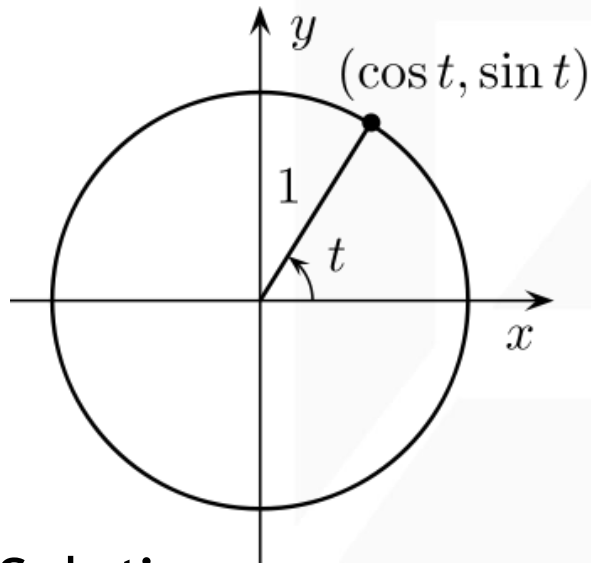
## Example 2

Find the phase angle between  $i_1 = -4 \sin(377t + 25^\circ)$

and  $i_2 = 5 \cos(377t - 40^\circ)$ , does  $i_1$  lead or lag  $i_2$ ?



Complementary Angle:

- $\sin \theta = \cos(90^\circ - \theta)$
- $\cos \theta = \sin(90^\circ - \theta)$
- $\tan \theta = \cot(90^\circ - \theta)$
- $\cot \theta = \tan(90^\circ - \theta)$
- $\sec \theta = \operatorname{cosec}(90^\circ - \theta)$
- $\operatorname{cosec} \theta = \sec(90^\circ - \theta)$

$$\sin(\theta + \pi) = -\sin \theta$$

$$\cos(\theta + \pi) = -\cos \theta$$

$$\sin\left(\theta + \frac{\pi}{2}\right) = +\cos \theta$$

$$\cos\left(\theta + \frac{\pi}{2}\right) = -\sin \theta$$

Solution:

$$\sin(\omega t + 90^\circ) = \cos(\omega t)$$

$$i_1 = -4 \sin(377t + 25^\circ) = 4 \sin(377t + 180^\circ + 25^\circ) = 4 \sin(377t + 205^\circ)$$

$$i_2 = 5 \sin(377t - 40^\circ + 90^\circ) = 5 \sin(377t + 50^\circ)$$


therefore,  $i_1$  leads  $i_2$   $155^\circ$ .

# 9.2 Sinusoids (5)

Reflected in $\theta = 0$	Reflected in $\theta = \pi/2$ (co-function identities)	Reflected in $\theta = \pi$
$\sin(-\theta) = -\sin \theta$ $\cos(-\theta) = +\cos \theta$	$\sin\left(\frac{\pi}{2} - \theta\right) = +\cos \theta$ $\cos\left(\frac{\pi}{2} - \theta\right) = +\sin \theta$	$\sin(\pi - \theta) = +\sin \theta$ $\cos(\pi - \theta) = -\cos \theta$
Shift by $\pi/2$	Shift by $\pi$ Period for tan and cot	Shift by $2\pi$ Period for sin, cos
$\sin\left(\theta + \frac{\pi}{2}\right) = +\cos \theta$ $\cos\left(\theta + \frac{\pi}{2}\right) = -\sin \theta$	$\sin(\theta + \pi) = -\sin \theta$ $\cos(\theta + \pi) = -\cos \theta$	$\sin(\theta + 2\pi) = +\sin \theta$ $\cos(\theta + 2\pi) = +\cos \theta$
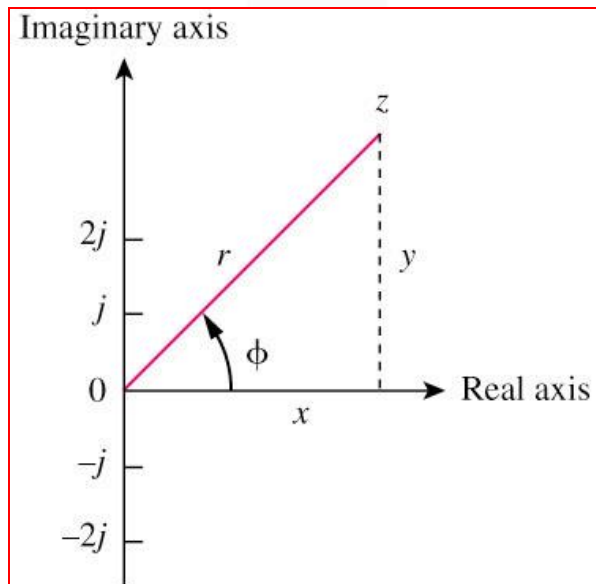
# 9.3 Phasor (1)

- A phasor is a complex number that represents the amplitude and phase of a sinusoid.
- It can be represented in one of the following three forms:



a. Rectangular  $z = x + jy = r(\cos \phi + j \sin \phi)$

b. Polar  $z = r \angle \phi$

c. Exponential  $z = re^{j\phi}$

where

$$r = \sqrt{x^2 + y^2}$$

$$\phi = \tan^{-1} \frac{y}{x}$$

# 9.3 Phasor (2)

Example 3 Evaluate the following complex numbers:

a.  $[(5 + j2)(-1 + j4) - 5 \angle 60^\circ]$

$-13 + j18$

$5(\cos(60^\circ) + j \sin(60^\circ)) = 2.5 + j4.33$

b.  $\frac{10 + j5 + 3 \angle 40^\circ}{-3 + j4} + 10 \angle 30^\circ$

$-0.3672 - j2.7996$

$10(\cos(30^\circ) + j \sin(30^\circ)) = 8.66 + j5$

Solution:

- a.  $-15.5 + j13.67$
- b.  $8.293 + j2.2$

# 9.3 Phasor (3)

Mathematic operation of complex number:

---

1. Addition  $z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$

2. Subtraction  $z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$

3. Multiplication  $z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$

4. Division  $\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$

5. Reciprocal  $\frac{1}{z} = \frac{1}{r} \angle -\phi$

6. Square root  $\sqrt{z} = \sqrt{r} \angle \phi/2$

7. Complex conjugate  $z^* = x - jy = r \angle -\phi = r e^{-j\phi}$

8. Euler's identity  $e^{\pm j\phi} = \cos \phi \pm j \sin \phi$



# 9.3 Phasor (5)

Example 4 Transform the following sinusoids to phasors:

$$i = 6\cos(50t - 40^\circ) \text{ A}$$

$$v = -4\sin(30t + 50^\circ) \text{ V}$$

Solution:

a)  $i = 6\angle -40^\circ \text{ A}$

b) since  $-\sin(A) = \cos(A + 90^\circ)$

$$v(t) = 4\cos(30t + 50^\circ + 90^\circ) = 4\cos(30t + 140^\circ) = 4\angle 140^\circ$$

# 9.3 Phasor (6)

Example 5 Transform the sinusoids corresponding to phasors:

a.  $\mathbf{V} = -10 \angle 30^\circ \text{ V}$

b.  $\mathbf{I} = j(5 - j12) \text{ A}$

Solution:

a).  $v(t) = 10 \cos(\omega t + 210^\circ) \text{ V}$

Since  $\mathbf{I} = 12 + j5 = \sqrt{12^2 + 5^2} \angle \tan^{-1}\left(\frac{5}{12}\right) = 13 \angle 22.62^\circ$

b).  $i(t) = 13 \cos(\omega t + 22.62^\circ) \text{ V}$



# 9.3 Phasor (7)


The differences between  $v(t)$  and  $V$

- $v(t)$  is instantaneous or time-domain representation  
 $V$  is the frequency or phasor-domain representation.
- $v(t)$  is time dependent,  $V$  is not.
- $v(t)$  is always real with no complex term,  $V$  is generally complex.

Note: Phasor analysis applies only when frequency is constant; when it is applied to two or more sinusoid signals only if they have the same frequency.
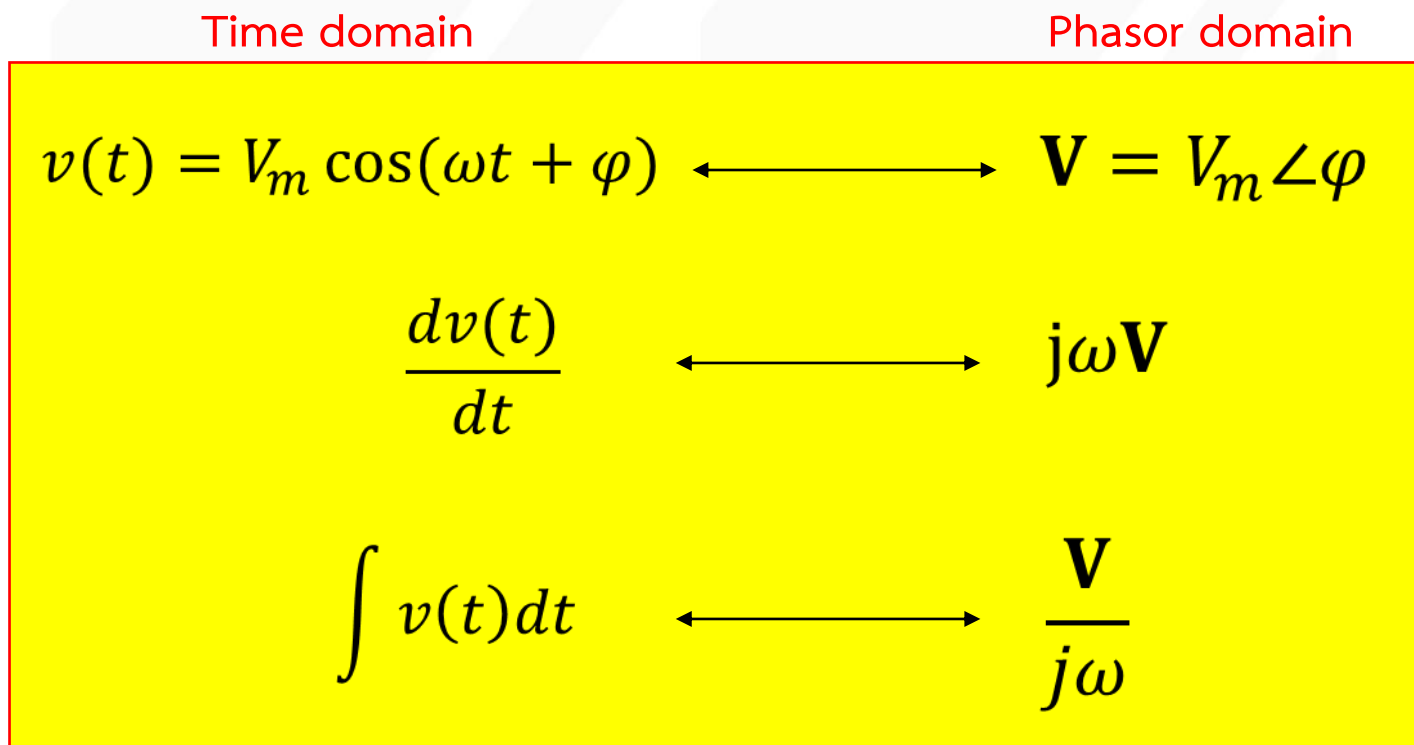
# 9.3 Phasor (8)

Relationship between differential, integral operation in phasor listed as follow:



$$v(t) = V_m \cos(\omega t + \varphi) = \text{Re}(V_m e^{j\varphi} e^{j\omega t}) = \text{Re}(\mathbf{V} e^{j\omega t}) \leftrightarrow \mathbf{V} = V_m \angle \varphi = V_m e^{j\varphi}$$

# 9.3 Phasor (9)

Example 6 Use phasor approach, determine the current  $i(t)$  in a circuit described by the integrodifferential equation.

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

$$4I + 8 \frac{I}{j\omega} - 3j\omega I = 50 \angle 75^\circ$$

$$\omega = 2$$

$$4I - j4I - j6I = 50 \angle 75^\circ$$



$$4I(1 - j - j1.5) = 10.77 \angle -68.2^\circ I = 50 \angle 75^\circ$$

$$I = 4.642 \angle 143.2^\circ \longleftrightarrow i(t) = 4.642 \cos(2t + 143.2^\circ)$$

**Answer:**  $i(t) = 4.642 \cos(2t + 143.2^\circ) \text{ A}$
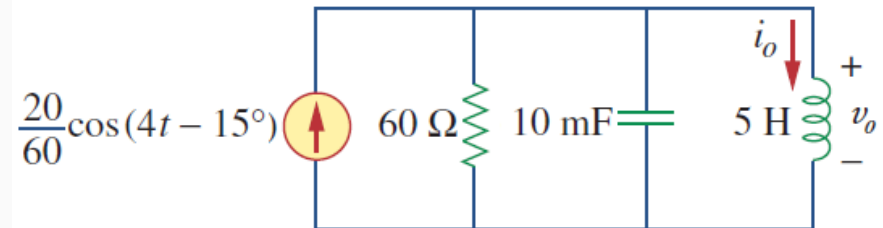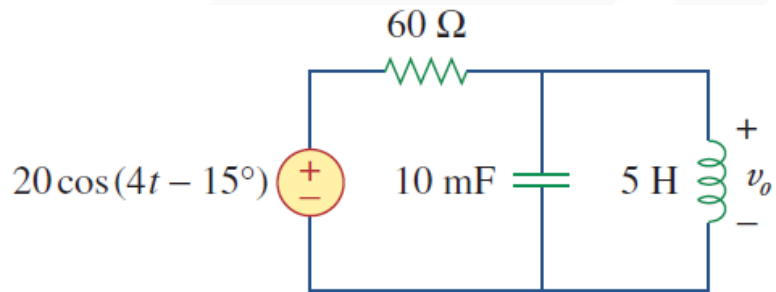
# 9.3 Phasor (10)

We can derive the differential equations for the following circuit in order to solve for  $v_o(t)$  in phasor domain  $V_o$ .



$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

$$\frac{d^2 i_o}{dt^2} + \frac{5}{3} \frac{di_o}{dt} + 20i_o = \frac{20}{3} \cos(4t - 15^\circ)$$

$$v_o = L \frac{di_o}{dt}$$

- However, the derivation may sometimes be very tedious.

Is there any quicker and more systematic methods to do it?



## 9.3 Phasor (11)

The answer is YES!



Instead of first deriving the differential equation and then transforming it into phasor to solve for  $V_o$ , we can transform all the RLC components into phasor first, then apply the KCL laws and other theorems to set up a phasor equation involving  $V_o$  directly.

# 9.4 Phasor Relationships for Circuit Elements (1)






Resistor:

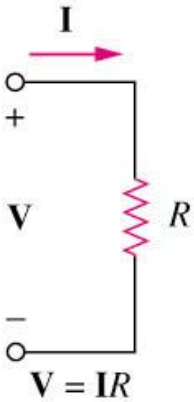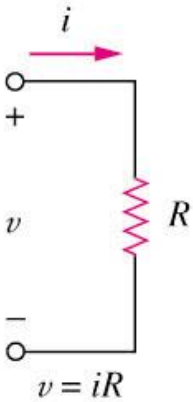

Inductor:

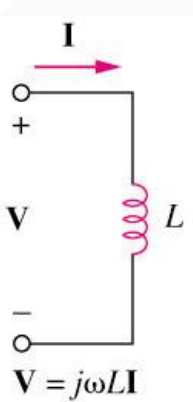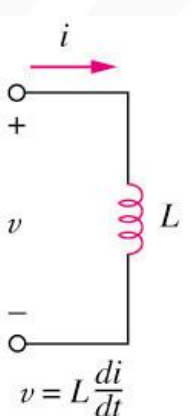

Capacitor:

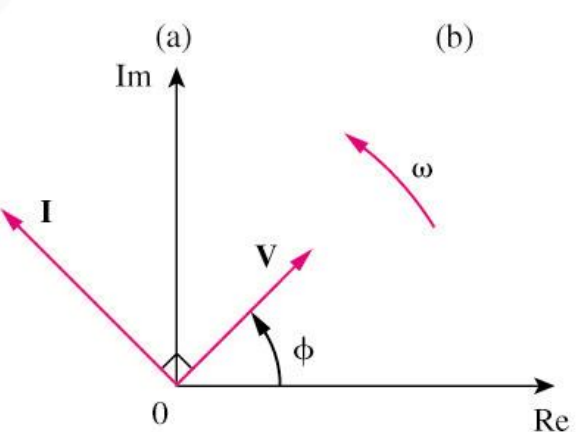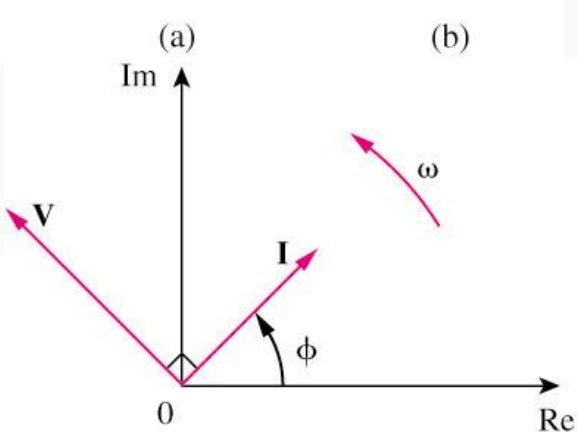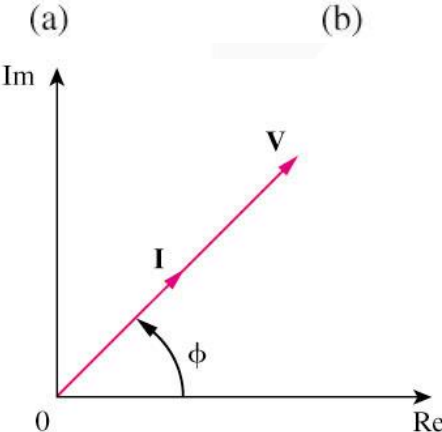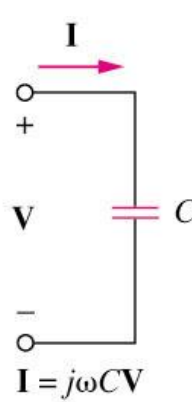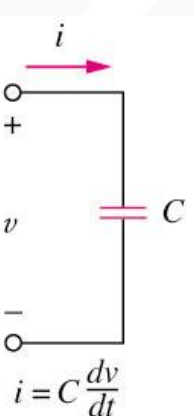

# 9.4 Phasor Relationships for Circuit Elements (2)

## Summary of voltage-current relationship

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

# 9.4 Phasor Relationships for Circuit Elements (3)

## Example 7

If  $v(t) = 6\cos(100t - 30^\circ)$  is applied to a  $50 \mu\text{F}$  capacitor, calculate the current,  $i(t)$ , through the capacitor.

$$I = j\omega CV$$

$$I = j \times 100 \times 50 \times 10^{-6} \times 6 \angle -30^\circ = 0.03 \angle 90^\circ \times \angle -30^\circ = 0.03 \angle 60^\circ$$

$$i(t) = 0.03\cos(100t + 60^\circ)$$

**Answer:  $i(t) = 30 \cos(100t + 60^\circ) \text{ mA}$**



# 9.5 Impedance and Admittance (1)

- The impedance  $Z$  of a circuit is the ratio of the phasor voltage  $V$  to the phasor current  $I$ , measured in ohms  $\Omega$ .

$$Z = \frac{V}{I} = R + jX$$

where  $R = \text{Re}(Z)$  is the resistance and  $X = \text{Im}(Z)$  is the reactance. **Positive  $X$  is for L** and **negative  $X$  is for C**.

- The admittance  $Y$  is the reciprocal of impedance ( $Z$ ),


measured in siemens (S). 
$$Y = \frac{1}{Z} = \frac{I}{V}$$

# 9.5 Impedance and Admittance (2)


## Impedances of elements

Element	Impedance	Admittance
<b>R</b>	$Z = R$	$Y = \frac{1}{R}$
<b>L</b>	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
<b>C</b>	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

# 9.5 Impedance and Admittance (3)


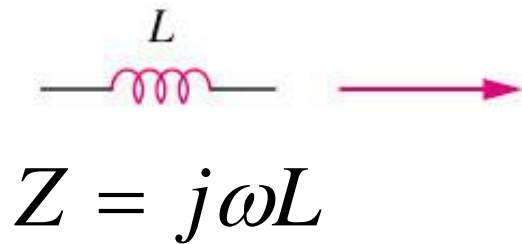


$\rightarrow \omega = 0; Z = 0$

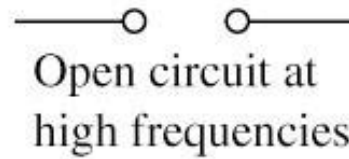


$\rightarrow \omega \rightarrow \infty; Z \rightarrow \infty$

(a)

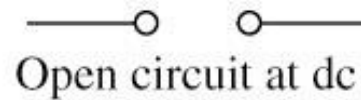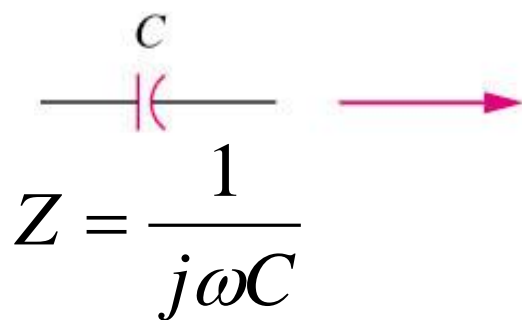

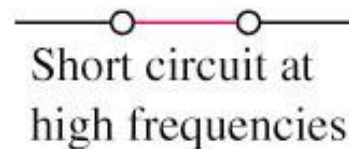$\rightarrow \omega = 0; Z \rightarrow \infty$



$\rightarrow \omega \rightarrow \infty; Z = 0$

(b)


# 9.5 Impedance and Admittance (4)

After we know how to convert RLC components from time to phasor domain, we can transform a time domain circuit into a phasor/frequency domain circuit.

Hence, we can apply the KCL laws and other theorems to directly set up phasor equations involving our target variable(s) for solving.

# 9.5 Impedance and Admittance (5)

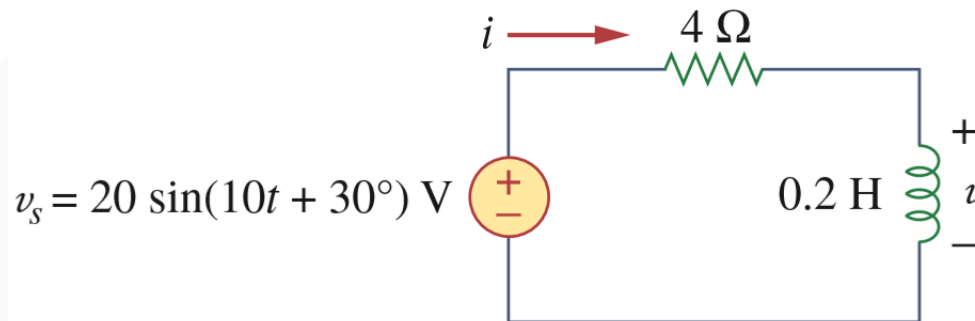Example 8 Refer to Figure below, determine  $v(t)$  and  $i(t)$ .



$$i = \frac{v_s}{Z} = \frac{20 \sin(10t + 30^\circ)}{4 + j2} = \frac{20 \cos(10t + 30^\circ - 90^\circ)}{4 + j2} \times \frac{4 - j2}{4 - j2} = 1 \angle -60^\circ \times 2\sqrt{5} \angle -26.57^\circ$$


$$i = 2\sqrt{5} \angle -86.57^\circ = 4.472 \cos(10t - 86.57^\circ) = 4.472 \sin(10t + 3.43^\circ)$$

$$v = iZ_L = 2\sqrt{5} \angle -86.57^\circ \times j2 = 4\sqrt{5} \angle 3.43^\circ = 8.944 \cos(10t + 3.43^\circ) = 8.944 \sin(10t + 93.43^\circ)$$


**Answers:**  $8.944 \sin(10t + 93.43^\circ)$  V,  $4.472 \sin(10t + 3.43^\circ)$  A.

# 9.5 Impedance and Admittance (6)

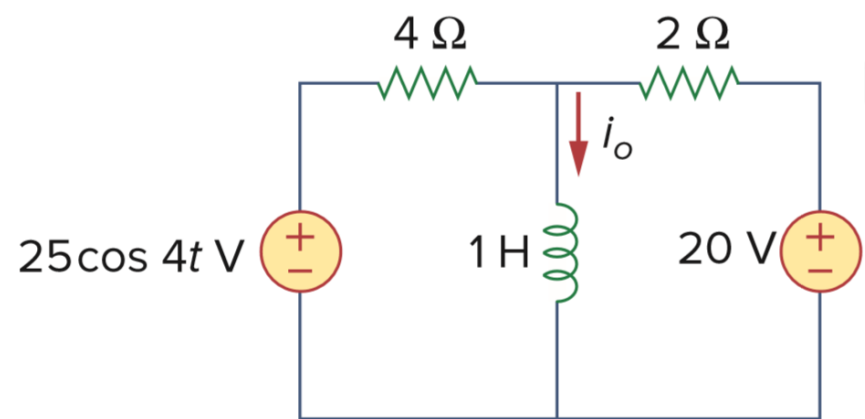Example 9 Find  $i_o$  in the circuit using superposition.




**a**

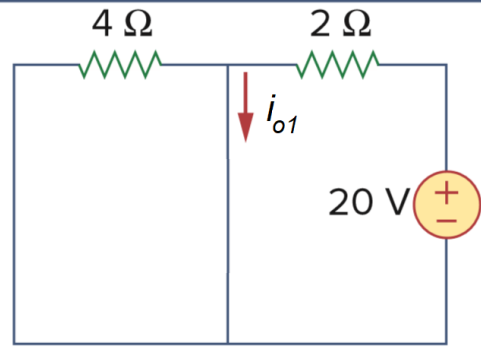

$$i_{o1} = \frac{20}{2} = 10 \text{ A}$$

**b**

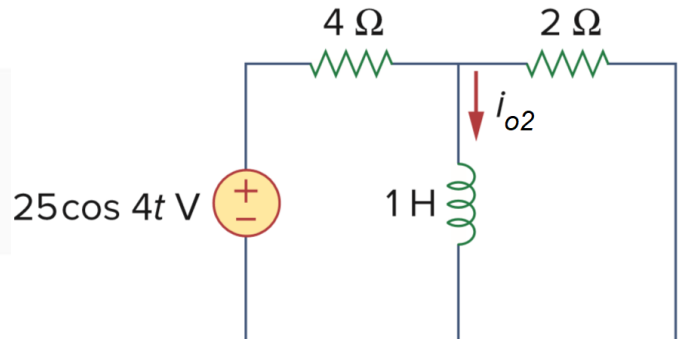

$$\frac{v_{o2} - 25 \cos 4t}{4} + \frac{v_{o2}}{4j} + \frac{v_{o2}}{2} = 0$$

$$0.25v_{o2} - j0.25v_{o2} + 0.5v_{o2} = \frac{25 \cos 4t}{4}$$

$$(0.75 - j0.25)v_{o2} = 6.25 \cos 4t$$

$$v_{o2} = \frac{6.25 \angle 0^\circ}{0.79 \angle -18.4^\circ} = 7.91 \angle 18.4^\circ$$

$$i_{o2} = \frac{7.91 \angle 18.4^\circ}{4j} = \frac{7.91 \angle 18.4^\circ}{4 \angle 90^\circ} = 1.98 \angle -71.6^\circ$$

$$i_o = i_{o1} + i_{o2} = 10 + 1.98 \cos(4t - 71.6^\circ)$$

## 9.6 Kirchhoff's Laws in the Frequency Domain

- Both KVL and KCL are hold in the phasor(frequency) domain.
- Moreover, the variables to be handled are phasors, which are complex numbers.


# 9.7 Impedance Combinations (1)

- The following principles used for DC circuit analysis all apply to AC circuit.
- For example:
  - a. voltage division
  - b. current division
  - c. circuit reduction
  - d. impedance equivalence
  - e. Y- $\Delta$  transformation



# 9.7 Impedance Combinations (2)

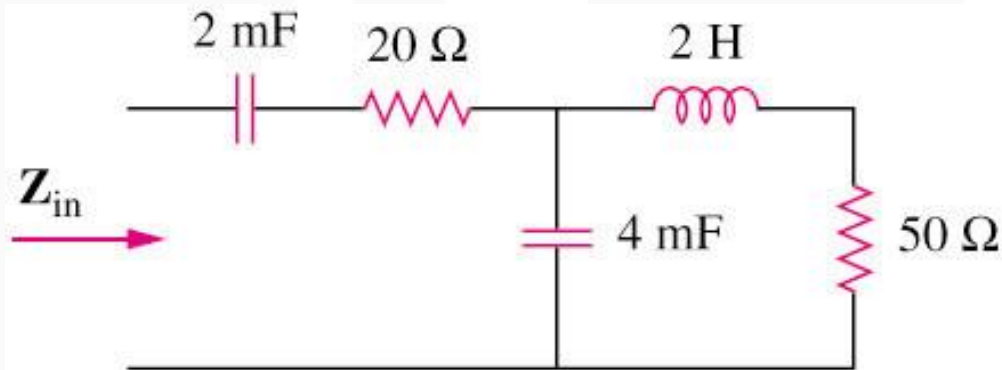Example 9 Determine the input impedance of the circuit in figure below at  $\omega = 10$  rad/s.



Answer:  $Z_{in} = 32.38 - j73.76$